

Magnetically Coupled Circuits

EE 101F19 Lecture 19, Dec 3, 2019


Contents

- Overview, 602
- 11-1 Magnetic Coupling, 602
- 11-2 Magnetic Resonance Imaging (MRI), 608
- 11-3 Transformers, 611
- 11-4 Energy Considerations, 615
- 11-5 Ideal Transformers, 617
- Summary, 622
- Problems, 623

Objectives

Learn to:

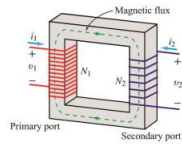- Incorporate mutual coupling in magnetically coupled circuits.
- Analyze circuits containing magnetically coupled coils.
- Relate input to output voltages, currents, and impedances for magnetically coupled transformers, including ideal transformers and three-phase transformers.



When two physically unconnected inductors are in close proximity to one another, current flow through one of them induces a *magnetically coupled voltage* across the other one. Magnetic coupling may be intentional or not. Highly coupled *voltage transformers* used in power distribution networks are an example of intentional coupling. If the coupling between two coils in a circuit is unintentional but significant, its effects should be incorporated into the analysis of the circuit.


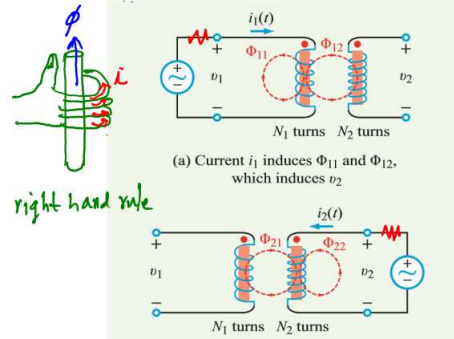
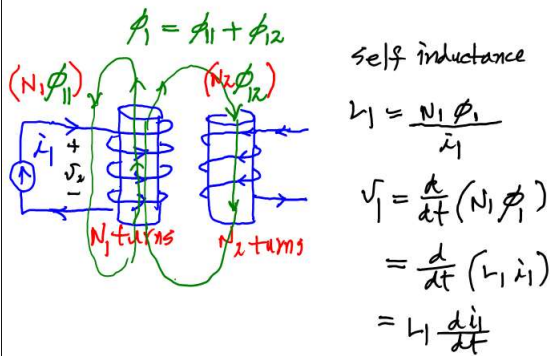
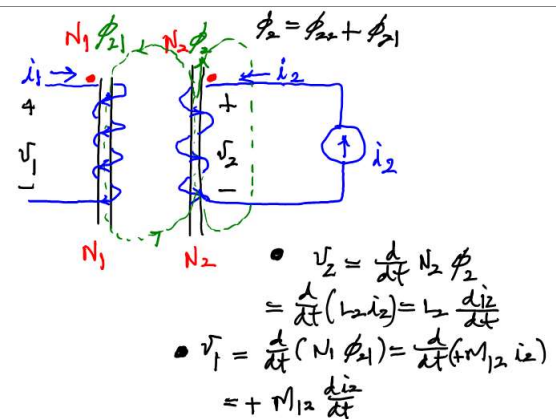


Figure 11-1: Magnetically coupled coils.

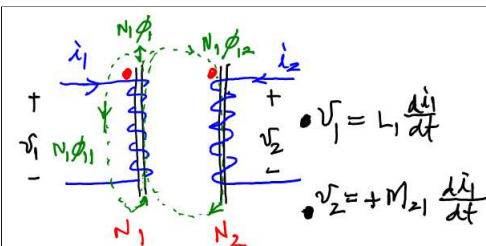


The voltage induced in the secondary coil

$$v_2 = \frac{d}{dt} (N_2 \Phi_{12}) = \frac{d}{dt} (+M_{21} i_1)$$

$$= +M_{21} \frac{di_1}{dt}$$


Usually, $M_{12} = M_{21} = M$

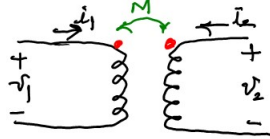


TIME DOMAIN: $v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$

$v_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$


AC Domain

$V_1 = j\omega L_1 I_1 + j\omega M I_2$

$V_2 = j\omega M I_1 + j\omega L_2 I_2$

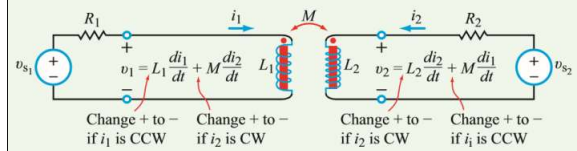

(a) Dots on same ends

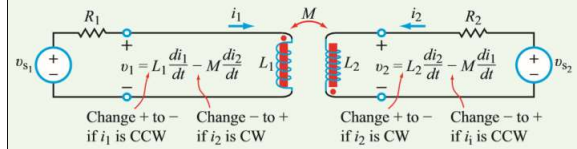

(b) Dots on opposite ends


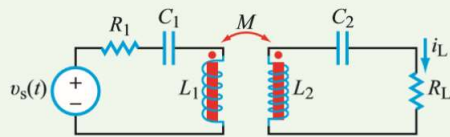
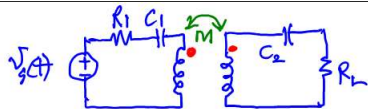


Fig. 11-4(a) Time domain

Example 11-1: 1 kHz Circuit

Determine load current $i_L(t)$ in the circuit of Fig. 11-4(a), given that $v_s(t) = 10 \cos(2\pi \times 10^3 t)$ (V), $R_1 = 5 \Omega$, $C_1 = C_2 = 10 \mu\text{F}$, $L_1 = 1 \text{ mH}$, $L_2 = 3 \text{ mH}$, $M = 0.5 \text{ mH}$, and $R_L = 20 \Omega$.

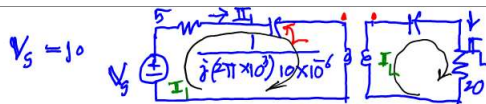

Example 11-1: 1 kHz Circuit

Determine load current $i_L(t)$ in the circuit of Fig. 11-4(a), given that $v_s(t) = 10 \cos(2\pi \times 10^3 t)$ (V), $R_1 = 5 \Omega$, $C_1 = C_2 = 10 \mu\text{F}$, $L_1 = 1 \text{ mH}$, $L_2 = 3 \text{ mH}$, $M = 0.5 \text{ mH}$, and $R_L = 20 \Omega$.

KVL: $-10 + [5 + \frac{1}{j2\pi \times 10^3} + j(4\pi \times 10^3)(1 \times 10^{-3})] I_1 + j(2\pi \times 10^3)(0.5 \times 10^{-3})(-I_L) = 0$

$-j(2\pi \times 10^3)(0.5 \times 10^{-3}) I_1 + \frac{1}{j2\pi \times 10^3} I_L + 20 I_L = 0$

$\frac{1}{j(2\pi \times 10^3)(10 \times 10^{-6})} = -j \frac{100}{2\pi} = -j \frac{50}{\pi} (= Z_C)$

$(\frac{1}{j} = \frac{-(-1)}{j} = \frac{-j^2}{j} = -j)$

20Ω

$j\omega L_2 = j(2\pi \times 10^3)(3 \times 10^{-3}) = j6\pi$

RLC $\rightarrow (20 - j \frac{50}{\pi} + j6\pi) I_L$

$= 20 + j(6\pi - \frac{50}{\pi})$

As was noted earlier in connection with Fig. 11-1(a), current I_1 through coil 1 generates magnetic fluxes Φ_{11} through coil 1 and Φ_{12} through both coils 1 and 2. The coupling coefficient is given by

$$k = \frac{\Phi_{12}}{\Phi_{11} + \Phi_{12}} = \frac{\Phi_{12}}{\Phi_1} \quad (11.20a)$$

where $\Phi_1 = \Phi_{11} + \Phi_{12}$. The perfectly coupled case corresponds to when the flux coupled to coil 2, namely Φ_{12} , is equal to the self-coupled flux Φ_1 . Similarly, from the standpoint of coil 2,

$$k = \frac{\Phi_{21}}{\Phi_{22} + \Phi_{21}} = \frac{\Phi_{21}}{\Phi_2} \quad (11.20b)$$


Through energy considerations, k can be related to L_1 , L_2 , and M as

$$k = \frac{M}{\sqrt{L_1 L_2}} \quad (11.21)$$


The mutual inductance M is a maximum when $k = 1$ (perfectly coupled transformer),

$$M(\max) = \sqrt{L_1 L_2} \quad (11.22)$$

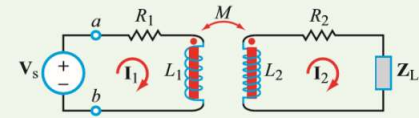(perfectly coupled transformer with $k = 1$)



(a) Original circuit

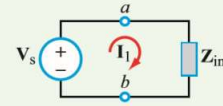

(b) Equivalent circuit

Figure 11-8: (a) Transformer circuit with coil resistors R_1 and R_2 , and (b) in terms of an equivalent input impedance Z_{in} .

$$-V_s + (R_1 + j\omega L_1)I_1 - j\omega M I_2 = 0 \quad (11.23a)$$

and

$$-j\omega M I_1 + (R_2 + j\omega L_2 + Z_L)I_2 = 0. \quad (11.23b)$$


From the standpoint of source V_s , the circuit to the right of terminals (a, b) can be represented by an equivalent **input impedance** Z_{in} , as depicted in Fig. 11-8(b). By manipulating Eqs. (11.23) to eliminate I_2 , we can generate the following expression for Z_{in} :

$$\begin{aligned} Z_{in} = \frac{V_s}{I_1} &= (R_1 + j\omega L_1) + \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L} \\ &= (R_1 + j\omega L_1) + Z_R, \end{aligned} \quad (11.24)$$


where we define the second term as the **reflected impedance** Z_R , namely

$$Z_R = \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L} \quad (11.25)$$

(a) Transformer

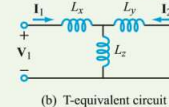

(b) T-equivalent circuit

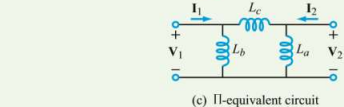

(c) Pi-equivalent circuit

Figure 11-10: The transformer can be modeled in terms of T- or Pi-equivalent circuits.

Transformer dots on same ends

$$L_x = L_1 - M, \quad (11.29a)$$

$$L_y = L_2 - M, \quad (11.29b)$$

and

$$L_z = M. \quad (11.29c)$$


Transformer with dots on same ends

$$L_a = \frac{L_1 L_2 - M^2}{L_1 - M}, \quad (11.31a)$$

$$L_b = \frac{L_1 L_2 - M^2}{L_2 - M}, \quad (11.31b)$$

and

$$L_c = \frac{L_1 L_2 - M^2}{M}. \quad (11.31c)$$

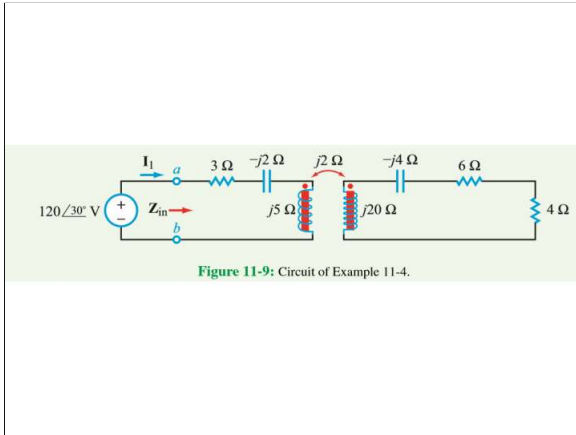

Example 11-5: Equivalent Circuit

Use the T-equivalent circuit model to determine I_1 in the circuit of Fig. 11-11.

Solution: Use of Eq. (11.29) gives

$$j\omega L_x = j\omega L_1 - j\omega M = j5 - j2 = j3 \, \Omega,$$

$$j\omega L_y = j\omega L_2 - j\omega M = j20 - j2 = j18 \, \Omega,$$

and

$$j\omega L_z = j\omega M = j2 \, \Omega.$$


The T-equivalent circuit is shown in Fig. 11-11(b). Application of the mesh analysis by-inspection method leads to the matrix equation

$$\begin{bmatrix} (3 - j2 + j3 + j2) & -j2 \\ -j2 & (j2 + j18 - j4 + 6 + 4) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 120\angle 30^\circ \\ 0 \end{bmatrix}.$$

Its solution is

$$I_1 = 28.6e^{-j12.2^\circ} \text{ A}.$$

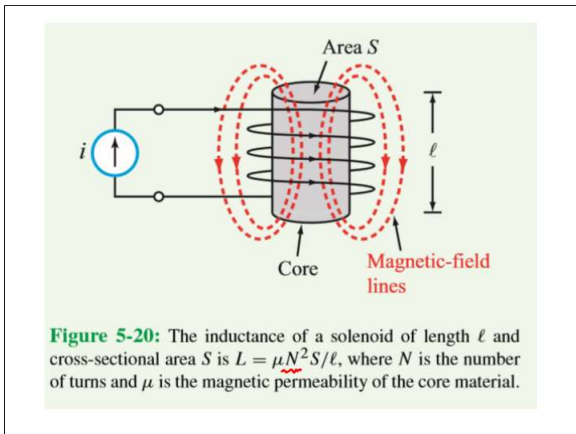Handwritten notes: A phasor diagram shows a vector of magnitude 30 at 30 degrees. Calculations show $\cos 30^\circ = \frac{\sqrt{3}}{2}$ and $\sin 30^\circ = \frac{1}{2}$. The matrix equation is solved using Cramer's rule, resulting in $I_1 = \frac{60\sqrt{3} + j60}{3 + j3 - j2} = \frac{100\sqrt{3} - j2}{10 + j16}$.



11-4 Ideal Transformers

An ideal transformer is characterized by lossless coils ($R_1 = R_2 = 0$) and a maximum coupling coefficient $k = 1$. The mutual inductance M is a maximum and given by Eq. (11.22) as

$$M(\max) = \sqrt{L_1 L_2}. \quad (11.34)$$

(ideal transformer)

According to Eq. (5.52), the inductance L of a solenoid-shaped inductor is proportional to N^2 , where N is the number of turns wound around the core. Hence, for an ideal transformer with N_1 turns on the primary side and N_2 on the secondary, as depicted in Fig. 11-14,

$$\frac{L_2}{L_1} = \frac{N_2^2}{N_1^2} = n^2, \quad (11.35)$$

where $n = N_2/N_1$ is called the turns ratio.

The transformer is called a step-up transformer ($V_2 > V_1$) when $n > 1$ and a step-down transformer ($V_2 < V_1$) when $n < 1$.

For a lossless transformer, complex power S_1 supplied by its primary side must match complex power S_2 absorbed by its secondary:

$$S_1 = S_2, \quad (11.37)$$

or equivalently

$$V_1 I_1^* = V_2 I_2^*. \quad (11.38)$$

In view of Eq. (11.36), it follows that

$$\frac{I_2}{I_1} = \frac{1}{n} \quad (\text{ideal transformer with dots on same ends}), \quad (11.39)$$

The expressions for the voltage and current ratios given by Eqs. (11.36) and (11.39) apply to the current directions, voltage polarities and dot locations indicated in both configurations of Fig. 11-14.

Self-inductance refers to the magnetic-flux linkage of a coil (or circuit) with itself, in contrast with **mutual inductance**, which refers to magnetic-flux linkage in a coil due to the magnetic field generated by another coil (or circuit). Usually, when the term **inductance** is used, the intended reference is to self-inductance. Mutual inductance is covered in Chapter 11.

The (self) inductance of any conducting system is defined as the ratio of Λ to the current i responsible for generating it, given as

$$L = \frac{\Lambda}{i} \quad (\text{H}), \quad (5.51)$$

and its unit is the henry (H), so named to honor the American inventor Joseph Henry (1797–1878). Using the expression for Λ given by Eq. (5.50), we have

$$L = \frac{\mu N^2 S}{\ell} \quad (\text{solenoid}), \quad (5.52)$$

The inductance L is directly proportional to μ , the magnetic permeability of the core material. The relative magnetic permeability μ_r is defined as

$$\mu_r = \frac{\mu}{\mu_0}, \quad (5.53)$$

where $\mu_0 = 4\pi \times 10^{-7}$ (H/m) is the magnetic permeability of free space.