



Solution

ECE101F19 Quiz 8, Nov. 21, 2019

Name _____

Student ID _____

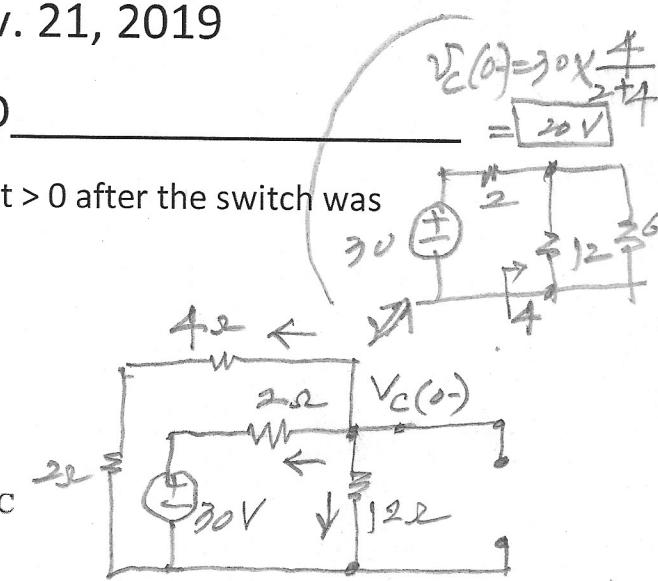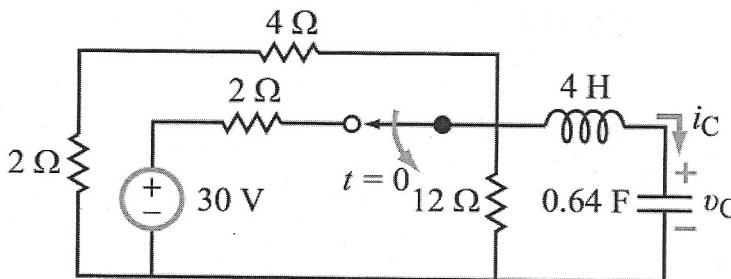For the RLC circuit below, let us consider $v_C(t)$ for $t > 0$ after the switch was opened at $t=0$.



(1)(2 points) Find the current $v_C(0-)$.

$$v_C(0-) = 20 \text{ [V]}$$

$$\frac{v_C(0-)}{6} + \frac{v_C(0-)}{2} + \frac{v_C(0-)}{12} = 0$$

$$\times 12 \Rightarrow 2v_C(0-) + 6v_C(0-) - 180 + v_C(0-) = 0$$

$$9v_C(0-) = 180$$

$$\boxed{v_C(0-) = 20}$$

(2)(4 points) Write down the differential equation for $v_C(t)$ for $t > 0$.

6

$$30 - 2i - 12i - 4\frac{dv_C}{dt} - 0.64\frac{d^2v_C}{dt^2} = 0$$

$$\frac{d^2v_C}{dt^2} + \frac{4 \cdot 0.64}{2 \cdot 0.64} \frac{dv_C}{dt} + \frac{1}{2 \cdot 0.64} v_C = 0$$

$$\frac{d^2v_C}{dt^2} + 2.56 \frac{dv_C}{dt} + \frac{1}{2.56} v_C = 0$$

(3)(2 points) Is the differential equation in (2) overdamped, critically damped, or underdamped?

$$\omega = \frac{1}{2} \quad \omega_0 = \frac{1}{\sqrt{2.56}} = \frac{1}{2 \times 0.8} = \frac{1}{1.6}$$

$\omega < \omega_0$, underdamped

(4)(2 points) Find $v_C(\infty)$ by inspection of the circuit for $t > 0$.

$$v_C(\infty) = 0$$