

Solution

ECE101F19 Quiz 9, Dec. 3, 2019

Name _____ Student ID _____

We want to find the voltage between terminals a and b in time domain. But, since this quiz is only for 15 minutes, we will solve for the following sub-problems in parts 1 and 2.

- *7.32 Find voltage $v_{ab}(t)$ in the circuit of Fig. P7.32, given that $i_s(t) = 35 \sin(300t - 15^\circ)$ mA, $R = 80 \Omega$, $L = 15 \text{ mH}$, and $C = 200 \mu\text{F}$.

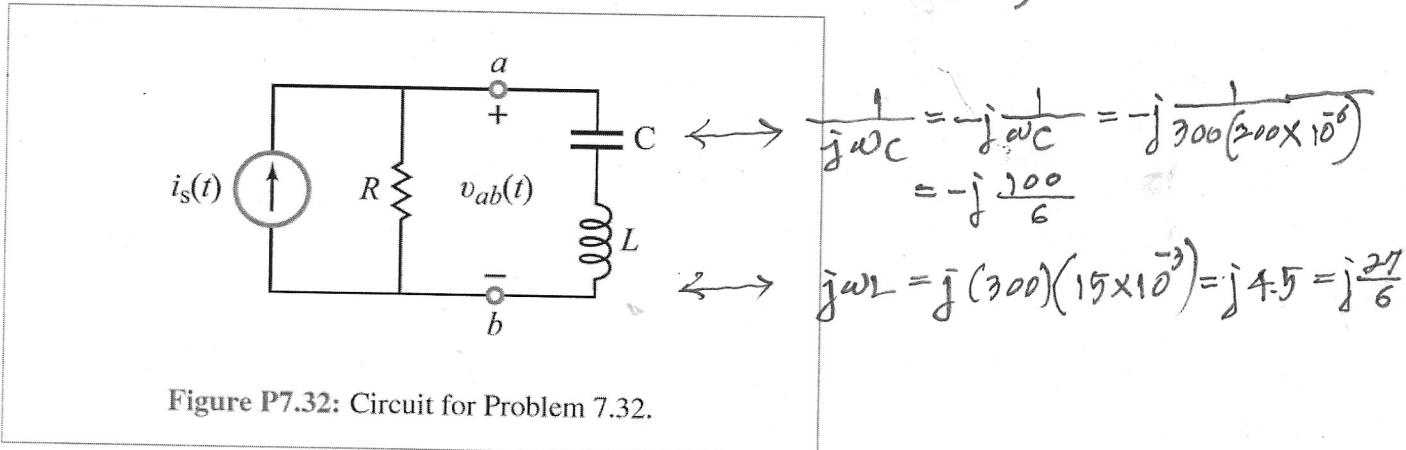


Figure P7.32: Circuit for Problem 7.32.

Part 1. (3 points) Find the phasor expression in polar form I_S for $i_s(t)$ with the correct magnitude unit. Recall that the reference function is cosine function in our phasor method.

$$i_s(t) = 35 \sin(300t - 15^\circ) = 35 \cos(300t - 15^\circ - 90^\circ) = 35 \cos(300t - 105^\circ)$$

$$I_S = 35 e^{-j105^\circ} = 35 \angle -105^\circ$$

Part 2. (3 points) Find the total impedance between a and b in polar form. You can just show the phase information in arctan form without finding the angle.

$$\begin{aligned} Z_{ab} &= 80 \parallel \left(-j\frac{100}{6} + j\frac{27}{6}\right) = 80 \parallel \left(-j\frac{73}{6}\right) = \frac{80 \left(-j\frac{73}{6}\right)}{80 - j\frac{73}{6}} = \frac{-j5840}{480 - j73} \\ &= \frac{5860 e^{-j90^\circ}}{\sqrt{480^2 + (-73)^2}} e^{-j\arctan\left(\frac{73}{480}\right)} = \frac{5860 e^{-j90^\circ}}{485.56 e^{j0^\circ - 186^\circ}} \\ &= 12.07 e^{-j88.14^\circ} \end{aligned}$$

Part 3. (4 points) Find V_{ab} in phasor form in polar form.

$$V_{ab} = Z_{ab} I_S = (12.07 e^{-j88.14^\circ})(35 e^{-j105^\circ}) = 422.45 e^{-j193.14^\circ}$$

$$v_{ab}(t) = 422.45 \cos(300t - 193.14^\circ) = 422.45 \sin(300t - 103.14^\circ)$$