

ECE 101

Norton and Thevenin equivalent circuits

Thursday 27 October

Sara Abrahamsson (guest lecturing for Steve Kang)
<https://saralab.soe.ucsc.edu/>

How do we deal with this?

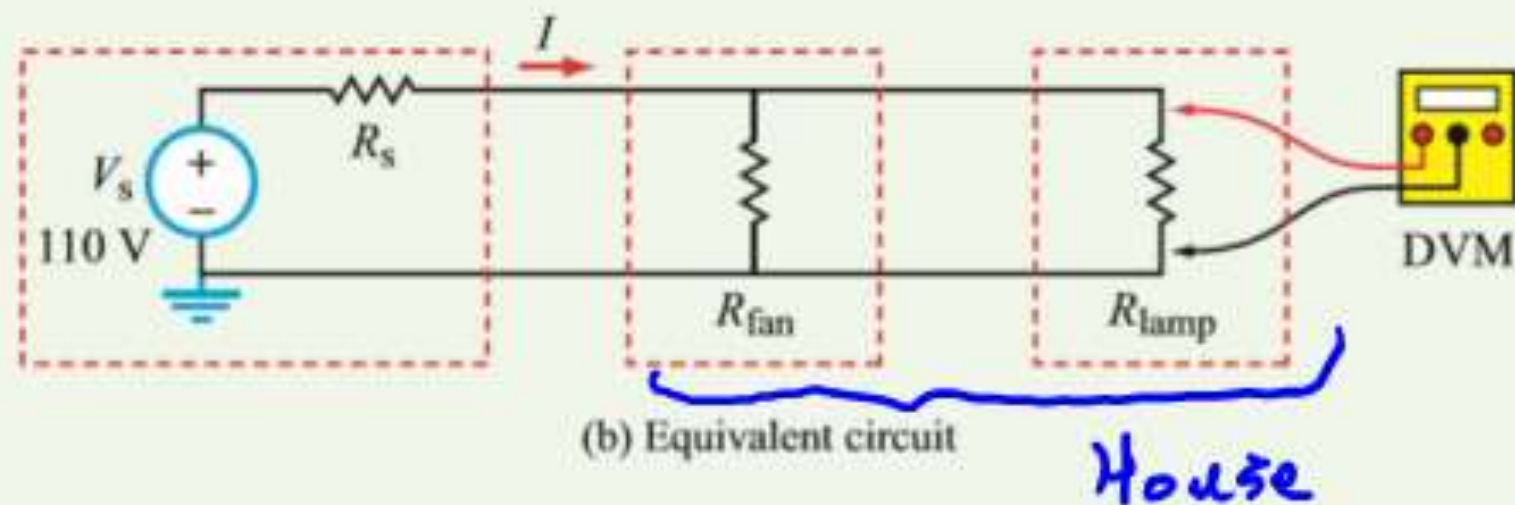
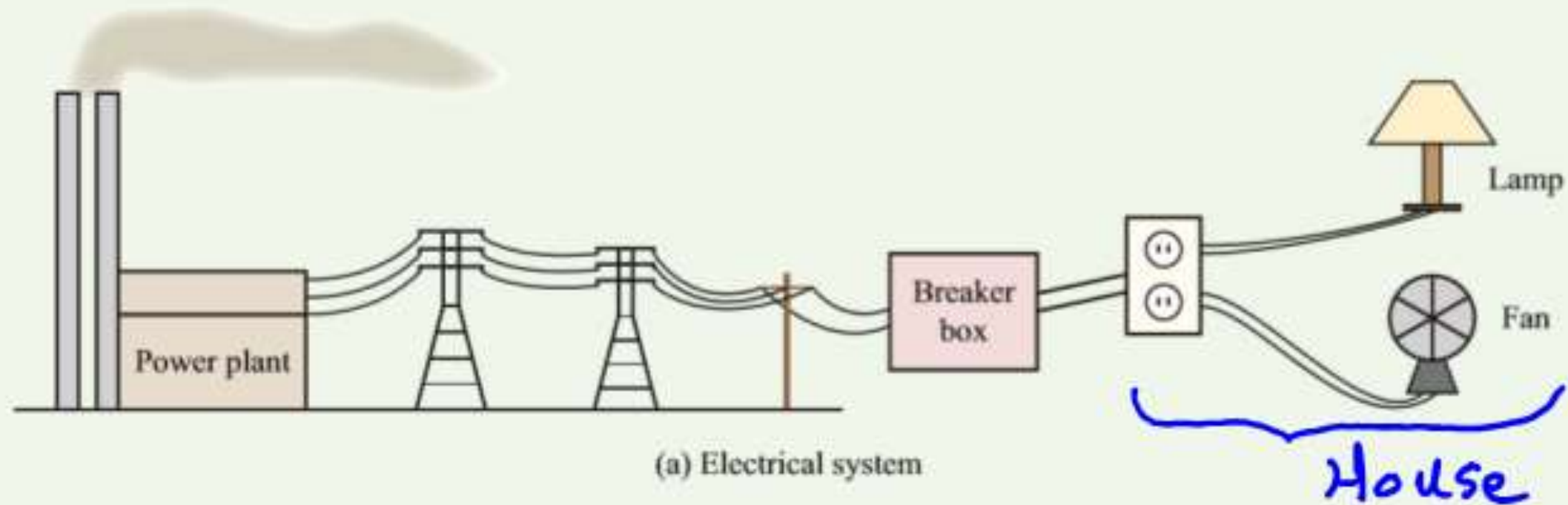


Figure 3-19: (a) Power distribution system driving a fan and a lamp in a house, and (b) block diagram of the source (power distribution system), fan, lamp, and a voltmeter measuring the voltage in the outlet.


Dealing with Variable Load

- In many circuits, one element will be **variable**
- In the example of mains power: many different appliances may be plugged into an outlet, each presenting a different resistance. This variable element is called the **load**
- Ordinarily one would have to reanalyze the circuit for each change in the load...

Thevenin's Theorem


- Thevenin's theorem allows us to simplify a large circuit and replaced it with a single independent voltage source and a single resistor.
- The equivalent circuit behaves externally as the original circuit.

Thevenin circuit

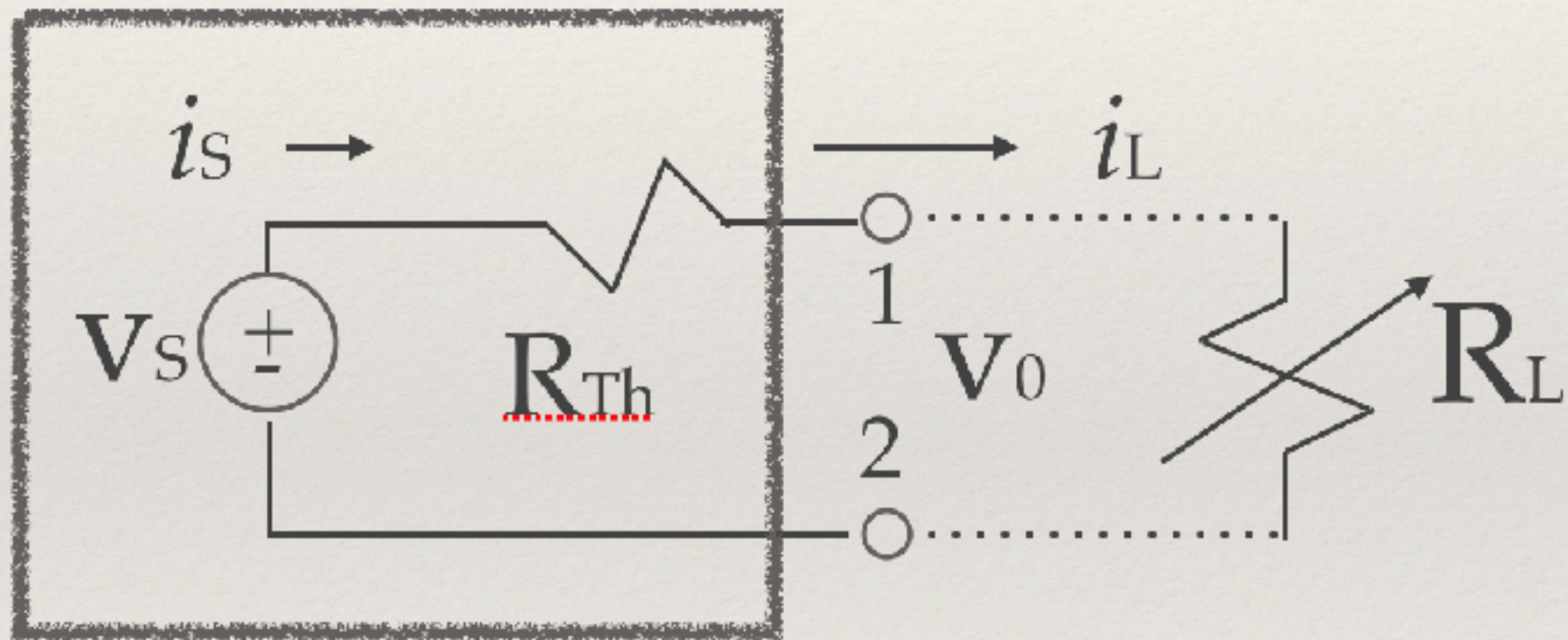

Thevenin's Theorem

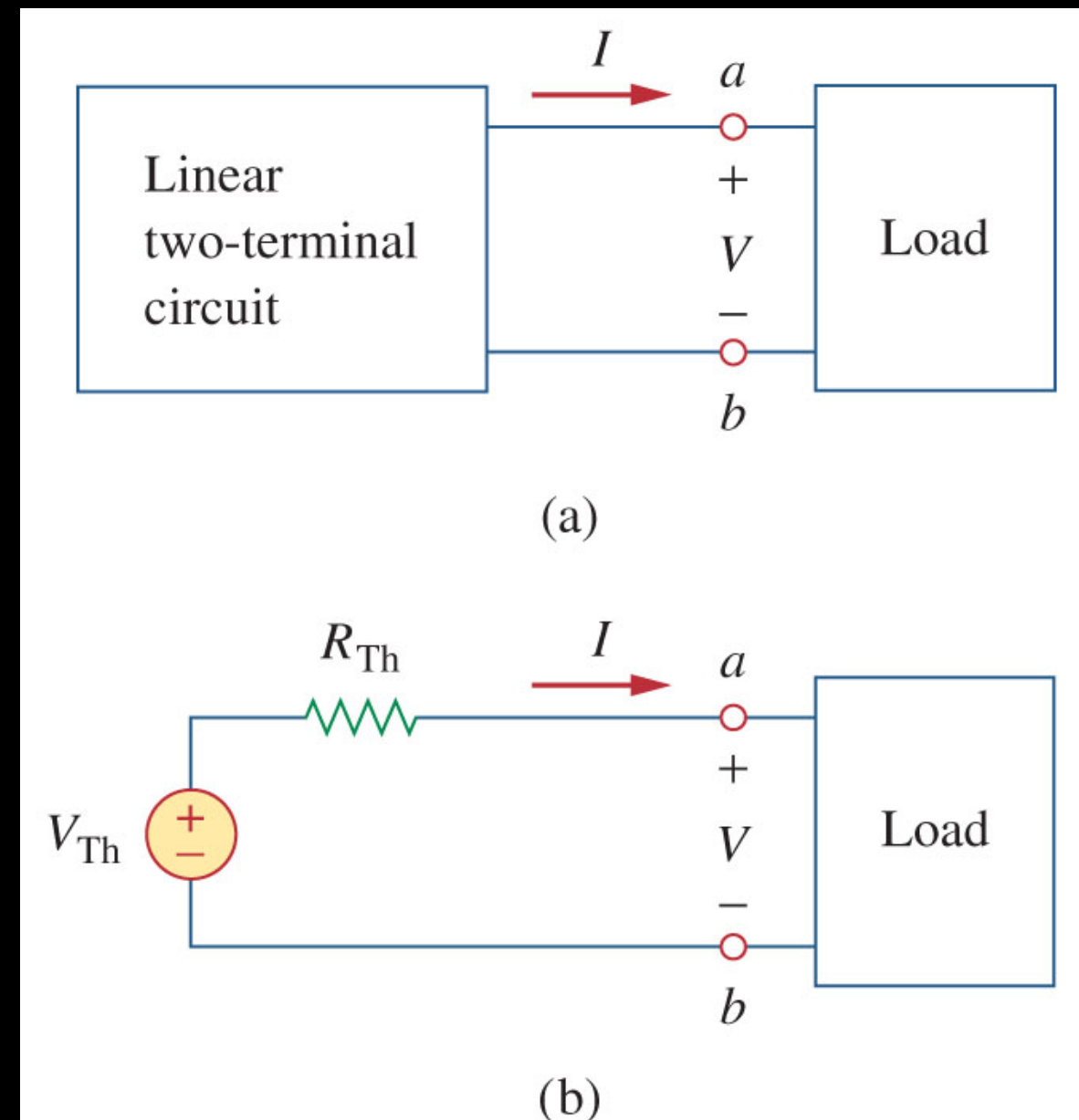
- Thevenin's theorem states that a linear two terminal circuit may be replaced with a **voltage source and resistor**
- The voltage source's value is equal to the open circuit voltage at the terminals
- The resistance is equal to the resistance measured at the terminals when the independent sources are turned off.



Finding R_{Th} for Thevenin

Case 1:

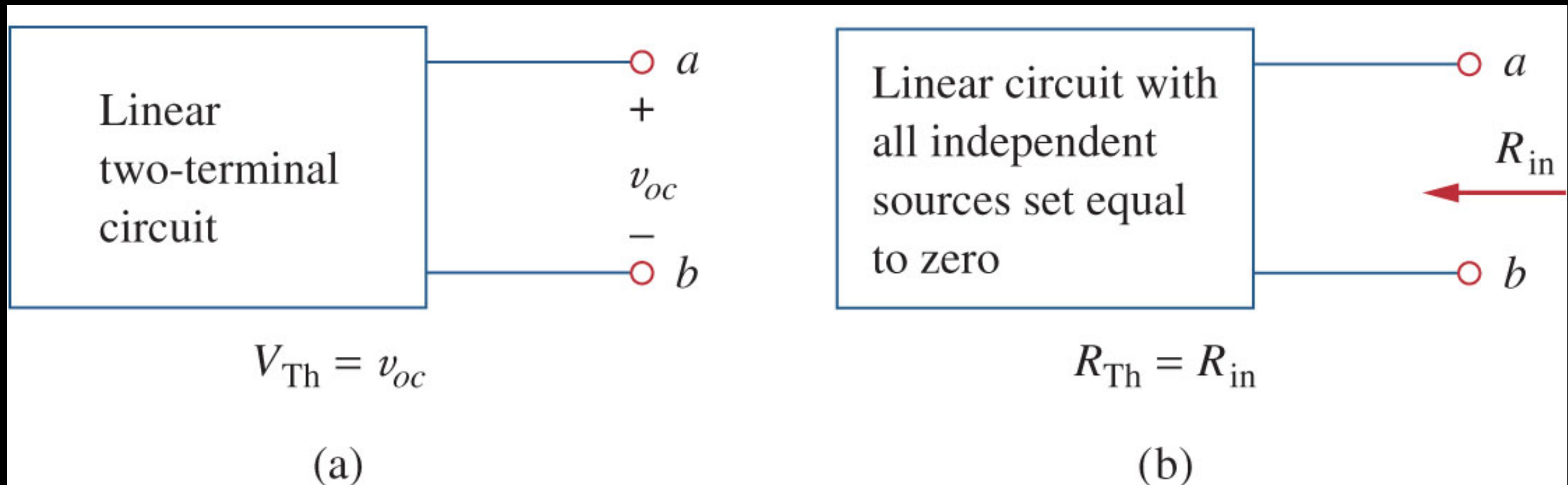If there are **no dependent sources** the resistance R_{Th} may be found by simply turning off all the sources:




Finding R_{eq} for Thevenin

Case 2:


If there are **dependent sources**: to find the resistance R_{Th} we

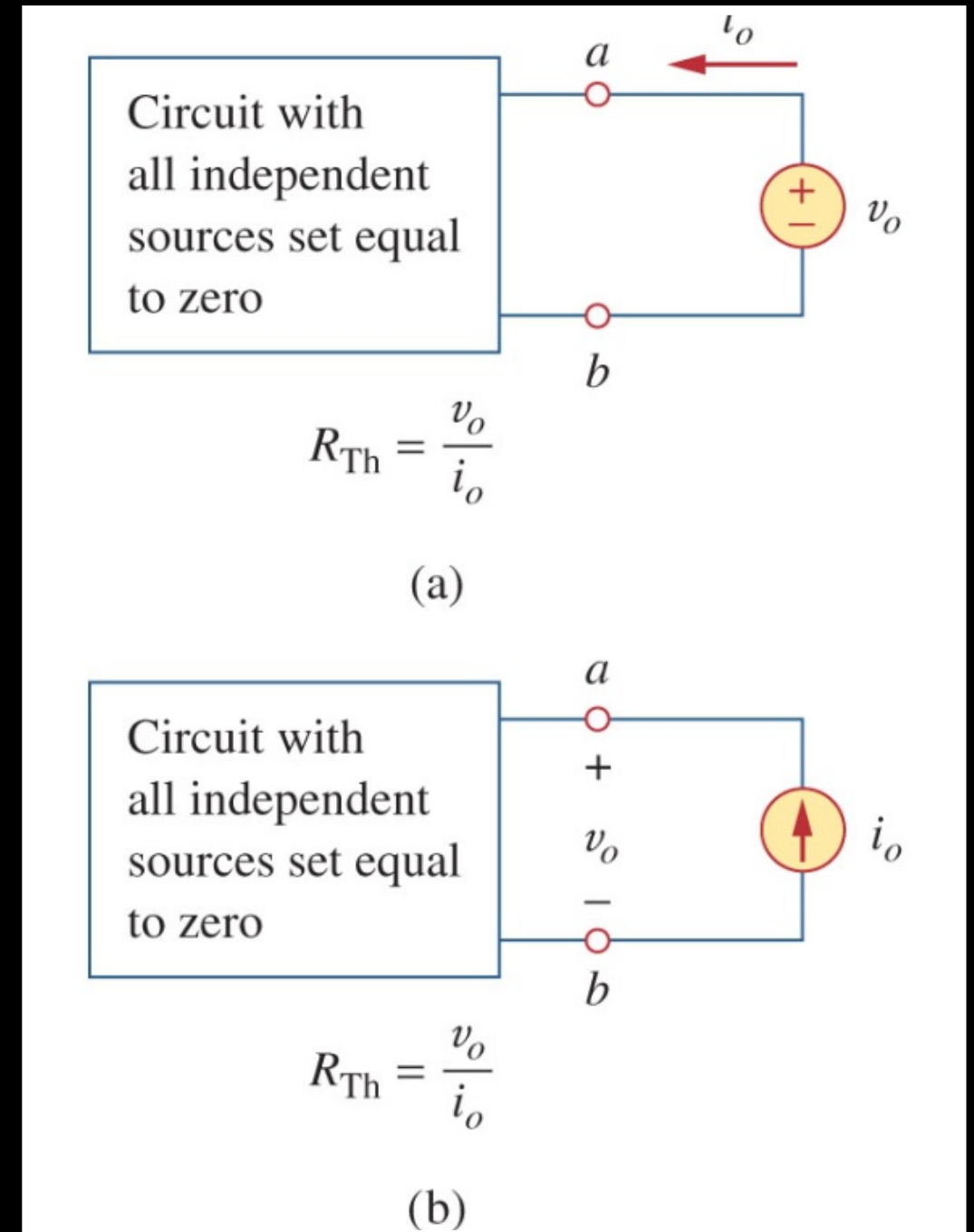- Turn off all the sources (like before, and then...)
- Apply a voltage v_o (or current i_o) to the terminals and then determine the current i_o (or voltage v_o)



Finding V_{Th} for Thevenin

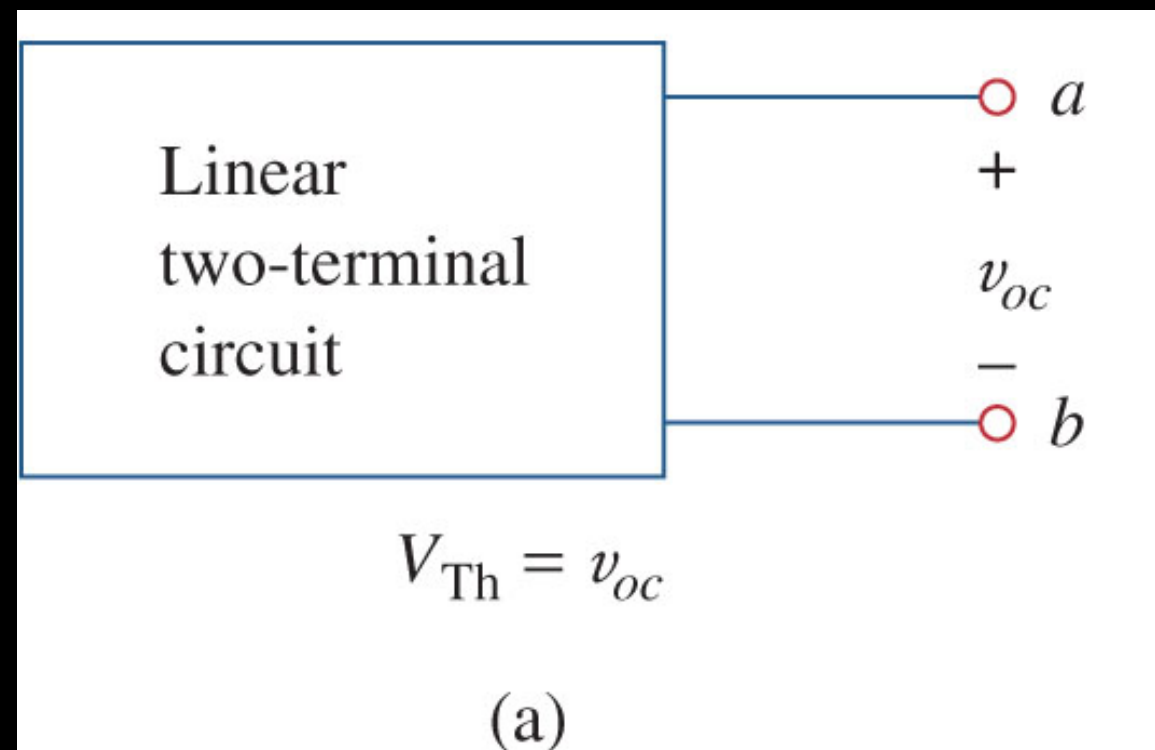- V_{Th} (voltage source's value) is equal to the open circuit voltage at the terminals





Negative Resistance?

- If we find a **negative resistance** this implies the circuit is **supplying power**
- This is reasonable with dependent sources

Example of Thevenin equivalent circuit

Find Thevenin equivalent circuit:

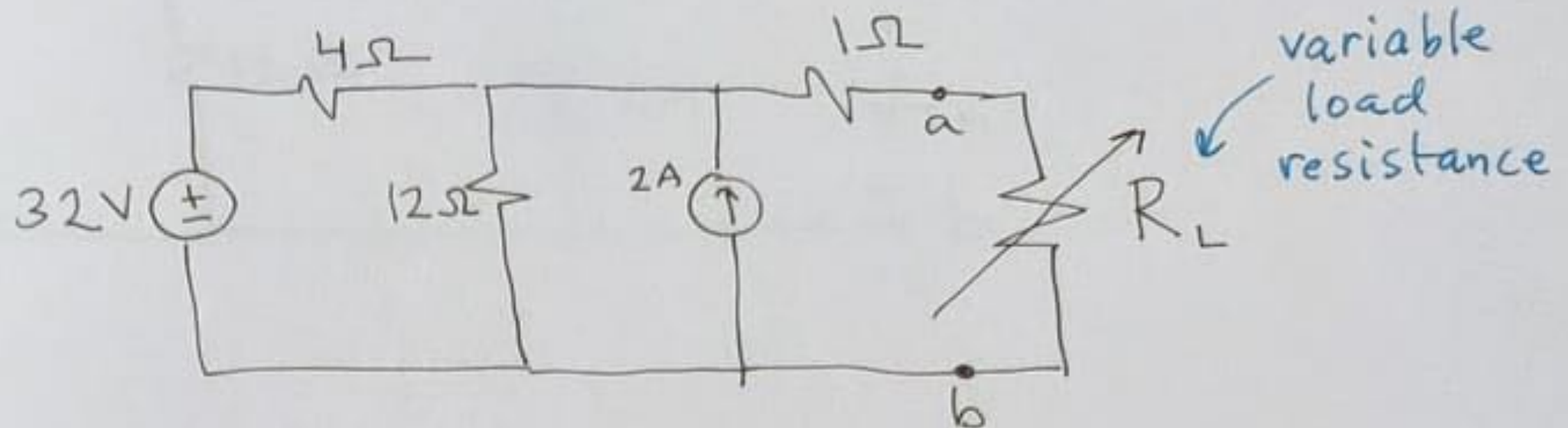


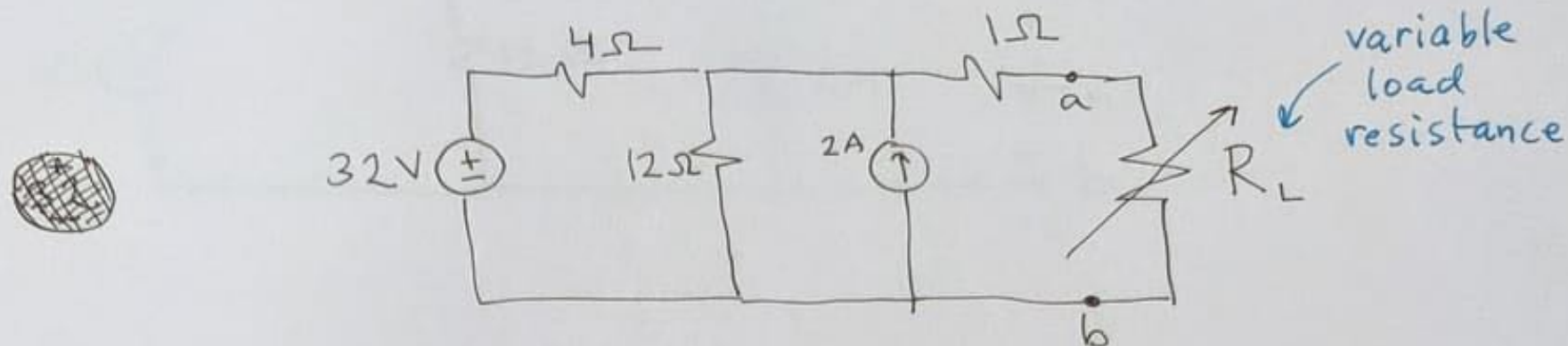

To find R_{Th} : ~~use~~ ^(Thevenin equiv.) (resistance at terminal a b)

We find the resistance of the circuit at the terminal ab when ab is open and all independent sources are turned off.

Redraw the circuit:

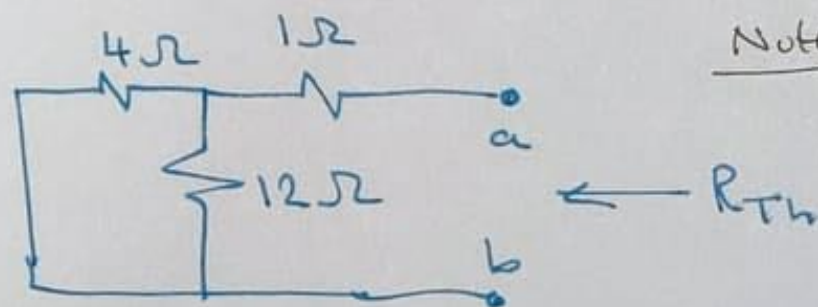


Note: We turn off the 32V voltage source. Ideal voltage source has zero internal resistance so we replace it with short circuit.

We turn off the 2A current source. Ideal current source has ∞ infinite internal resistance so we replace with open circuit.

We have 4Ω and 12Ω in parallel and this in series with 1Ω \Rightarrow

$$\begin{aligned} \underline{\underline{R_{Th}}} &= 4 \parallel 12 + 1 = \frac{4 \cdot 12}{4 + 12} + 1 = \\ &= \frac{4 \cdot 4 \cdot 3}{\cancel{4 \cdot 4}} + 1 = 3 + 1 = \underline{\underline{4 [\Omega]}} \end{aligned}$$

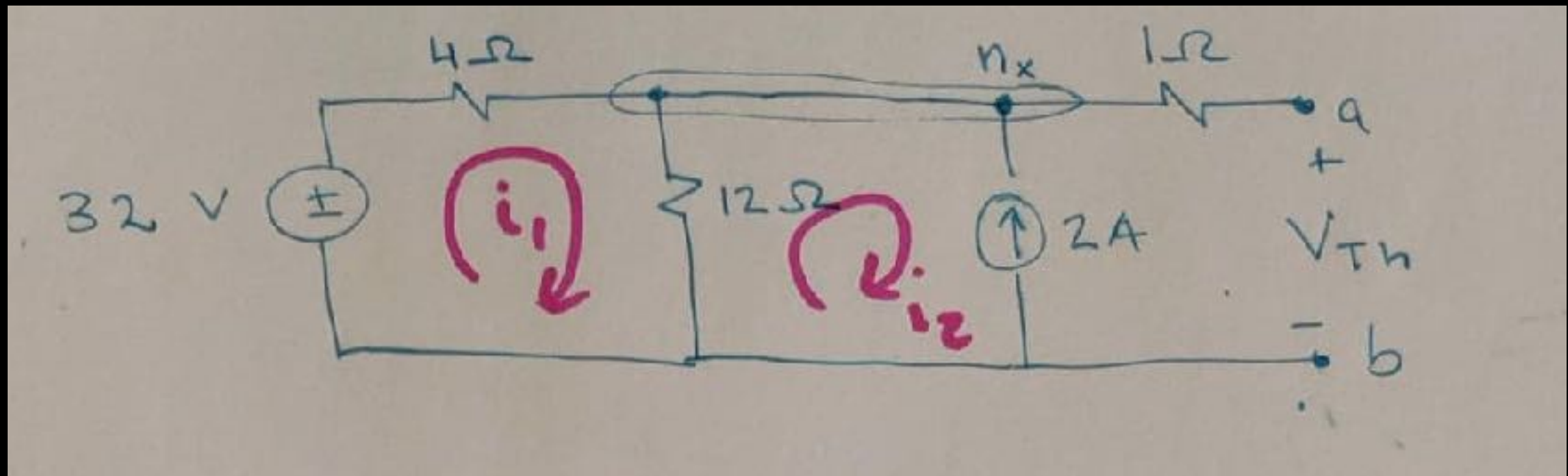- We have found R_{Th} , now we need to find V_{Th} which is the open circuit voltage at the a b terminal
- We can for example do this using mesh analysis. Set up KVL at the loops 1 and 2:



MESH ANALYSIS:

$$\begin{cases} -32 + 4i_1 + 12(i_1 - i_2) = 0 \\ i_2 = -2[A] \end{cases}$$

$$-32 + 4 \cdot i_1 + 12(i_1 + 2) =$$

$$\cancel{12i_1} - 32 + 4i_1 + 12i_1 + 24 =$$

$$= 16i_1 \cancel{+ 12i_1} - 8$$



$$\Rightarrow i_1 = \cancel{\frac{8}{16}} = +\frac{8}{16} = \frac{1}{2} [A]$$

Voltage at node n_x is same as V_{Th} since there is no current flowing across the 1Ω resistor.


$$\Rightarrow V_{Th} = 12(i_1 - i_2) = 12(0.5 - (-2)) = 12 \times 2.5 = 30[V]$$


↑ voltage drop across 12Ω resistor

We get the Thevenin equivalent circuit:

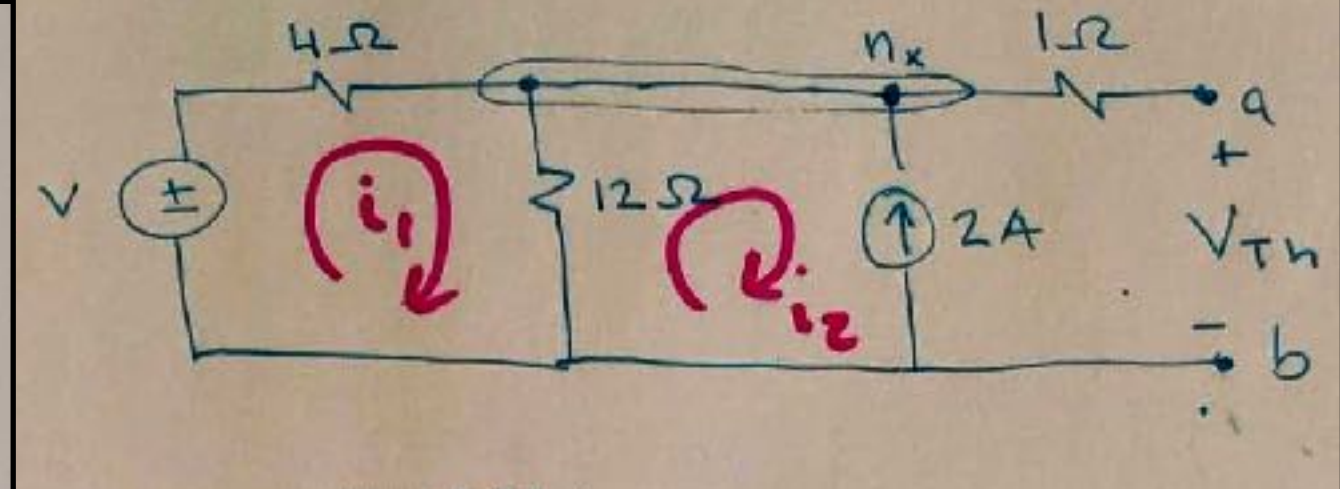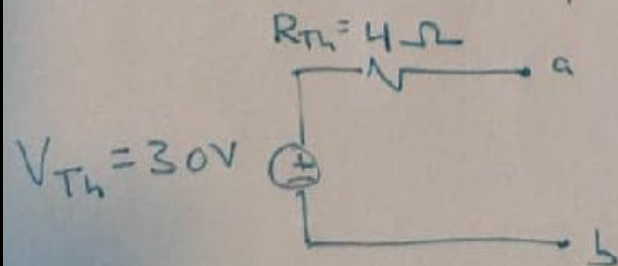

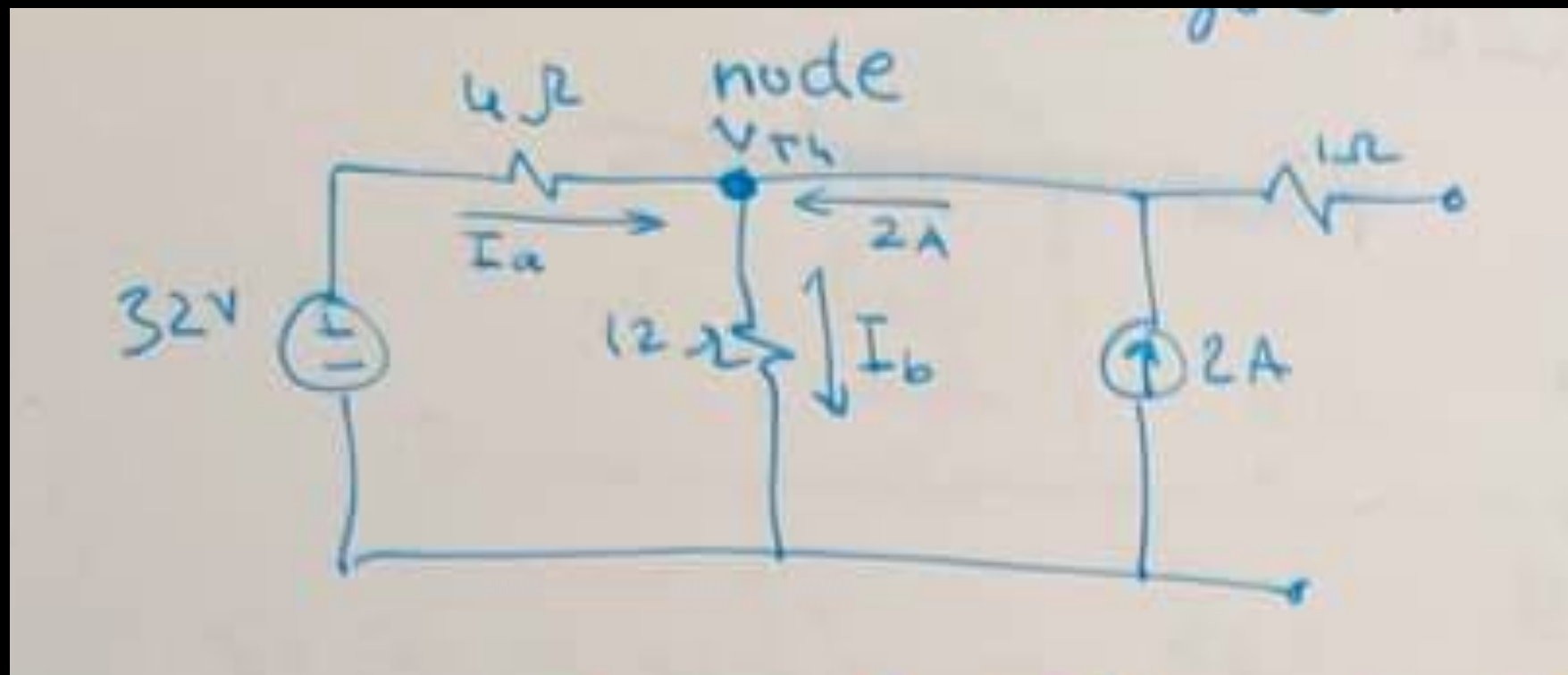- Alternatively, we can find V_{Th} using nodal analysis:



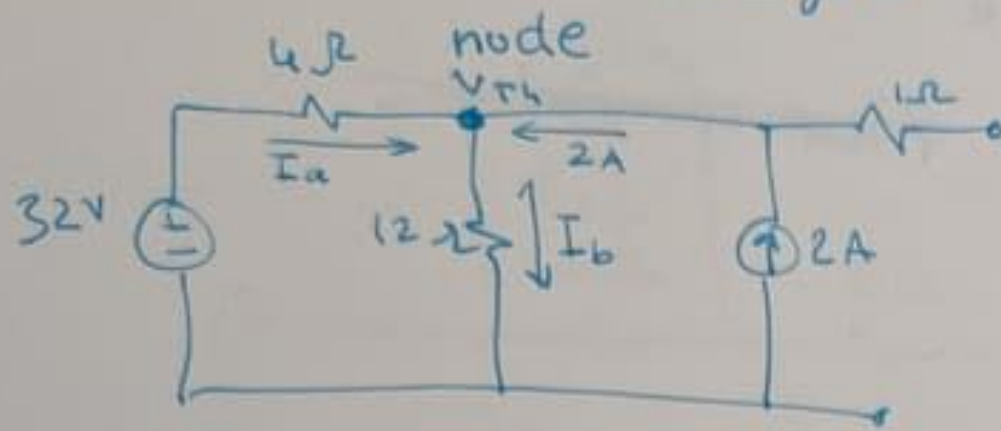

$$I_a + 2 = I_b \Rightarrow \frac{32 - V_{TH}}{4} + 2 = \frac{V_{TH}}{12}$$

\uparrow \uparrow
 $\frac{32 - V_{TH}}{4}$ $\frac{V_{TH}}{12}$

$$\frac{32}{4} - \frac{V_{TH}}{4} + 2 = \frac{V_{TH}}{12}$$

$$\frac{32}{4} + 2 = \frac{V_{TH} \cdot 3}{4 \cdot 3} + \frac{V_{TH}}{12} = \frac{4}{4 \cdot 3} V_{TH}$$

$$\frac{4 \cdot 8}{4} + 2 = \frac{V_{TH}}{3}$$

$$\frac{10}{10} = \frac{V_{TH}}{3}$$

$$\underline{\underline{V_{TH} = 30V}}$$


~~V_{TH} = 30V~~

- Nice! We get the same answer with this method

Now what happens if we load this circuit
with $R_{\text{load}} = 6 \text{ Ohm}$?
or with $R_{\text{load}} = 16 \text{ Ohm}$?

Ex: find out what happens when
 $R_{\text{Load}} = 6$:

Current through R_L is :

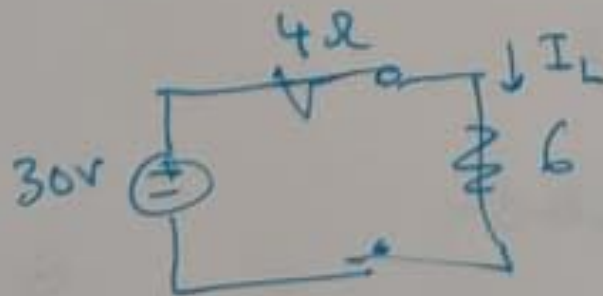


$$I_L = \frac{V_{\text{Th}}}{R_{\text{Th}} + R_L} = \frac{30}{4 + R_L} =$$

$$= \frac{30}{10} = \underline{\underline{3A}}$$

What if load has resistance 16Ω ?


$$I_L = \frac{30}{4 + R_L} = \frac{30}{4 + 16} = \frac{30}{20} = \underline{\underline{1.5A}}$$

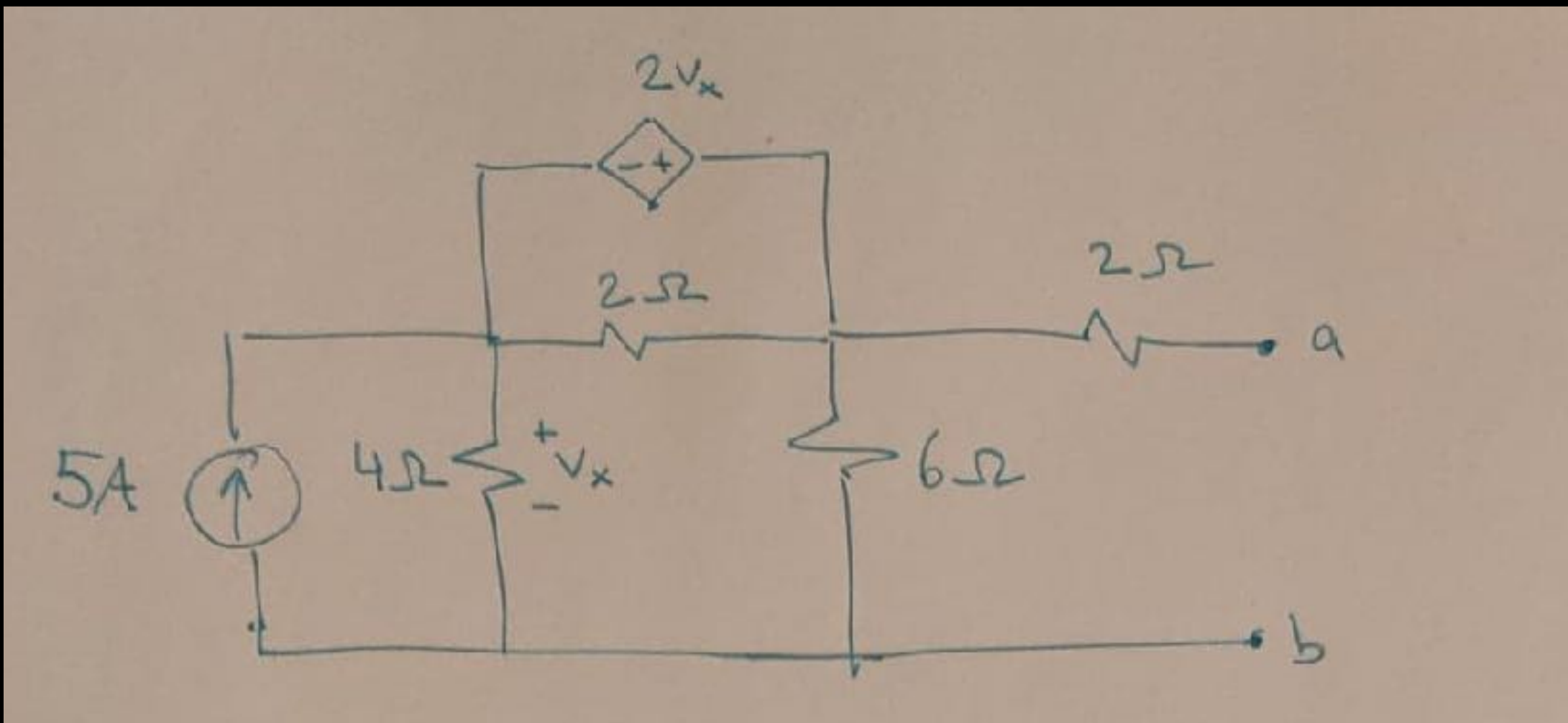Example of finding Thevenin equivalent for circuit with dependent sources




- Turn off all independent sources
- Connect a source V_o to ab terminal
- Find current i_o at terminal to obtain R_{Th} :

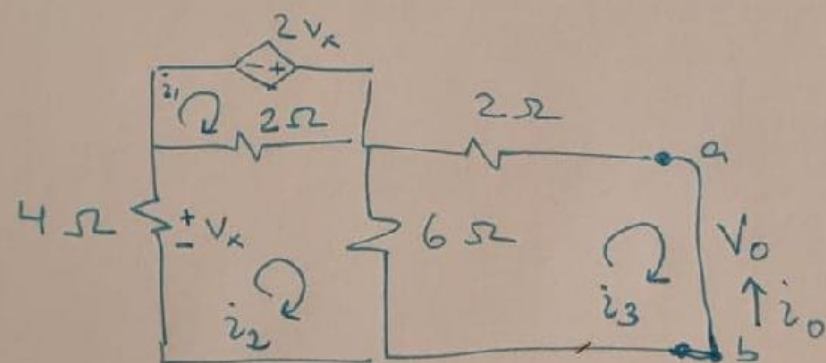5A current source is turned off, acts like an open circuit! \Rightarrow



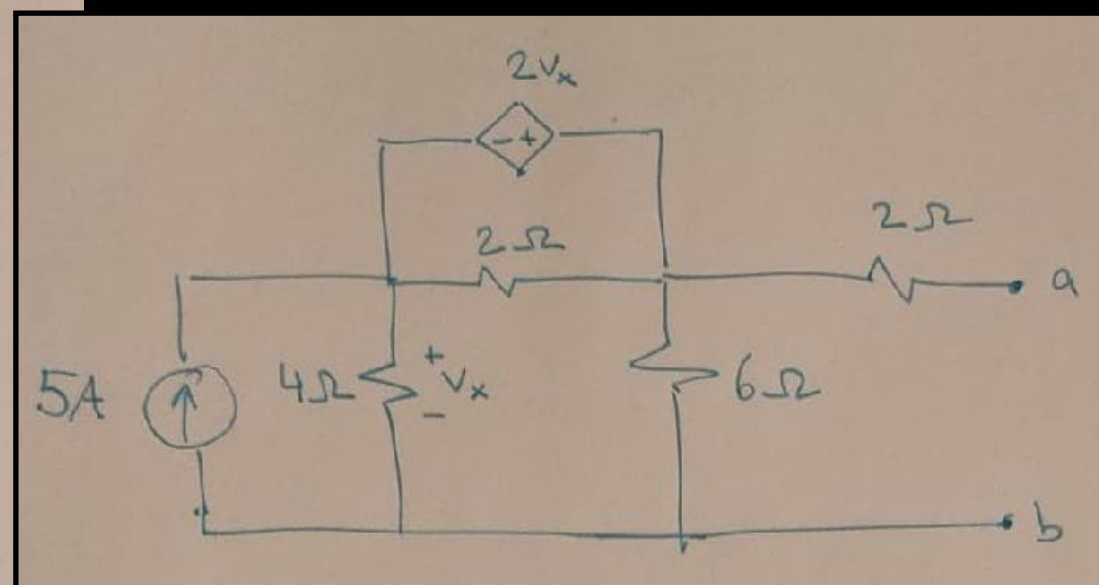Easy way to handle this, set $V_o = 1V$ (cancels out anyway)



For example we can use mesh analysis: KVL:

Loop 1: $-2V_x + 2(i_1 - i_2) = 0 \Rightarrow$

$\Rightarrow V_x = i_1 - i_2$

Voltage drop over 4Ω resistor:

$V_x = 4(-i_2) = -4i_2$

Kirchhoff's Voltage Law

$i_1 - i_2 = -4i_2 \Rightarrow$

$i_1 = -3i_2$

↑ passive sign convention: negative since current flows into negative terminal

Loop 2:

$4i_2 + 2(i_2 - i_1) + 6(i_2 - i_3) = 0$

Loop 3:

$6(i_3 - i_2) + 2i_3 + 1 = 0$

For example we can use mesh analysis. KVL:

Loop 1:

$$-2V_x + 2(i_1 - i_2) = 0 \Rightarrow$$

$$\Rightarrow V_x = i_1 - i_2$$

Voltage drop over 4Ω resistor:

$$V_x = 4(-i_2) = -4i_2$$

Kirchhoffs
Voltage
Law

$$i_1 - i_2 = -4i_2 \Rightarrow$$

$$i_1 = -3i_2$$

↑ passive sign convention:
negative since current flows i- to
negative terminal

Loop 2:

$$4i_2 + 2(i_2 - i_1) + 6(i_2 - i_3) = 0$$

Loop 3:

$$6(i_3 - i_2) + 2i_3 + 1 = 0$$

Eg 1:

$$4i_2 + 2i_2 - 2i_1 + 6i_2 - 6i_3 = 0$$

$$= i_2(4+2+6) - 2i_1 - 6i_3 =$$

$$= -2i_1 + 12i_2 - 6i_3 = 0$$

$$\text{we have that } i_1 = -3i_2 \Rightarrow$$

$$-2(-3i_2) + 12i_2 - 6i_3 =$$

$$\Rightarrow 18i_2 = 6i_3 \Rightarrow 3i_2 = i_3$$

Eg 2:

$$6i_3 - 6i_2 + 2i_3 + 1 = 0$$

$$8i_3 - 6i_2 = -1$$


$$\text{from (1) we have } i_2 = \frac{i_3}{3}$$

$$\Rightarrow 8i_3 - 6\left(\frac{i_3}{3}\right) = -1$$

$$6i_3 = -1 \Rightarrow i_3 = -\frac{1}{6} \text{ [A]}$$

$$\text{we see that: } i_0 = -i_3 = \frac{1}{6} \text{ [A]} \Rightarrow R_{Th} = \frac{1V}{i_0} = 6\Omega$$

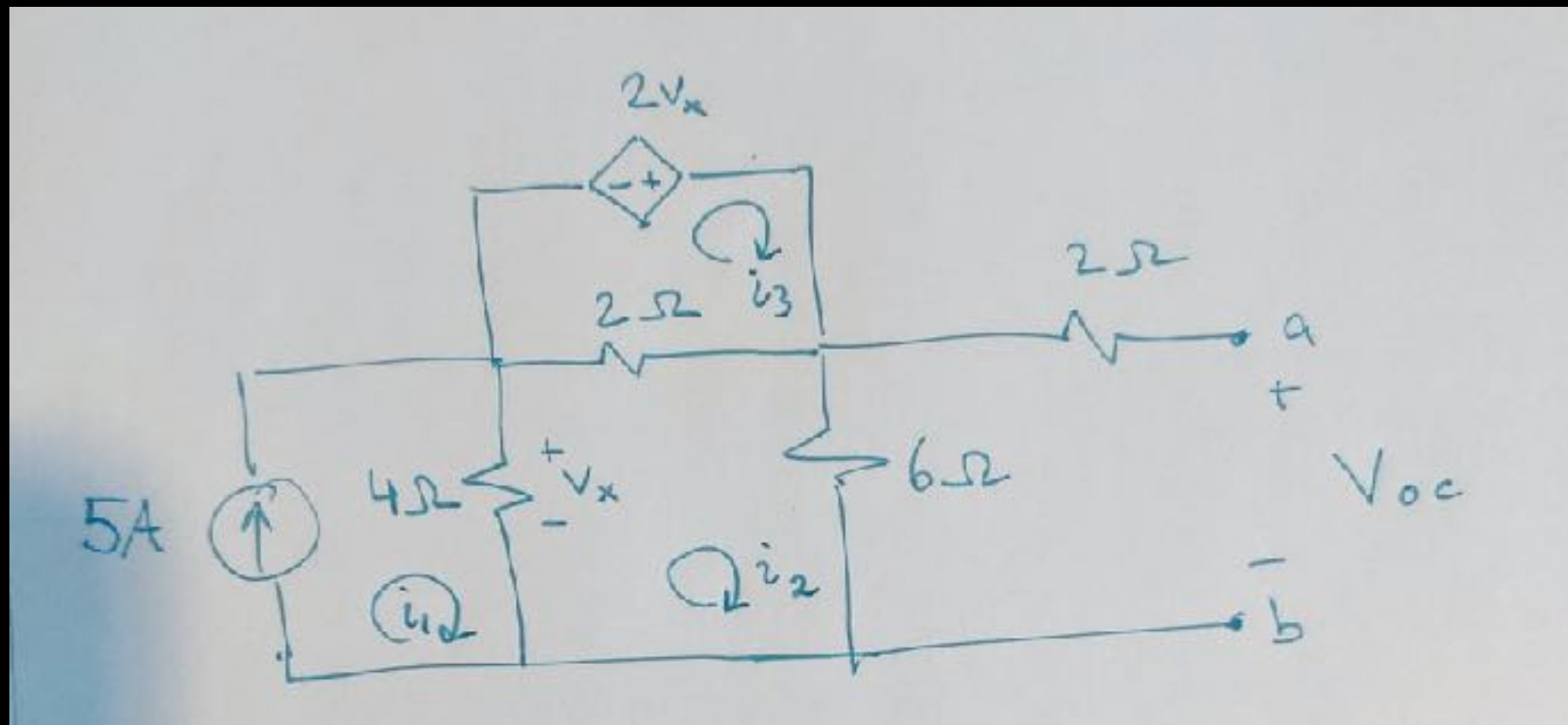- We have found R_{Th} , now we need to find V_{Th} which is the open circuit voltage V_{oc} at the a b terminal
- We can for example do this using mesh analysis. Set up KVL at the loops 1, 2 and 3:



We see that $4(i_1 - i_2) = V_x$

Loop 1 : $i_1 = 5$


Loop 3 : $-2V_x + 2(i_3 - i_2) = 0 \Rightarrow$
 $\Rightarrow V_x = i_3 - i_2 \dots (1)$

Loop 2 : $4(i_2 - i_1) + 2(i_2 - i_3) + 6i_2 = 0$

Solve for $i_2 = \frac{10}{3} \text{ [A]}$

$\Rightarrow V_{Th} = V_{oc} = 6i_2 = 20\text{V}$

Ans:

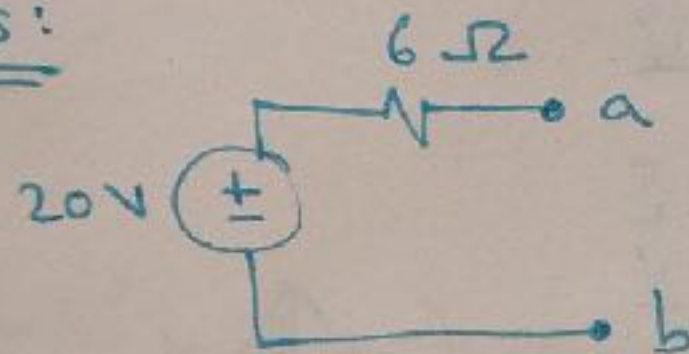


Maximum Power Transfer

- In many applications, a circuit is designed to power a load
- Among those applications there are many cases where we **wish to maximize the power transferred to the load**
- Unlike an ideal source, internal resistance will restrict the conditions where maximum power is transferred.

Finding Maximum Power Transfer using Thevenin equivalent


- We can use the Thevenin equivalent circuit for finding the maximum power in a linear circuit
- We will assume that the load resistance can be varied
- Looking at the equivalent circuit with load included, the power transferred is:
($P = IV = I^2V$)
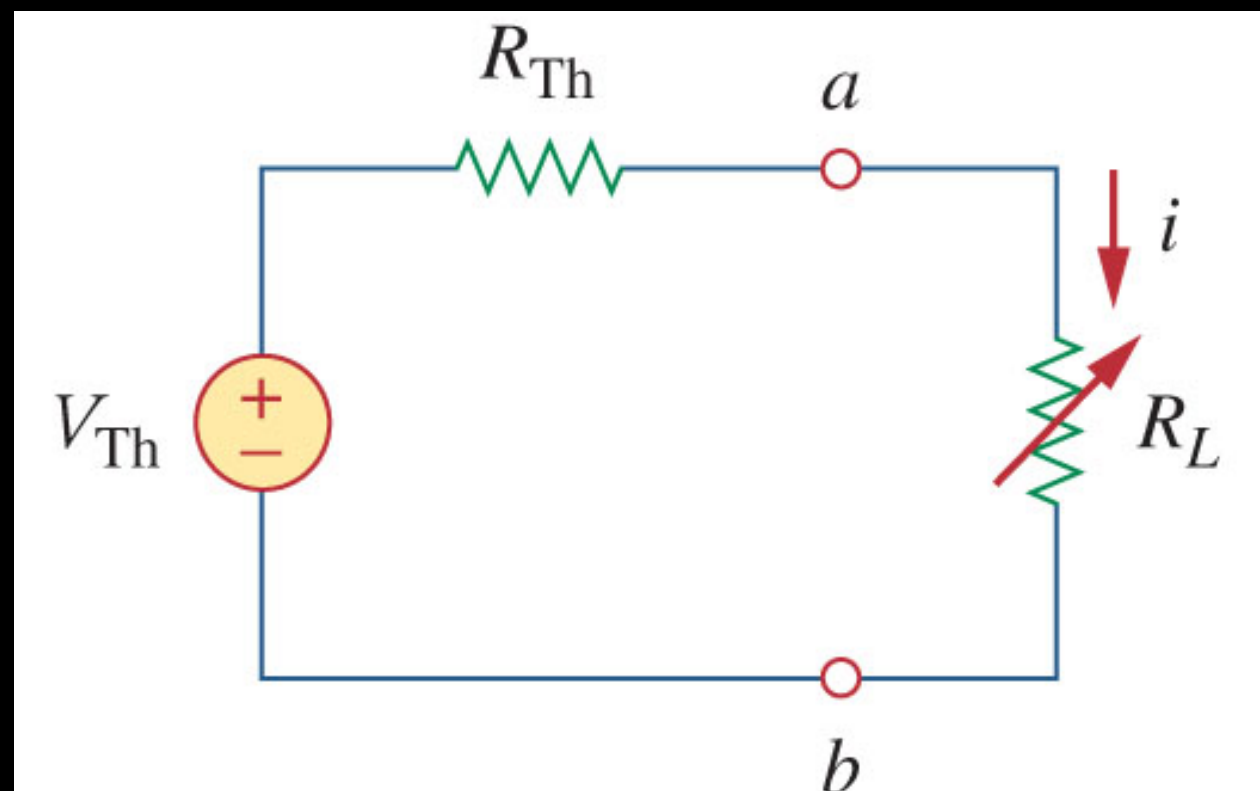
$$p = \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$




Maximum Power Transfer

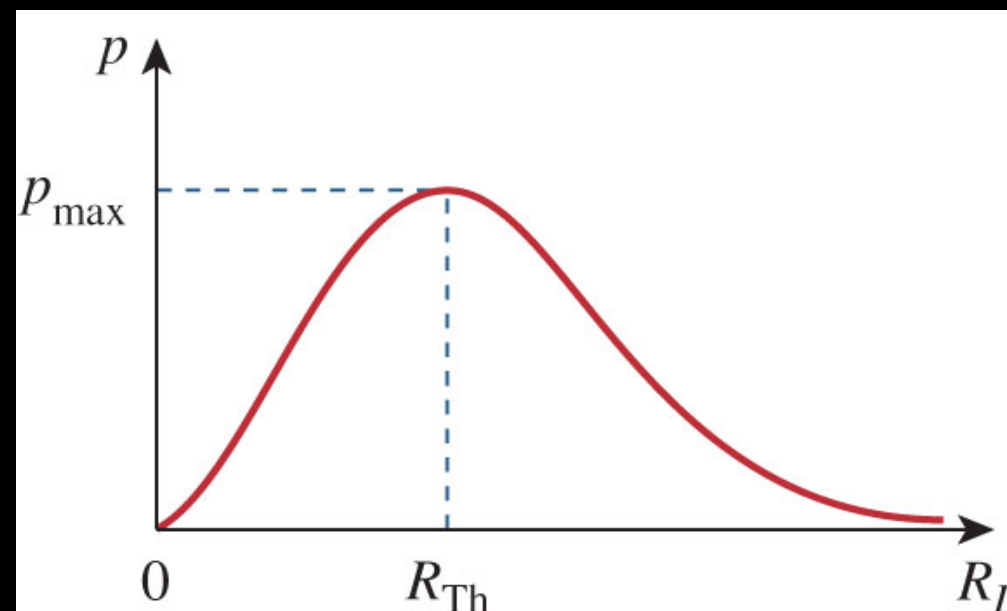- For a given circuit, V_{Th} and R_{Th} are fixed. By varying the load resistance R_L , the power delivered to the load varies as shown
- As R_L approaches 0 and ∞ the power transferred goes to zero.
- Maximum power is transferred when $R_L = R_{Th}$




Example

Max Power Transfer:

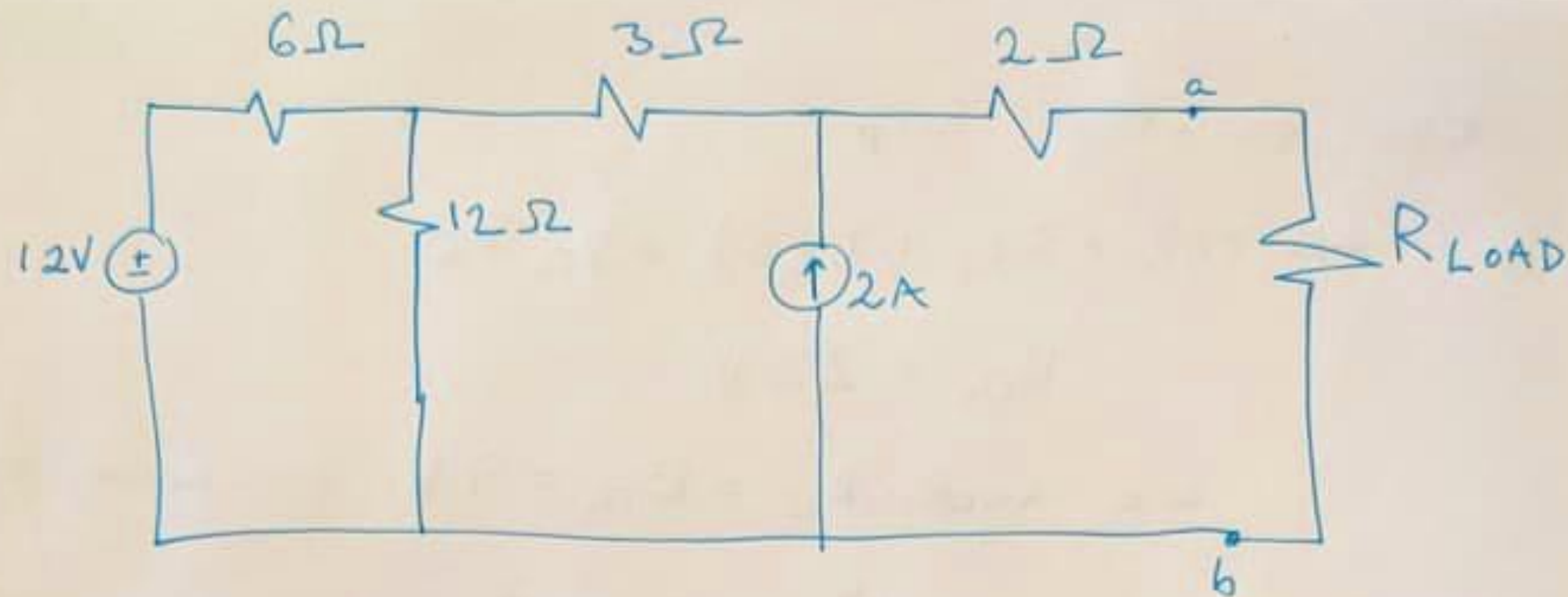


FIND R_L FOR MAX POWER TRANSFER

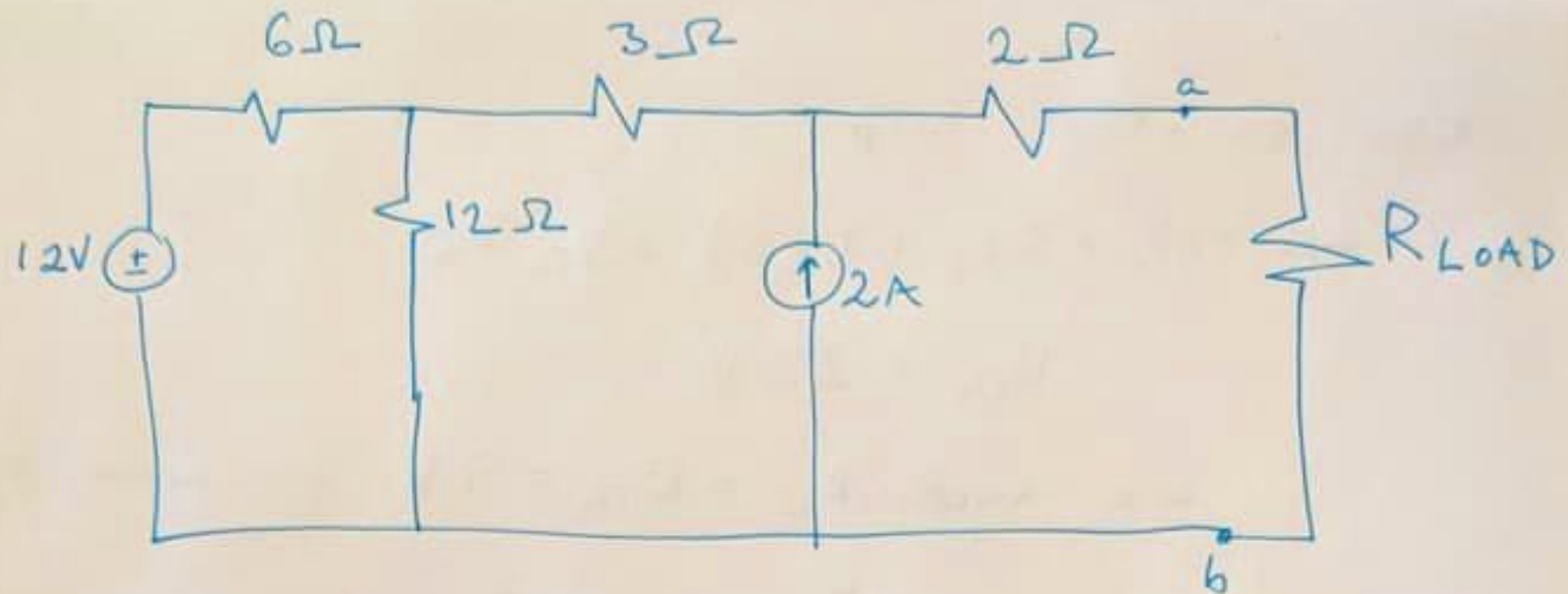


FIND R_L FOR MAX POWER TRANSFER

- Find R_{Th} : Turn off all the sources

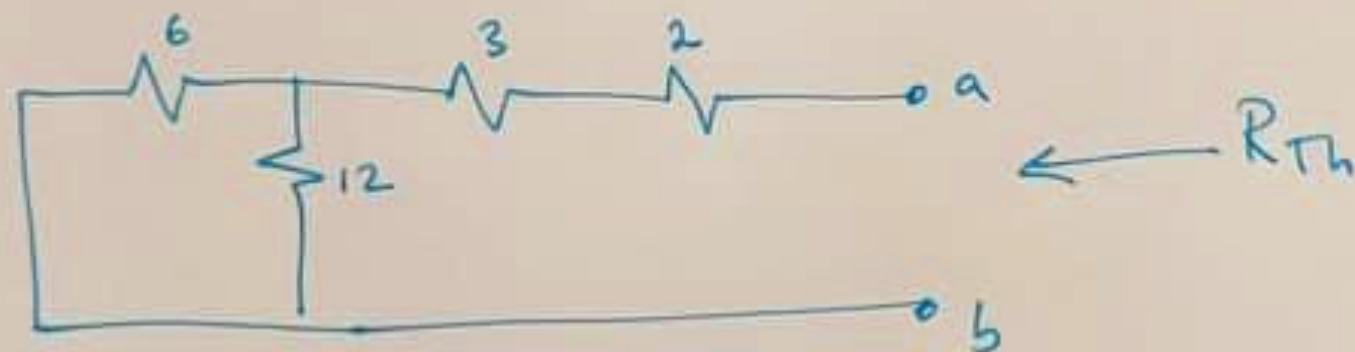(Remember: voltage source gets shorted
current source: open circuit)



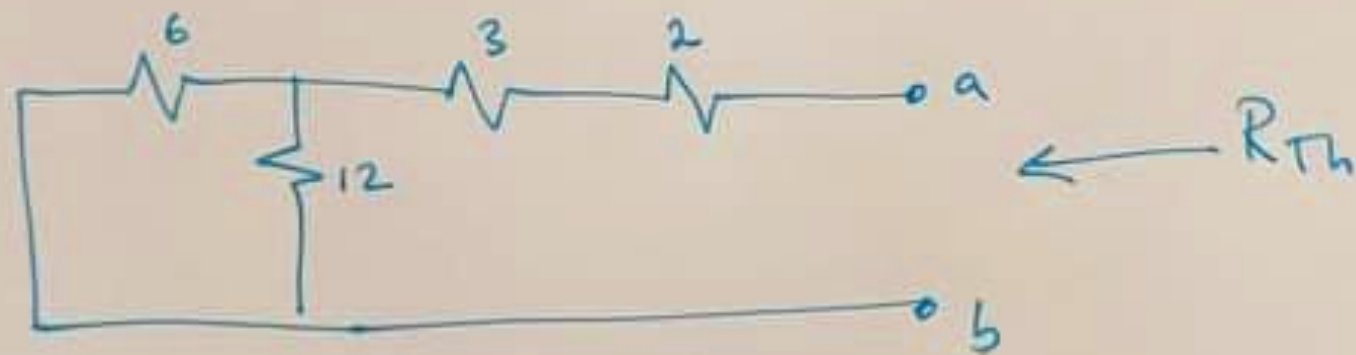


Resistors in series & parallel:

$$6 \parallel 12 + 3 + 2 = \frac{6 \cdot 12}{6 + 12} + 5 = \underline{\underline{9 \, [\Omega]}}$$

$$\frac{6 \cdot 12}{18} = 4$$

$\nearrow 3 \cdot 6$

Now find V_{Th} : Open circuit ~~is~~

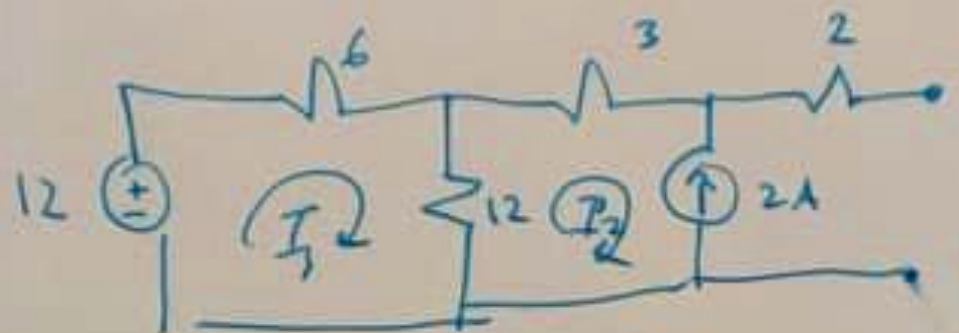

$$12i_1 = 6i_1 + 12(i_1 - i_2) \quad \text{and} \quad i_2 = 2A$$

$$\Rightarrow i_1 = -\frac{2}{3} [A]$$

KVL on other loop:

$$-12 + 6i_1 + 3i_2 + 2(0) + V_{Th} = 0$$


$$V_{Th} = 22V$$


we have $R_L = R_{Th} = 9\Omega$ for max power

$$P_{max} = \frac{V_{Th}^2}{4R_L} = \frac{22^2}{4 \times 9} = 13.44 [W]$$

Wheatstone bridge


for measuring resistance very accurately

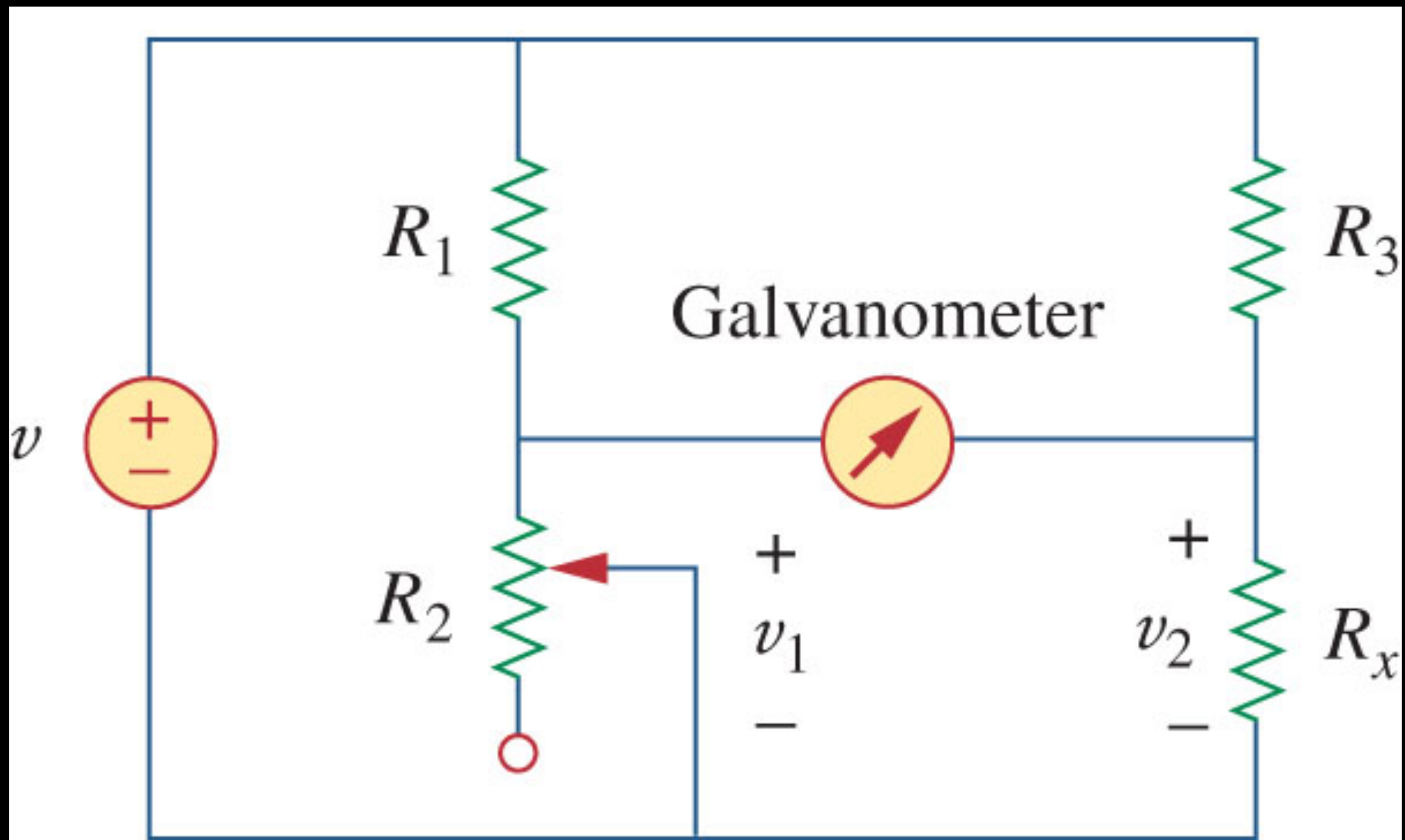

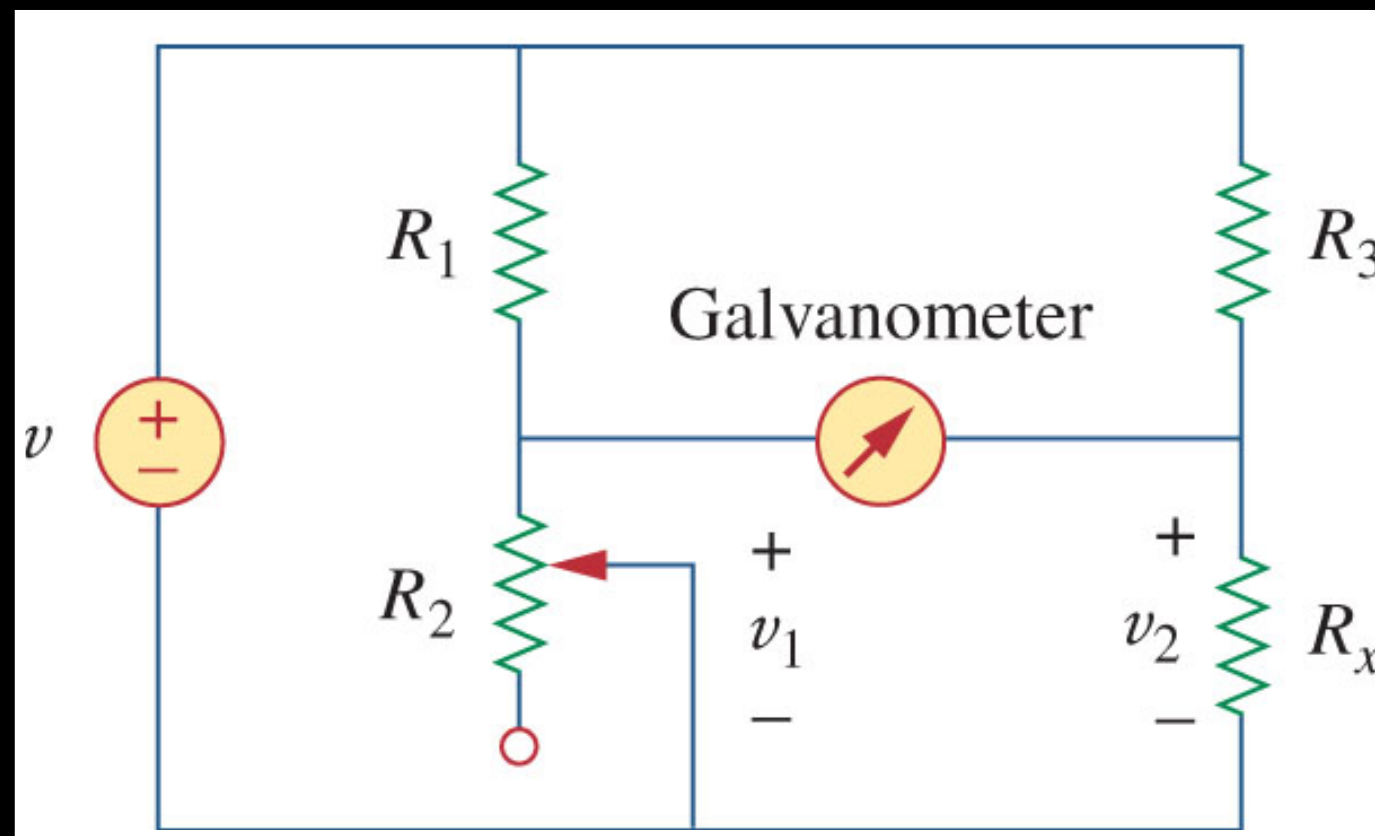

$$R_x = \frac{R_3}{R_1} R_2$$

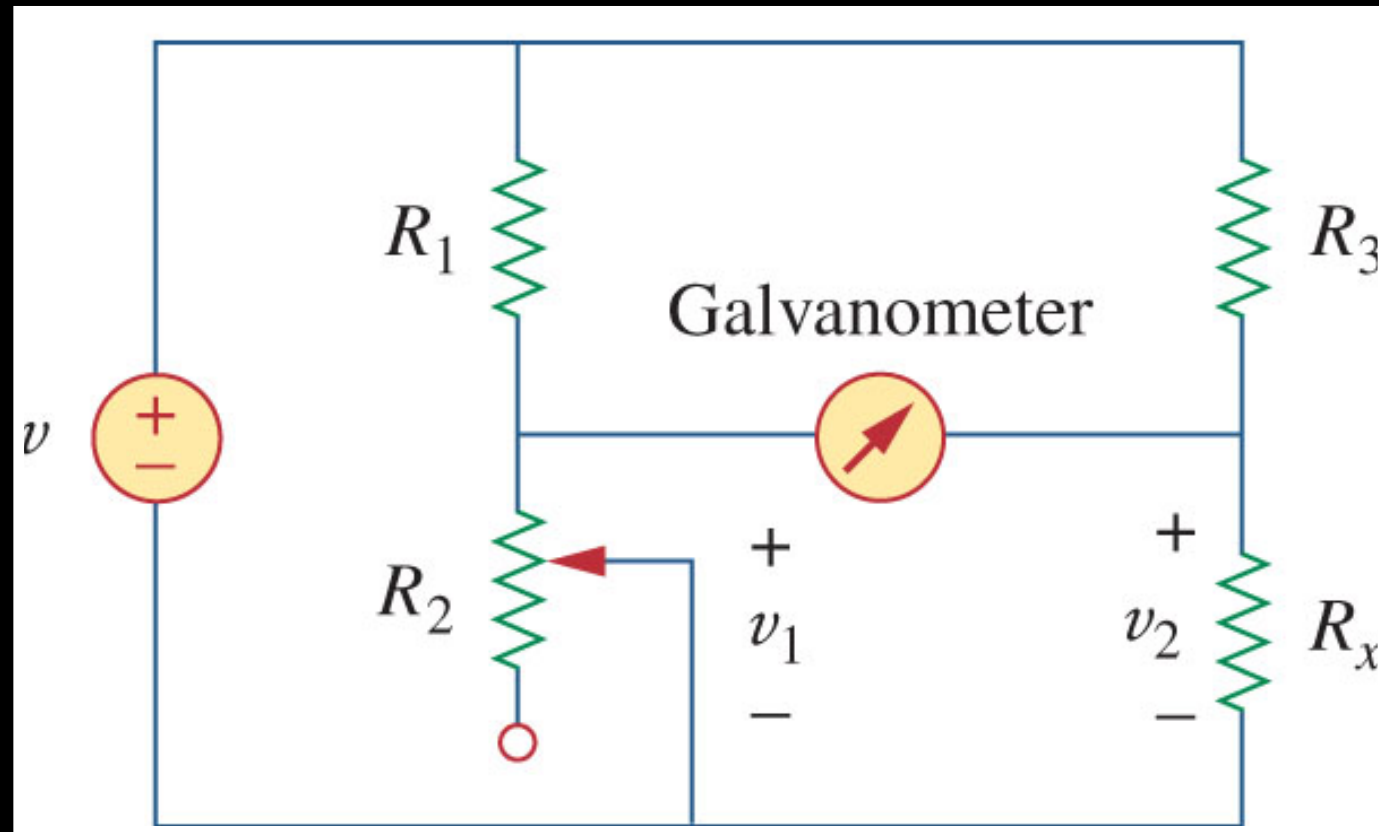- Based on the principle of the voltage divider
- Using three known resistors and a galvanometer, an unknown resistor R_x can be tested
- The variable resistor R_2 is adjusted until the galvanometer shows zero current
- At this point, the bridge is “balanced” and the voltages from the two dividers are equal




Current through galvo under unbalanced condition:

$$I = \frac{V_{Th}}{R_{Th} + R_m}$$

Simple Example

Wheatstone bridge

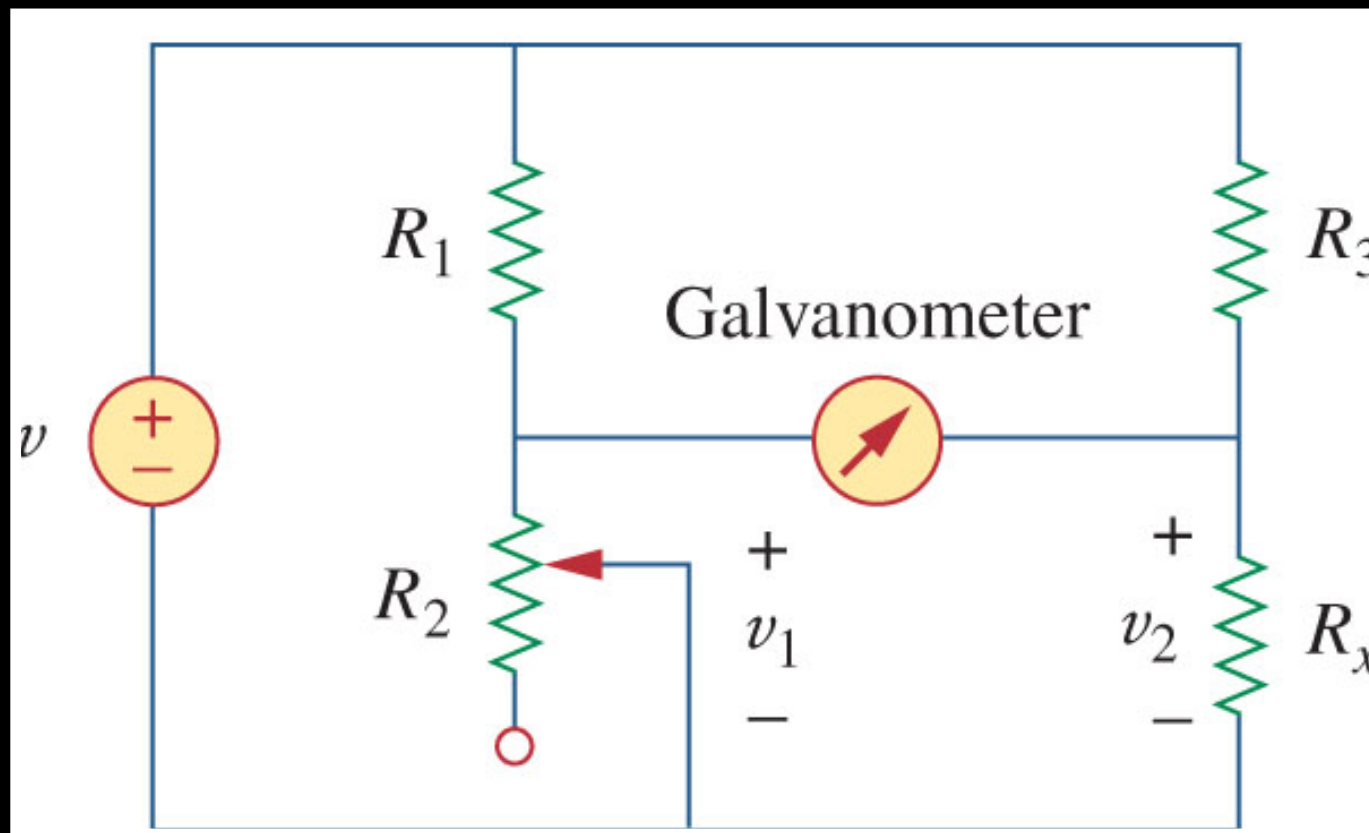
- $R_1 = 500\ \Omega$ and $R_3 = 200\ \Omega$ and the bridge is balanced when R_2 is adjusted to be $125\ \Omega$. Find R_x



Simple Example

Wheatstone bridge

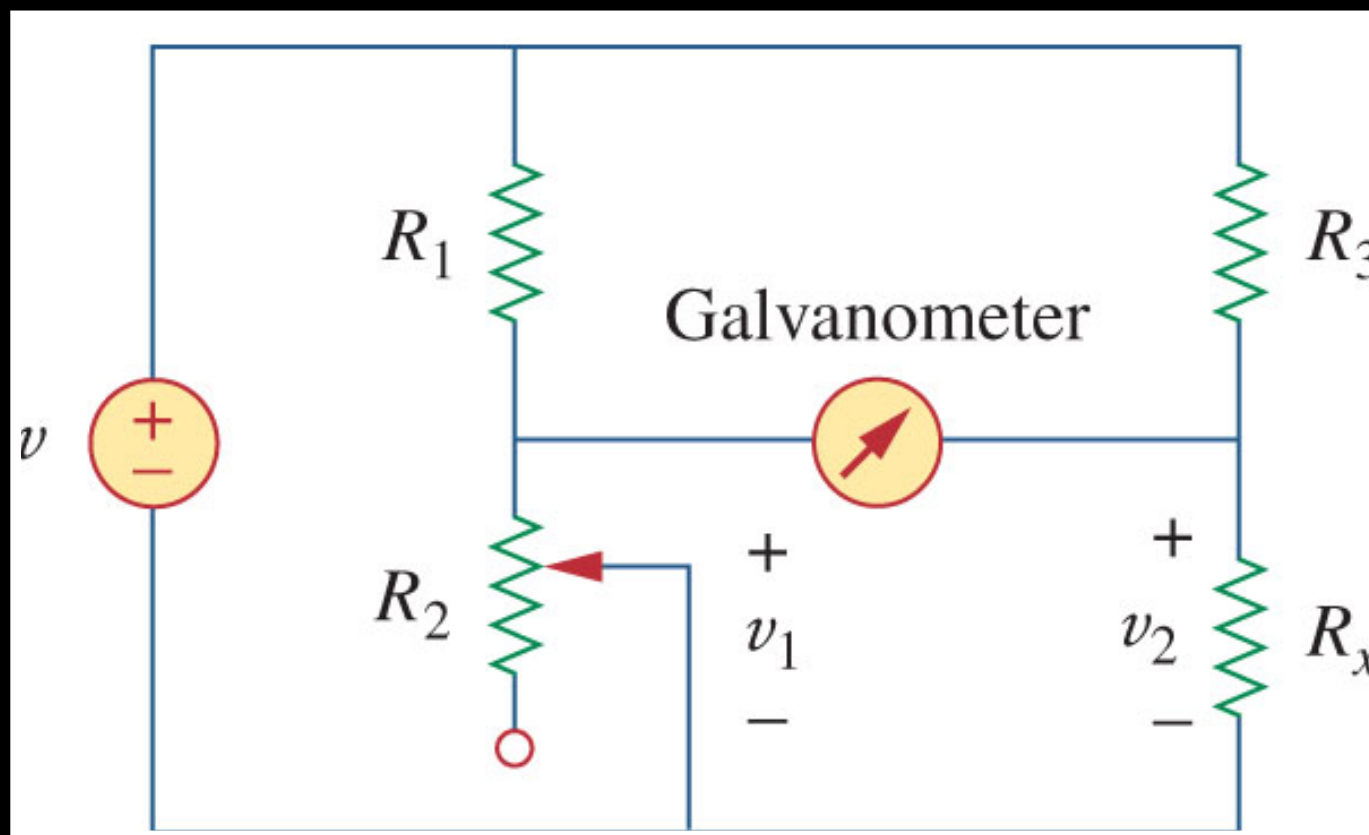- $R_1 = 500 \text{ Ohm}$ and $R_3 = 200 \text{ Ohm}$ and the bridge is balanced when R_2 is adjusted to be 125 Ohm . Find R_x



$$R_x = \frac{R_3}{R_1} R_2$$

$$R_x = (200/500) \times 125 = 50 \text{ [Ohm]}$$

Super Simple Example

Wheatstone bridge

- A Wheatstone bridge that $R_1 = R_2 = 2 \text{ k}\Omega$. R_2 is adjusted until no current flows through the galvanometer. At this point, $R_2 = 6.3 \text{ k}\Omega$.

What is the value of the unknown resistance?

Super Simple Example

Wheatstone bridge

- A Wheatstone bridge that $R_1 = R_2 = 2 \text{ k}\Omega$. R_2 is adjusted until no current flows through the galvanometer. At this point, $R_2 = 6.3 \text{ k}\Omega$.

What is the value of the unknown resistance?


Answer: $R_x = 6.3 \text{ k}\Omega$

Example 3

Wheatstone bridge

- Find the current through the galvanometer G:

Example of a Wheatstone bridge:

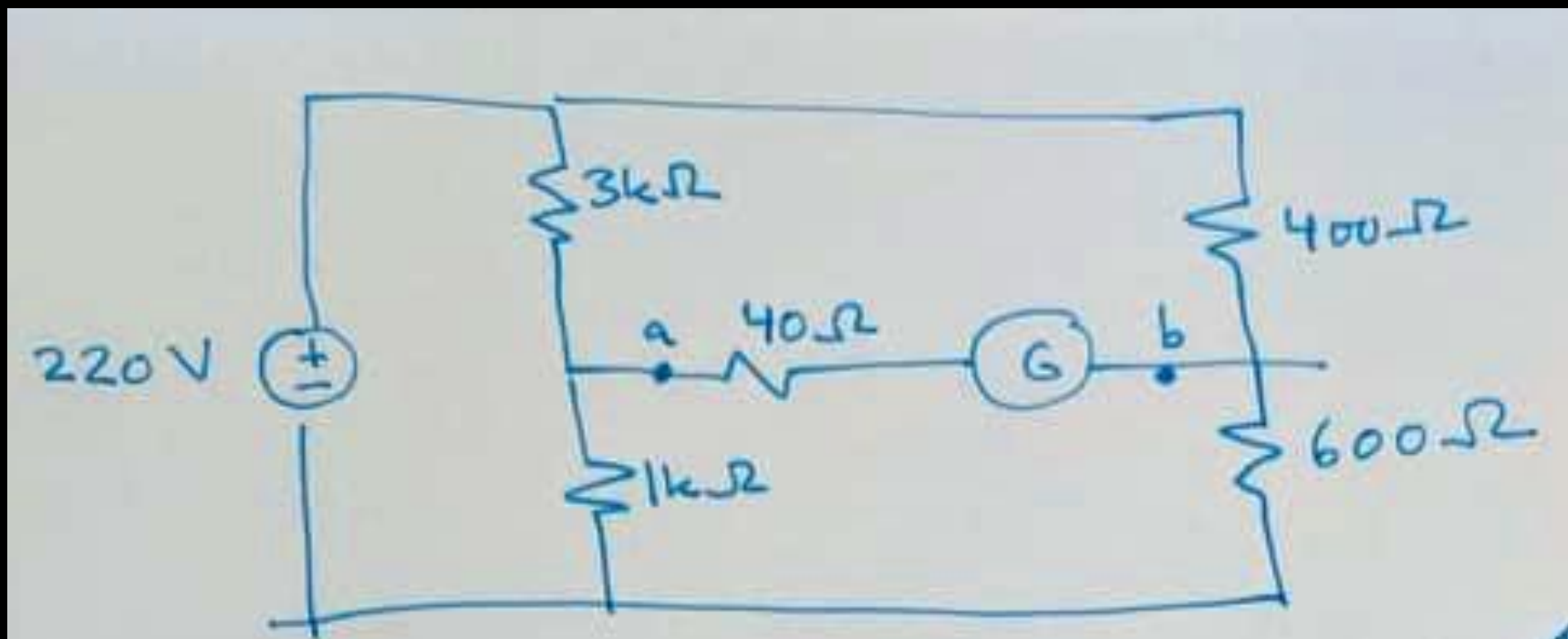


Often drawn like this instead:




Finding R_{Th}

Our bridge:

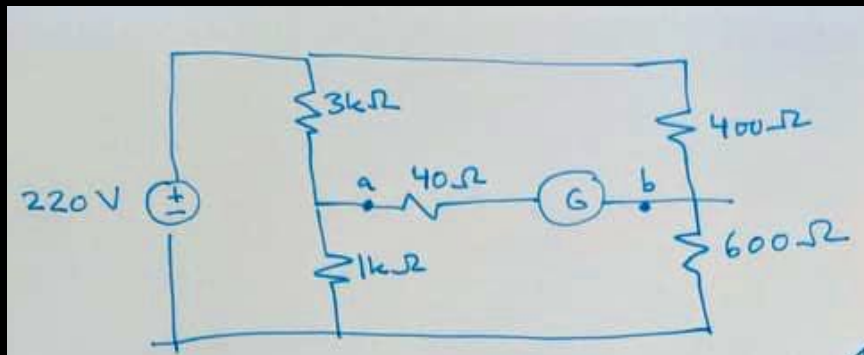


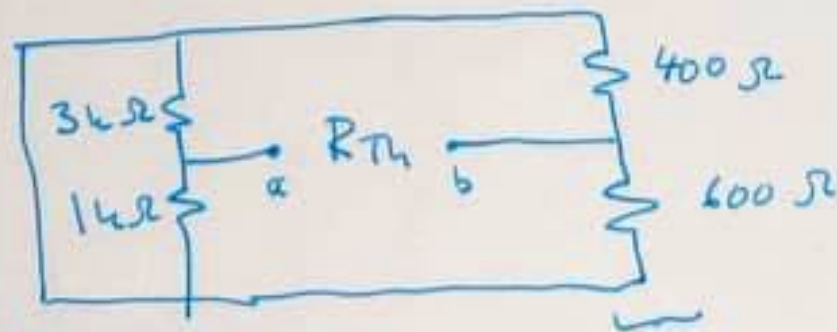- Thevenin Resistance: Shut off all the sources:




Finding R_{Th}

Our bridge:

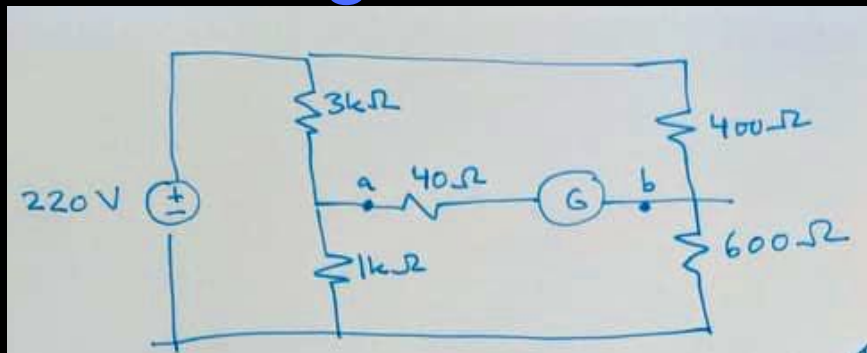

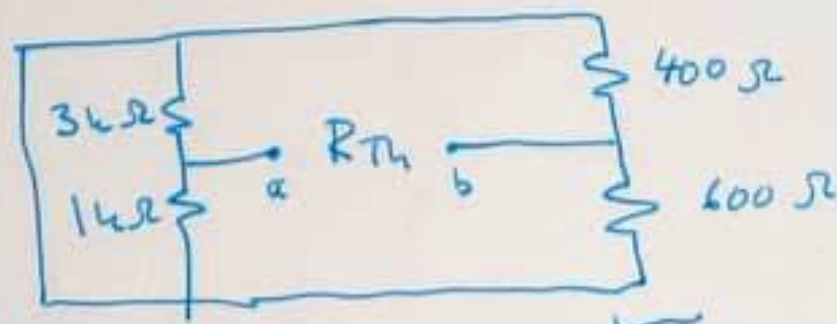- Thevenin Resistance: Shut off all the sources:




in parallel : in parallel


$$\Rightarrow R_{Th} = 3000 \parallel 1000 + 400 \parallel 600 = \frac{3000 \times 1000}{3000 + 1000} + \frac{400 \times 600}{400 + 600} =$$
$$= 750 + 240 = \underline{\underline{990 [\Omega]}}$$


Finding V_{Th}

Our bridge:

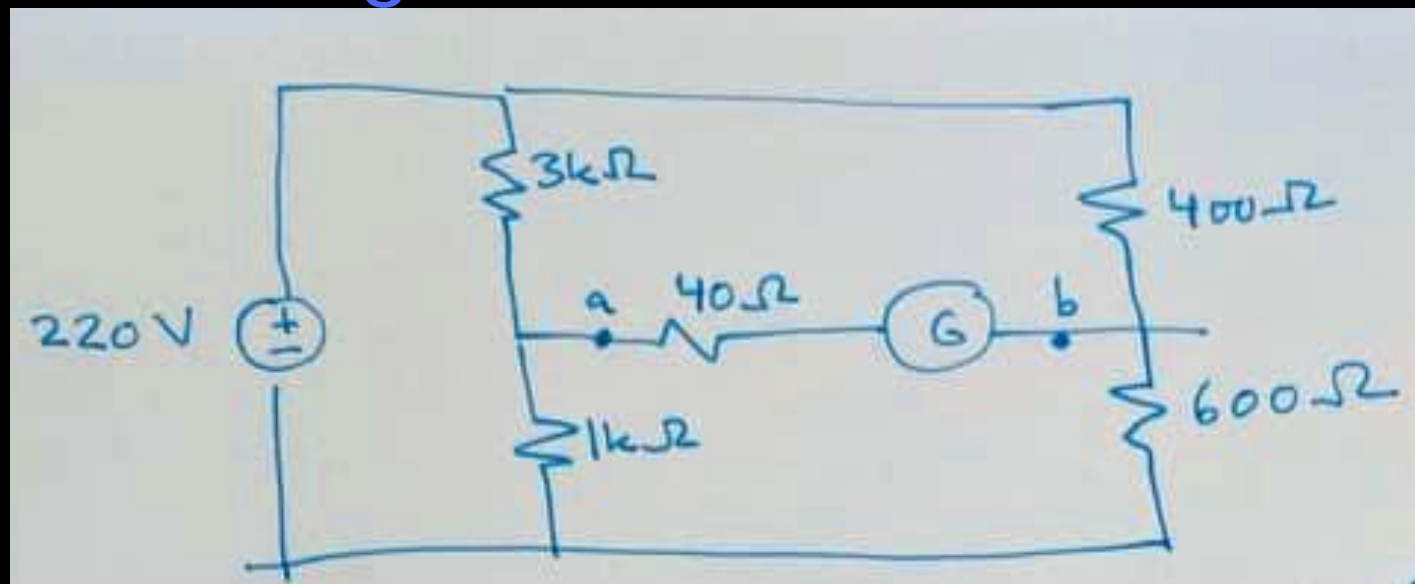

Finding V_{Th} : open the terminal :

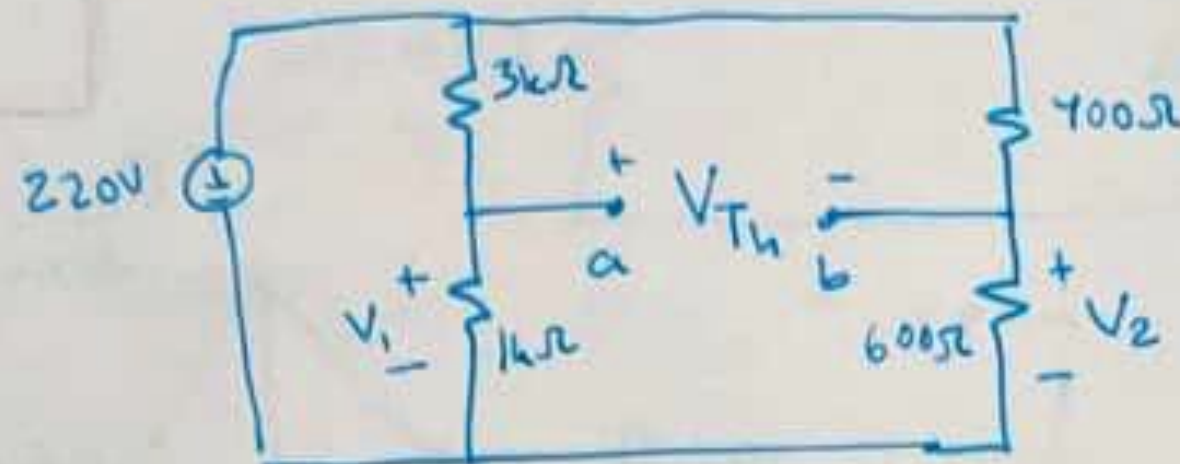


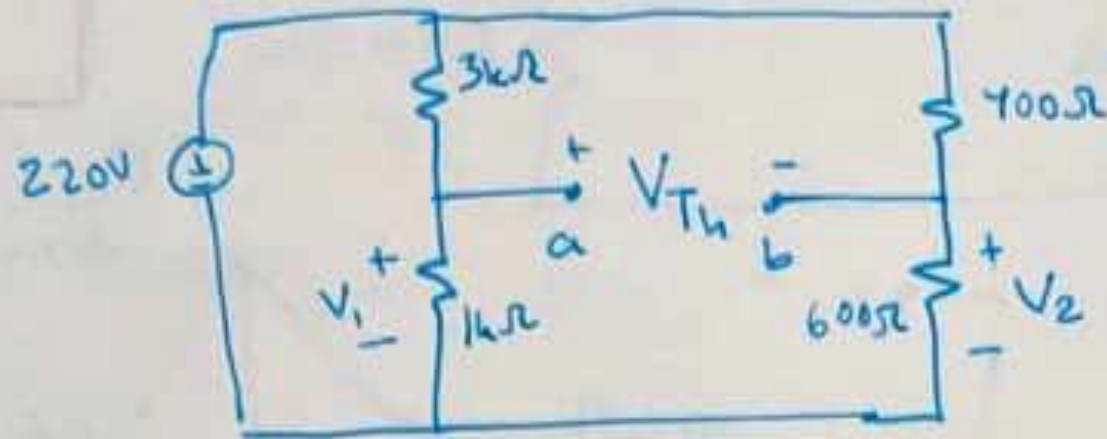

Voltage division :

$$V_1 = \frac{1000}{1000 + 3000} (220) = 55V$$
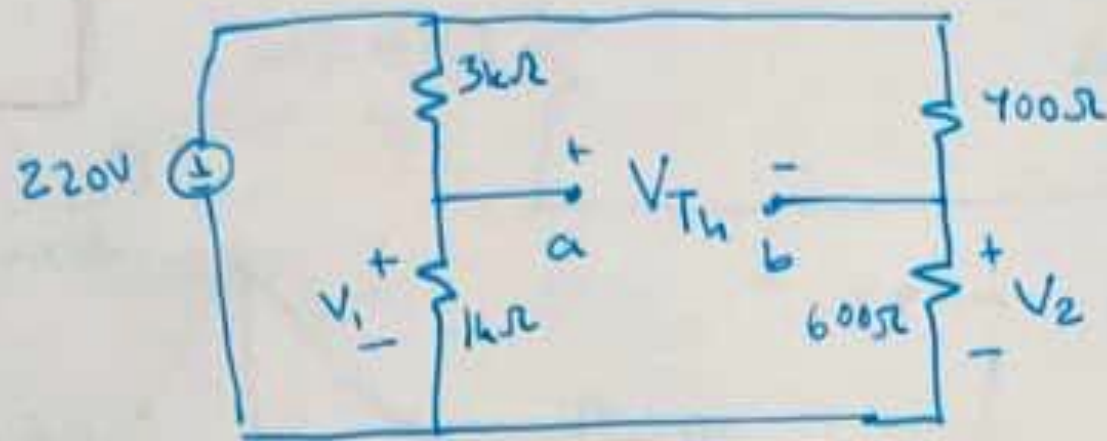
$$V_2 = \frac{600}{600 + 400} (220) = 132V$$



Voltage division :

$$V_1 = \frac{1000}{1000 + 3000} (220) = 55V$$

$$V_2 = \frac{600}{600 + 400} (220) = 132V$$


KVL around loop ab :

$$-V_1 + V_{Th} + V_2 = 0 \Rightarrow V_{Th} = V_1 - V_2 = 55 - 132 = -77V$$

- Now we have found $R_{Th} = 990 \text{ Ohm}$ and $V_{Th} = -77 \text{ V}$

Find current through the galvo:


Draw Thevenin equiv. circuit:

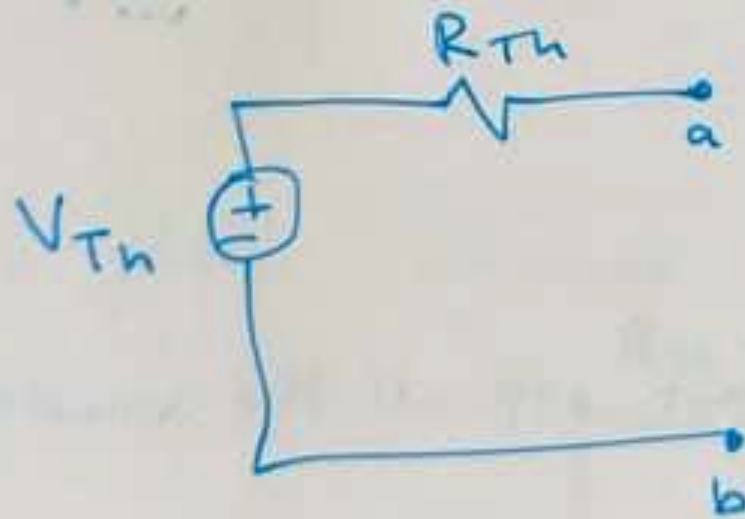


- Now we have found $R_{Th} = 990 \text{ Ohm}$ and $V_{Th} = -77 \text{ V}$

Find current through the galvo:

Draw Thevenin equiv. circuit:

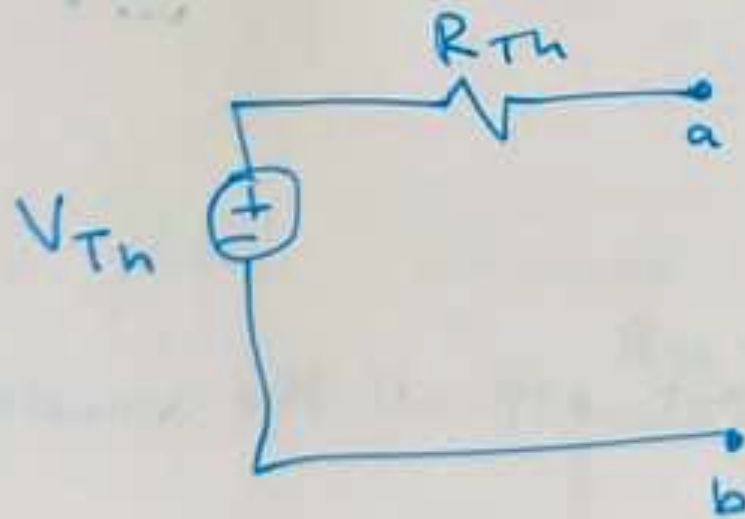

we put on our "load"

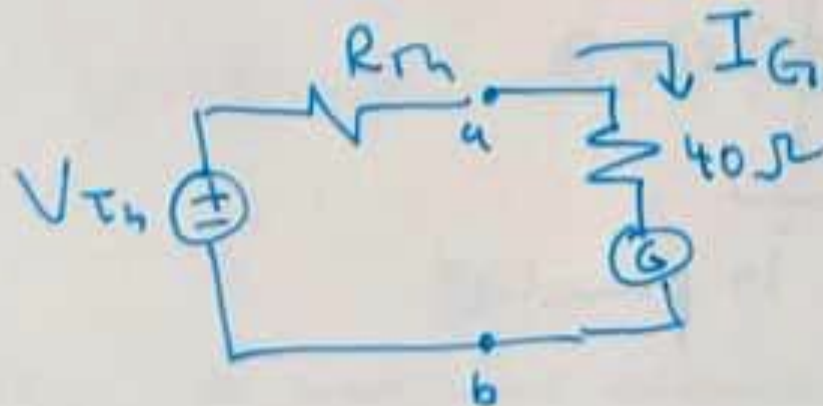


$$I_G = \frac{V_{Th}}{R_{Th} + R_{galvo}} = \frac{-77}{990 + 40} =$$

$$= -74.6 \text{ [mA]}$$


\Rightarrow current flows from b to a

Summary:

Our Wheatstone bridge:

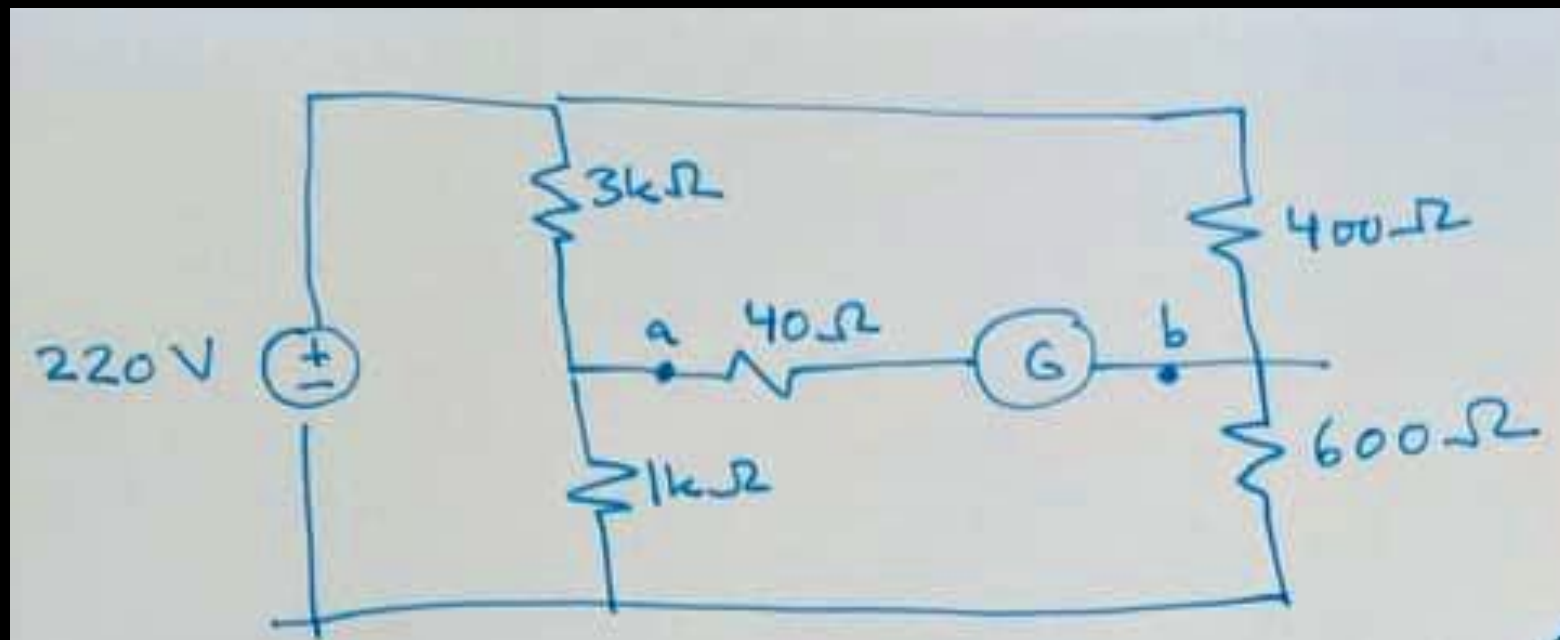


Thevenin equivalent:

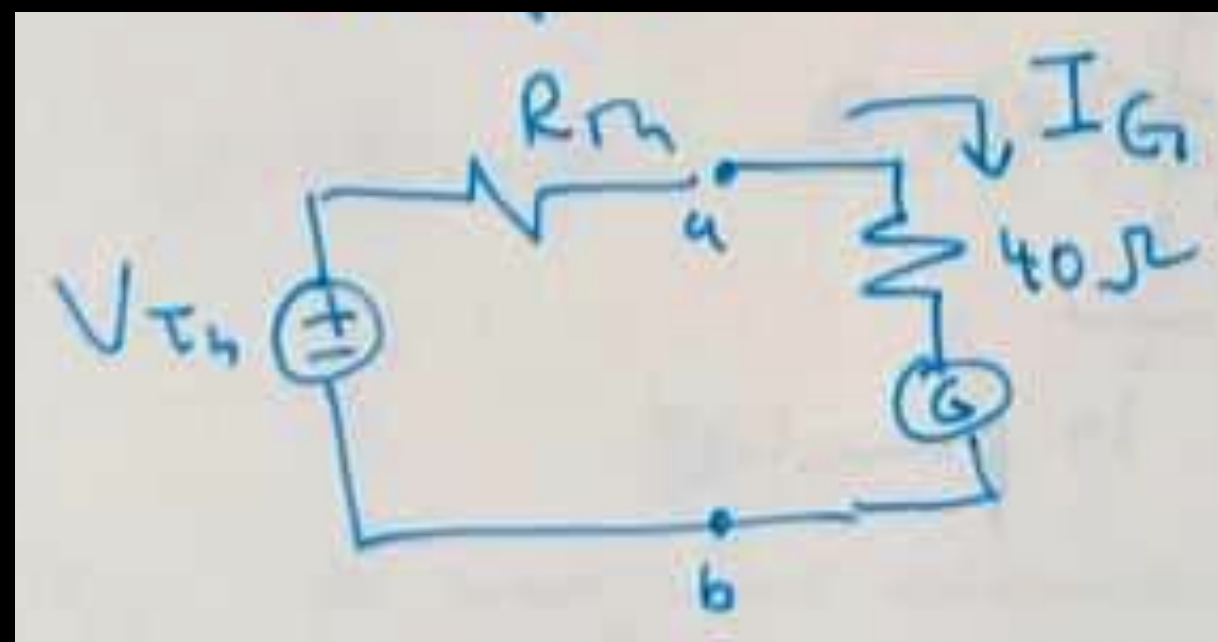

Now: Remember Source Transformation

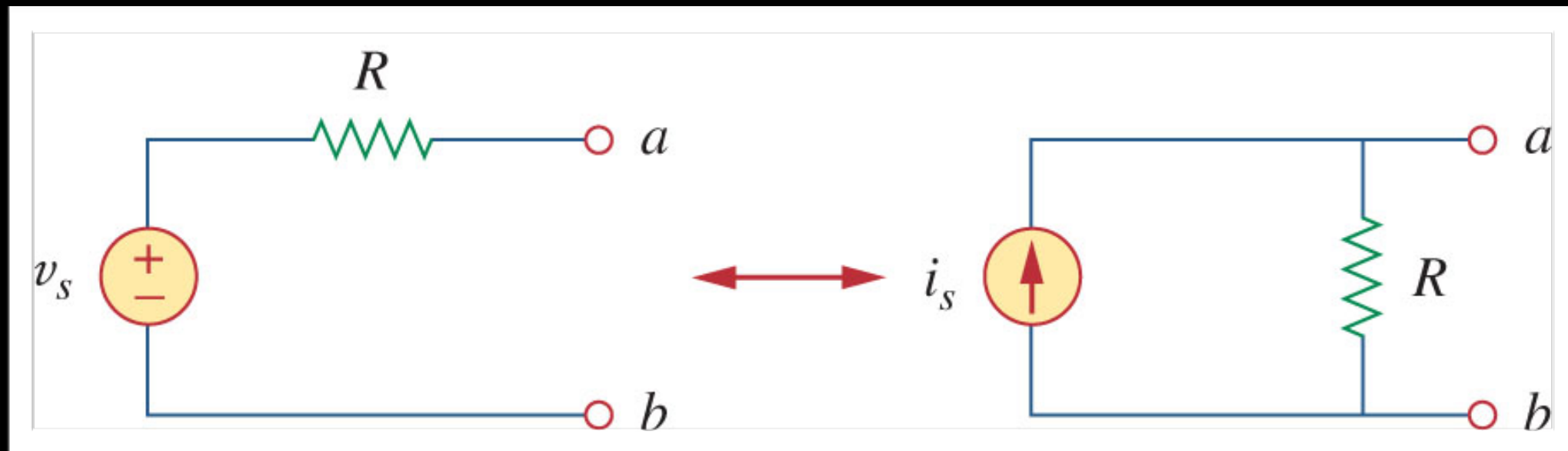We can replace a voltage source in series with a resistor by a current source in parallel with a resistor (and *vice versa*).



These sources have equivalent behavior at their terminals. If the sources are turned off the resistance at the terminals are both R . If the terminals are short circuited, the currents need to be the same, so that:

$$v_s = i_s R \quad \text{or} \quad i_s = \frac{v_s}{R}$$

Thevenin and Norton equivalent circuits


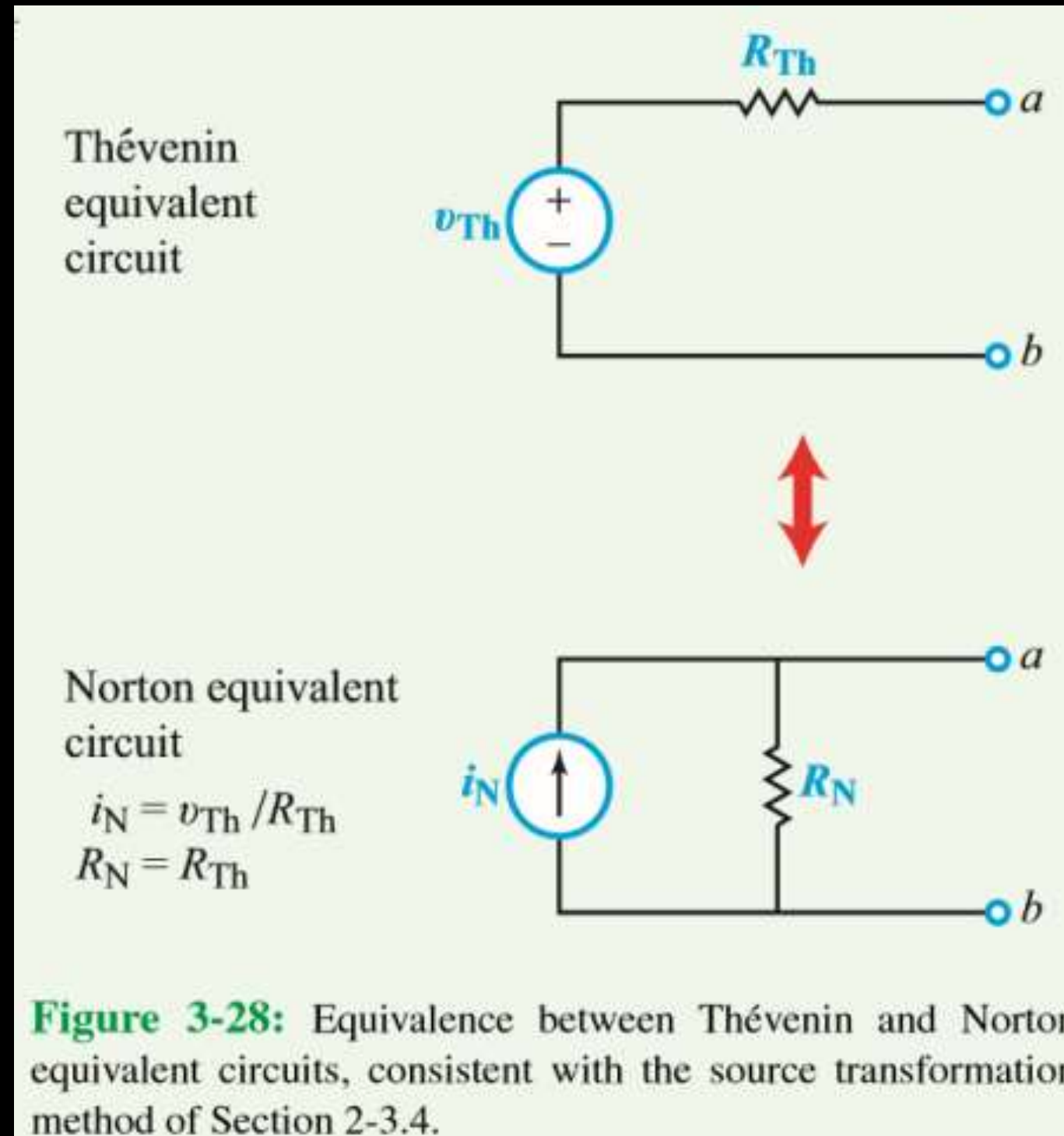


Figure 3-28: Equivalence between Thévenin and Norton equivalent circuits, consistent with the source transformation method of Section 2-3.4.

Norton's Theorem


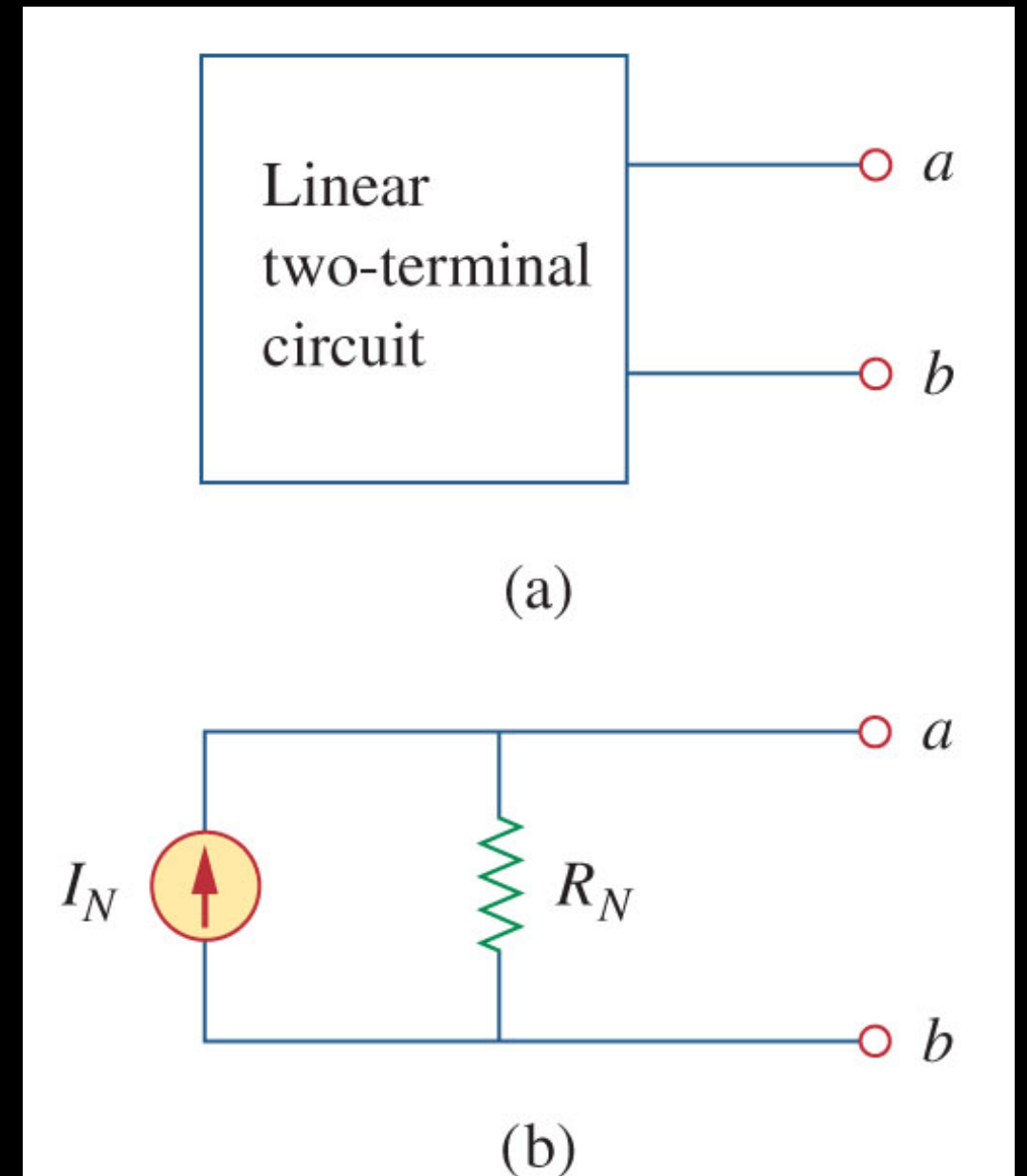
- Similar to Thevenin's theorem, Norton's theorem states that a linear two terminal circuit may be replaced with an equivalent circuit containing a **resistor** and a **current source**
- Norton resistance is the same as Thevenin resistance




Norton Current I_N

- The Norton current I_N is found by short circuiting the circuit's terminals and measuring the resulting current:


$$I_N = i_{sc}$$

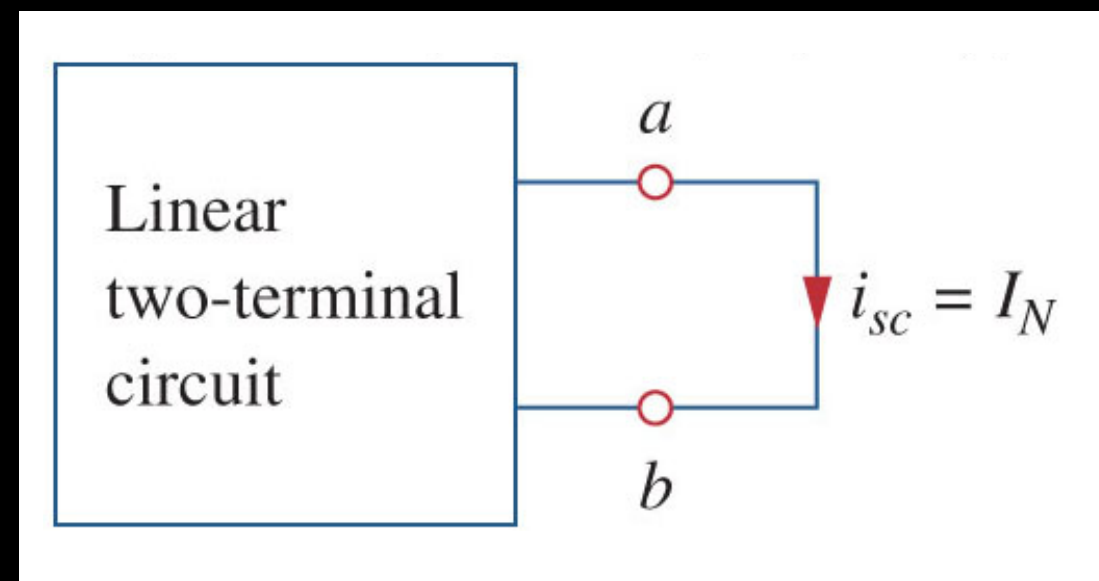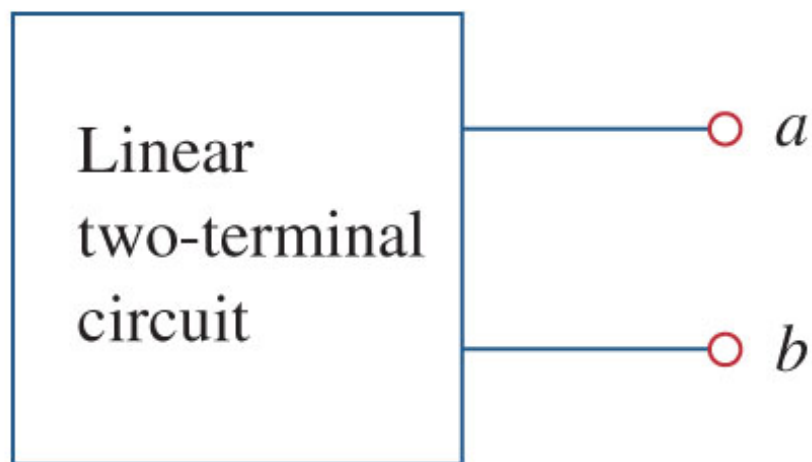

Example: Norton

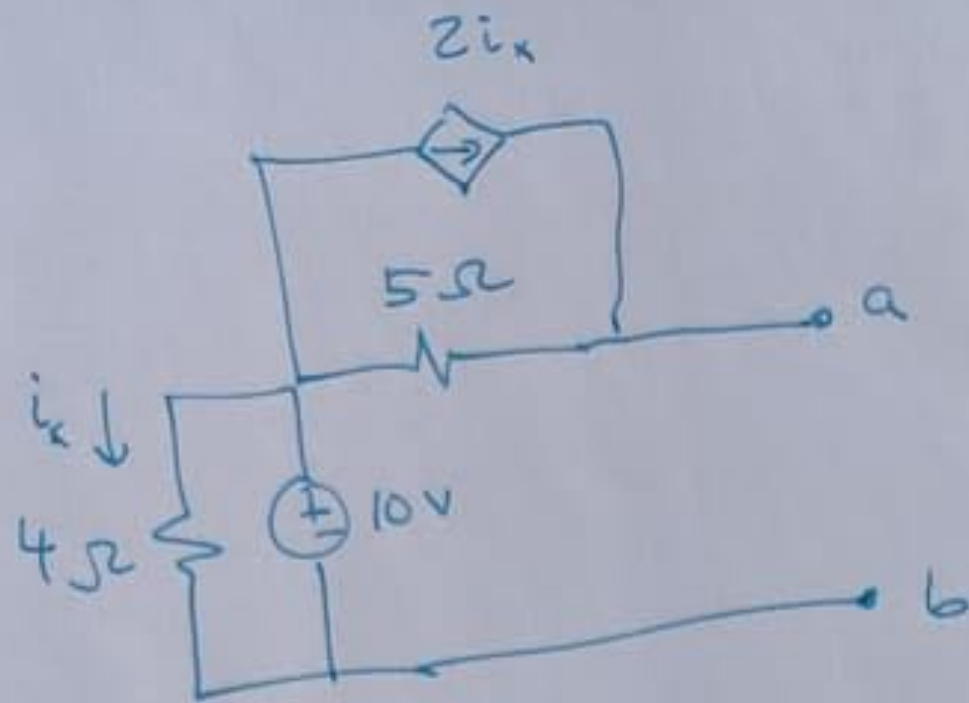

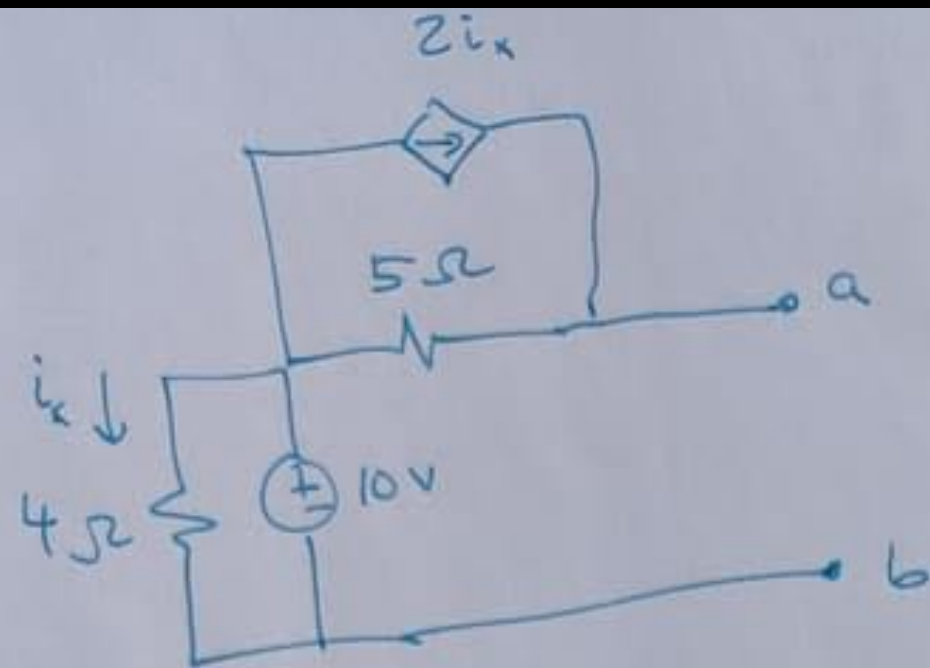
USING NORTON'S THEOREM
FIND R_N and I_N
at terminals a, b




USING NORTON'S THEOREM

FIND R_N and I_N
at terminals a, b

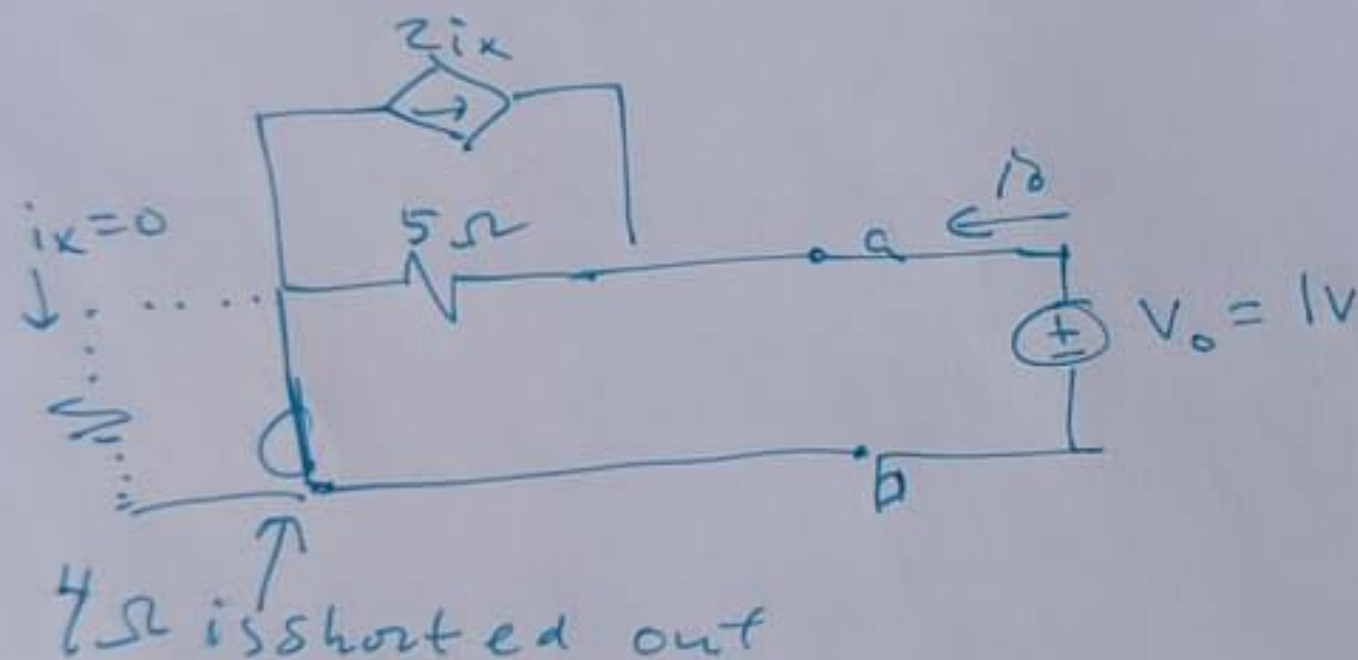- Set independent voltage source to zero
- We have ~~independent~~ source \Rightarrow connect voltage source V_0 to a, b terminal.
(we choose $V_0 = 1V$)



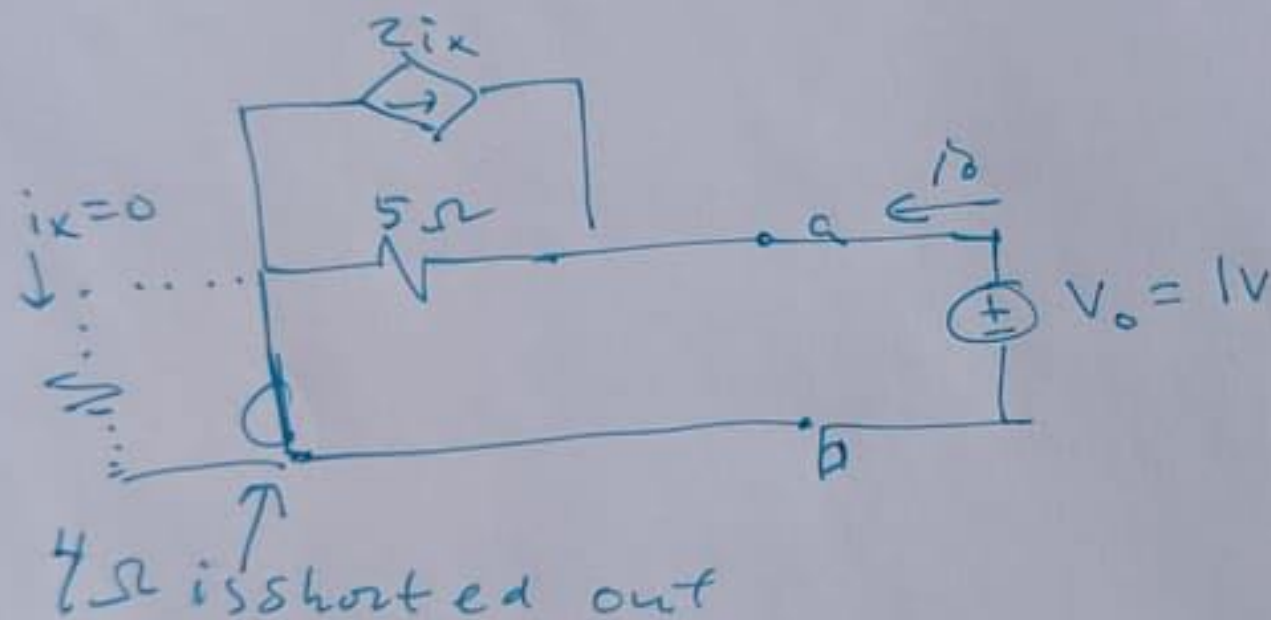


Everything is now in parallel

At node a: $i_o = \frac{1V}{5\Omega} = 0.2 A$

We have $R_N = \frac{V_o}{i_o} = \frac{1}{0.2} = 5 [\Omega]$

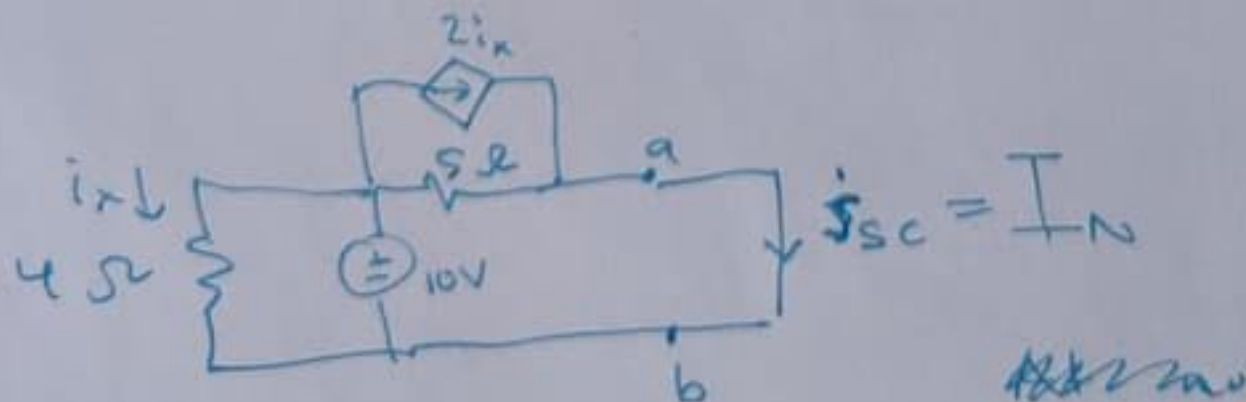Find I_N : short terminal ab and find isc



All still in parallel:

$i_x = \frac{10}{4} = 2.5 (A)$

At node a, KCL gives:

$i_{sc} = \frac{10}{5} + 2i_x = 2 + 2(2.5) = \underline{\underline{7A}}$

Norton and Thevenin Summary:


With V_{Th} , I_N , and $R_{Th} = R_N$ related, finding the Thevenin or Norton equivalent circuit requires that we find:

- The open-circuit voltage across terminals *a and b*.
- The short-circuit current at terminals *a and b*.
- The equivalent or input resistance at terminals *a and b* when all independent sources are turned off.

Norton *versus* Thevenin

Norton current and Thevenin voltage are related to each other (source substitution) as:

$$I_N = V_{Th} / R_{Th}$$

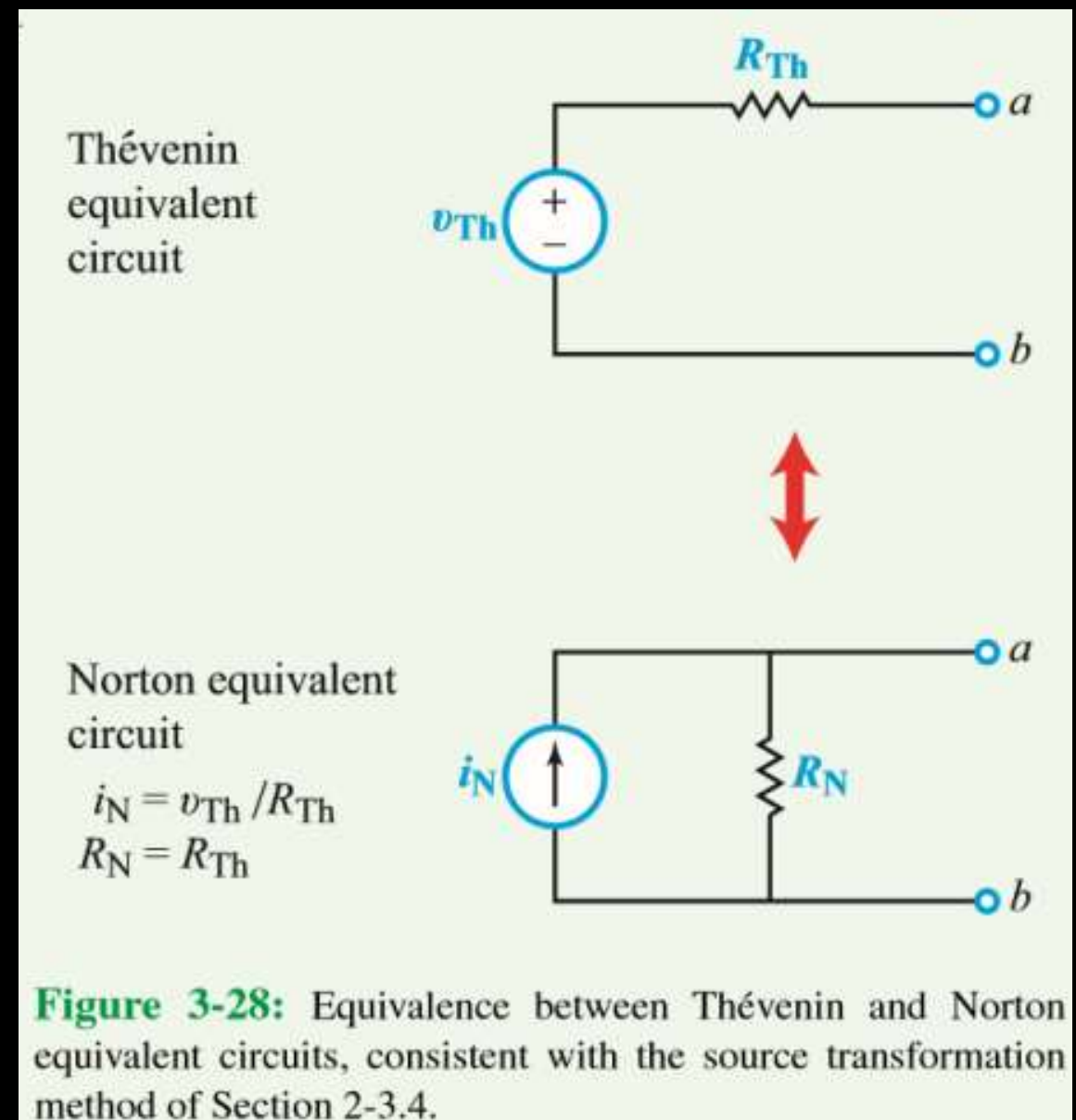

QUIZ TIME!!!