

ECE 101 F19 Lecture 1  
 Sept. 26, 2019  
 Course website:  
<https://ece101-fall19-01.courses.soe.ucsc.edu>  
 webcast: [ucsc.edu](http://ucsc.edu)  
 see ECE 101 video list  
[canvas.ucsc.edu/courses/24467](http://canvas.ucsc.edu/courses/24467)  
 watch announcements, posting, etc.  
 eTextbook can be freely downloadable from  
<http://cad.eecs.umich.edu/>

HW#1 (→ Quiz #1 next Th)  
 1) 1-1  
 2) 1-5  
 3) 1-14  
 4) 1-16 (b) + (c)  
 5) 1-25  
 6) 1-29  
 7) 1-31

} will be in Qz 1  
 → (15 minutes)  
 no calculator.






# CIRCUIT ANALYSIS AND DESIGN


Fawwaz T. Ulaby, Michel M. Maharbiz,  
 & Cynthia M. Furse





Figure 1-1: Cell phone.



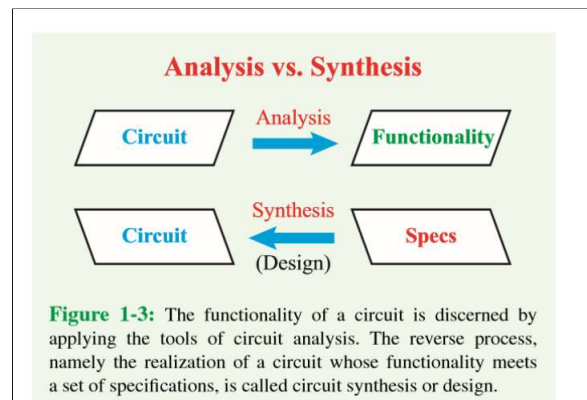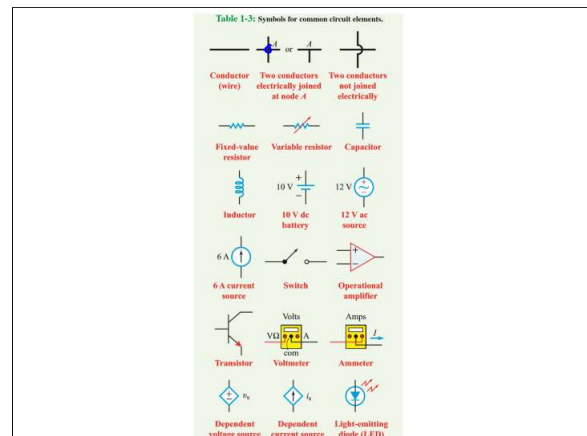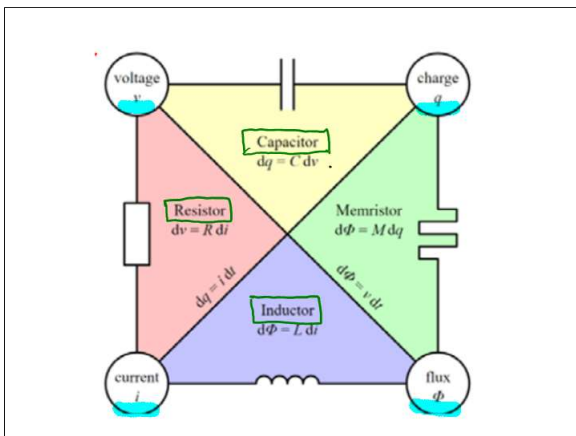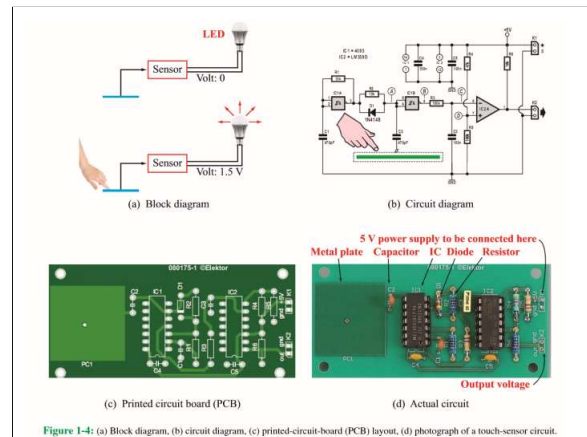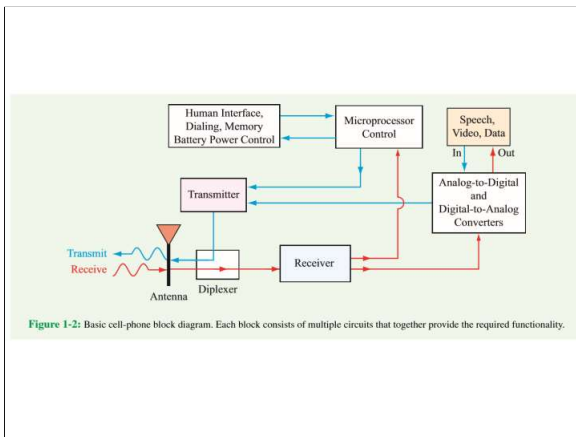

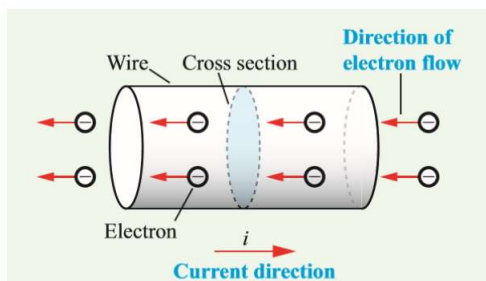

**Figure 1-11:** Direction of (positive) current flow through a conductor is opposite that of electrons.

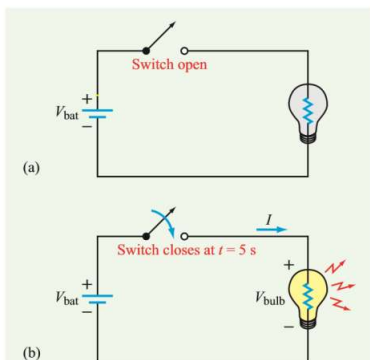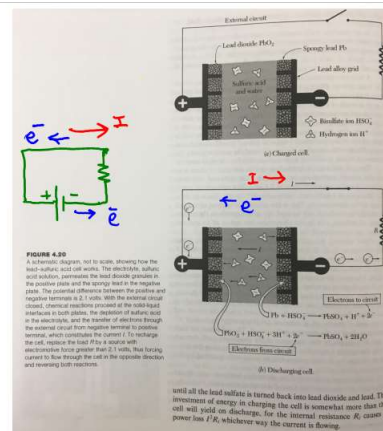

**Figure 1-21:** Current flow through a resistor (light-bulb filament) after closing the switch.

**Table 1-1: Fundamental and electrical SI units.**

Dimension	Unit	Symbol
<b>Fundamental:</b>		
Length	meter	m
Mass	kilogram	kg
Time	second	s
Electric charge	coulomb	C
Temperature	kelvin	K
Amount of substance	mole	mol
Luminous intensity	candela	cd
<b>Electrical:</b>		
Current	ampere	A
Voltage	volt	V
Resistance	ohm	$\Omega$
Capacitance	farad	F
Inductance	henry	H
Power	watt	W
Frequency	hertz	Hz

**Table 1-2: Multiple and submultiple prefixes.**

Prefix	Symbol	Magnitude
exa	E	$10^{18}$
peta	P	$10^{15}$
tera	T	$10^{12}$
giga	G	$10^9$
mega	M	$10^6$
kilo	k	$10^3$
milli	m	$10^{-3}$
micro	$\mu$	$10^{-6}$
nano	n	$10^{-9}$
pico	p	$10^{-12}$
femto	f	$10^{-15}$
atto	a	$10^{-18}$

**1.2** Use appropriate multiple and submultiple prefixes to express the following quantities:

- (a)  $4.71 \times 10^{-8}$  seconds (s)  $4.71 \times 10^{-9} \text{ s} = 4.71 \text{ ns}$
- (b)  $10.3 \times 10^8$  watts (W)
- (c)  $0.00000000321$  amps (A)  $3.21 \text{ nA}$
- (d)  $0.1$  meters (m)
- (e)  $8,760,000$  volts (V)  $8.76 \text{ MV}$
- (f)  $3.16 \times 10^{-16}$  hertz (Hz)

$$2V \oplus \oplus 1A \times 2V$$

$$1A \rightarrow 1\Omega \rightarrow 1V = 1A \times 1\Omega = 1V$$

► A power supply, such as a battery, offers a **voltage rise** across it as we follow the current from the terminal at which it enters (denoted with a (−) sign) to the terminal from which it leaves (denoted with a (+) sign). In contrast, a power recipient (such as a light bulb) exhibits a **voltage drop** across its corresponding terminals. This set of assignments of voltage polarities relative to the direction of current flow for devices generating power versus those consuming power is known as the **passive sign convention** (Fig. 1-22). We will adhere to it throughout the book. ◀

#### Passive Sign Convention

$p = vi$   
 $p > 0$  power delivered to device  
 $p < 0$  power supplied by device  
 Note that  $i$  direction is defined as entering (+) side of  $v$ .

Figure 1-22: Passive sign convention.

or simply

$$p = vi \quad (\text{W})$$

Consistent with the passive sign convention:


► The power delivered to a device is equal to the voltage across it multiplied by the current entering through its (+) voltage terminal. ◀

For example, a 100 W light bulb in a 120 V household electrical system draws 0.83 A of current.

If the algebraic value of  $p$  is negative, then the device is a supplier of energy. For an isolated electric circuit composed of multiple elements, the **law of conservation of power** requires that the algebraic sum of power for the entire circuit be always zero. That is, for a circuit with  $n$  elements,

$$\sum_{k=1}^n p_k = 0 \quad (1.10)$$

$$P = v \times i$$

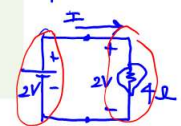


$$I = \frac{2V}{4\Omega} = 0.5[A]$$

$$P = V \cdot I = 2[V] \cdot 0.5[A] = 1[W]$$

$$\text{Energy}(+) = \int_0^t \text{power}(x) dt$$

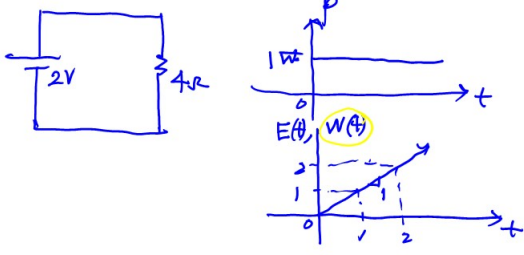Symbol for Energy  $E(t) \leftrightarrow \text{eBook } W(t)$



1.27 For each of the eight devices in the circuit of Fig. P1.27, determine whether the device is a supplier or a recipient of power and how much power it is supplying or receiving.

$$-64 - 27 = -91 \text{ W (generation)}$$

$$+24 + 10 + 8 + 4 + 24 + 21 = 91 \text{ W}$$

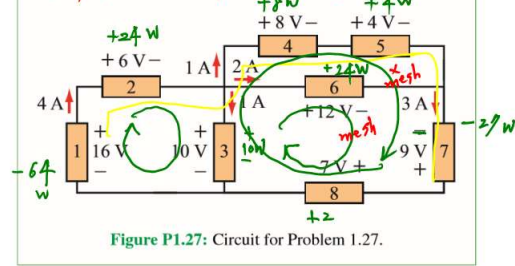


Figure P1.27: Circuit for Problem 1.27.

#### Table 1-4: Circuit terminology.

- ✓ **Node:** An electrical connection between two or more elements.
- ✓ **Ordinary node:** An electrical connection node that connects to only two elements.
- ✓ **Extraordinary node:** An electrical connection node that connects to three or more elements.
- ✓ **Branch:** Trace between two consecutive nodes with only one element between them.
- ✓ **Path:** Continuous sequence of branches with no node encountered more than once.
- ✓ **Extraordinary path:** Path between two adjacent extraordinary nodes.
- ✓ **Loop:** Closed path with the same start and end node.
- ✓ **Independent loop:** Loop containing one or more branches not contained in any other independent loop.
- ✓ **Mesh:** Loop that encloses no other loops.
- ✓ **In series:** Elements that share the same current. They have only ordinary nodes between them.
- ✓ **In parallel:** Elements that share the same voltage. They share two extraordinary nodes.

1.23 The plot in Fig. P1.23 displays the cumulative amount of charge  $q(t)$  that has exited a certain device up to time  $t$ . What is the current at

- \*(a)  $t = 2$  s
- (b)  $t = 6$  s
- (c)  $t = 12$  s



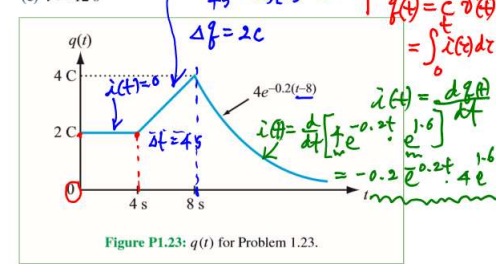


Figure P1.23:  $q(t)$  for Problem 1.23.

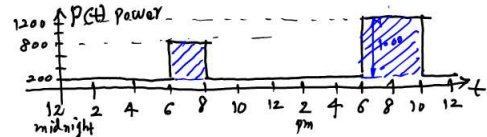

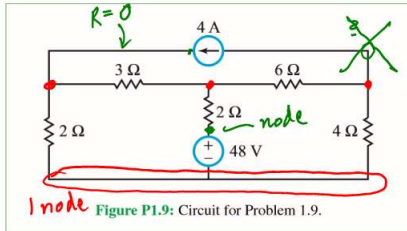1.9 For the circuit in Fig. P1.9:





- Identify and label all distinct nodes.
- Which of those nodes are extraordinary nodes?
- Identify all combinations of 2 or more circuit elements that are connected in series.
- Identify pairs of circuit elements that are connected in parallel.




[Q] Total energy consumed in one day?

$$\begin{aligned} 200 \times 24 &= 4800 \text{ W} \cdot \text{hr} \\ 1000 \times 2 &= 2000 \text{ W} \cdot \text{hr} \\ \hline 1000 \times 4 &= 4000 \text{ W} \cdot \text{hr} \\ 10,000 \text{ W} \cdot \text{hr} &= 10 \text{ kWh} \end{aligned}$$

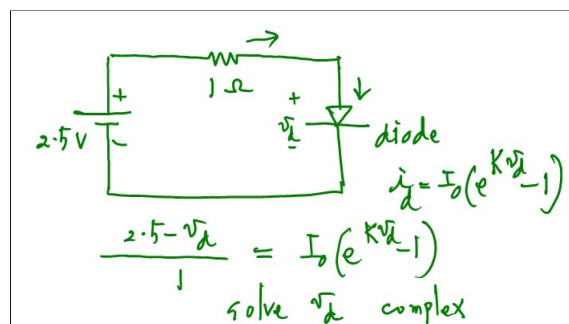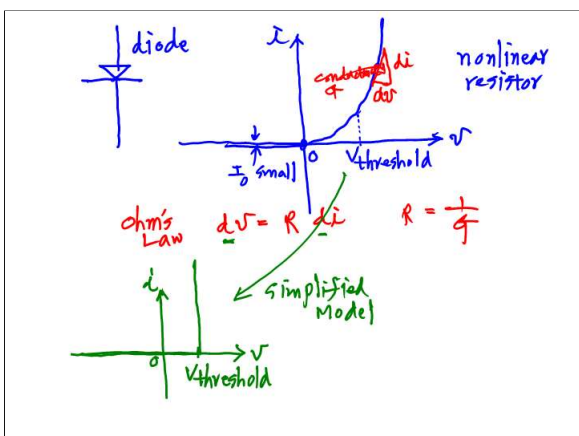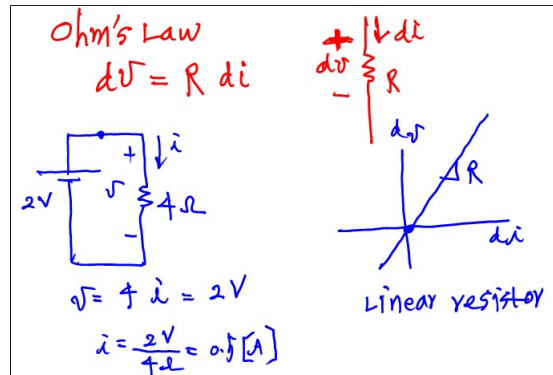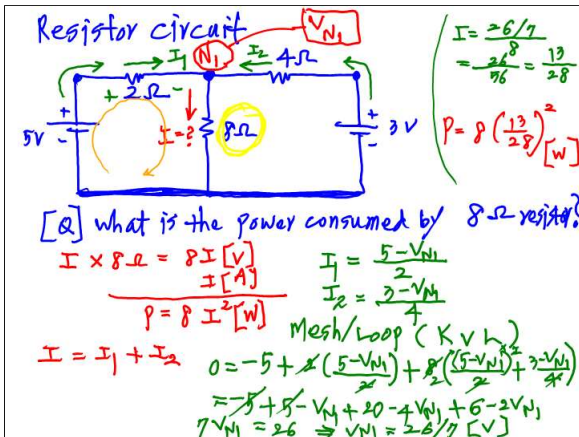
$$\begin{aligned} \text{Average power} = P_{av} &= \frac{W}{24 \text{ hr}} = \frac{10,000}{24} \\ &= 0.416 \text{ kW} \end{aligned}$$



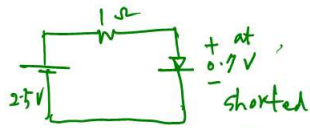

$$i = \frac{2.5 - 0.7}{1} = 1.8 \text{ [A]}$$

approximation

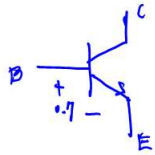

$V_{BE} = 0.7$  when BJT transistor is on (using the ideal diode model)