

ECE101  
F19  
Lecture 3  
Oct 3, 2019  
Quiz 1 Today  
HW #2 watch webpage this evening





Table 1-5: Voltage and current sources.







Independent Sources			
Ideal Voltage Source		Realistic Voltage Source	
$V_s$ or Battery	de source	$v_s$ or Any source*	Any source
Ideal Current Source		Realistic Current Source	
$i_s$ or de source	Any source	$i_s$ or Any source	Any source
Dependent Sources			
Voltage-Controlled Voltage Source (VCVS)		Voltage-Controlled Current Source (VCCS)	
$v_s = \alpha v_x$		$i_s = g v_x$	
Current-Controlled Voltage Source (CCVS)		Current-Controlled Current Source (CCCS)	
$v_s = r i_x$		$i_s = \beta i_x$	





Note:  $\alpha$ ,  $\beta$ ,  $r$ , and  $g$  are constants.  $v_x$  and  $i_x$  are a specific voltage and a specific current elsewhere in the circuit. \* $v_s$  and  $i_s$  represent voltage and current sources that may or may not be time-varying, whereas uppercase  $V$  and  $I$  denote dc sources.

Handwritten notes:  $2.5V$  and  $2.5A$  are circled. A note says "Interchangeable" with arrows pointing to the voltage and current source models.

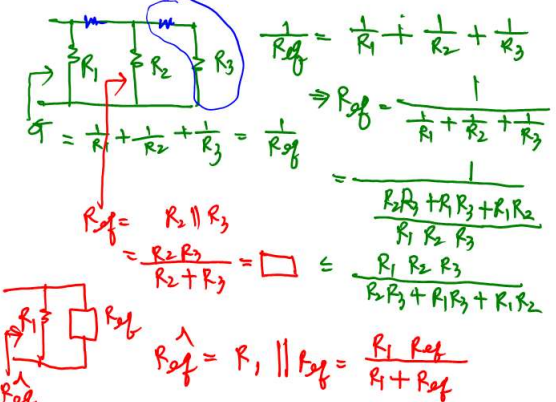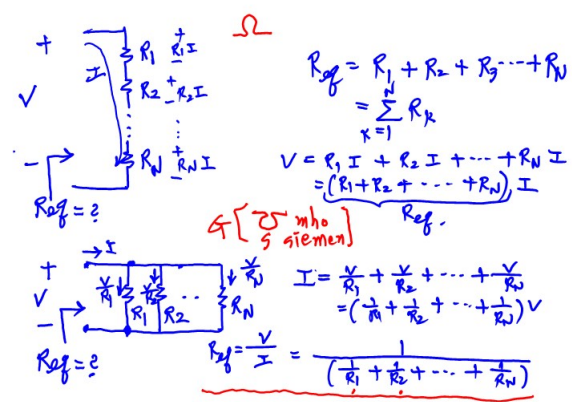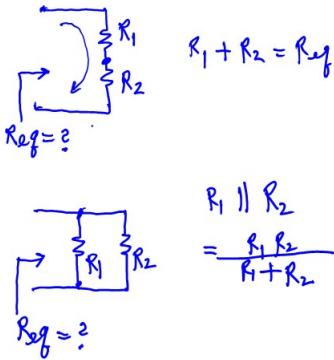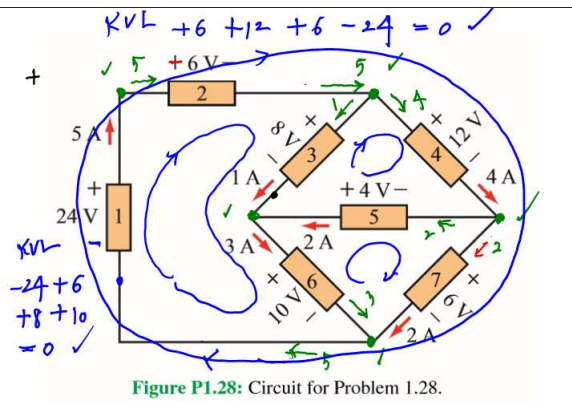- HW #2 Assignment on Oct 3.
- 1) Prob. 2-3
  - 2) Prob. 2-7
  - 3) Prob. 2-11
  - 4) Prob. 2-17
  - 5) Prob. 2-19
  - 6) Prob. 2-23
  - 7) Prob. 2-25
  - 8) Prob. 2-29
- 9) Prob. 2-34
- 10) Prob. 2-38
- one of these will be in QZ 2 on Oct. 10



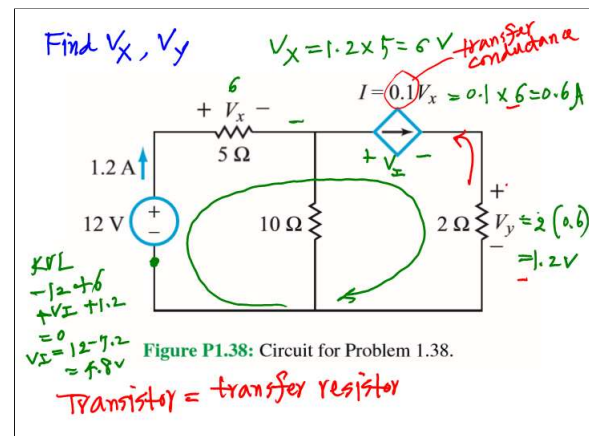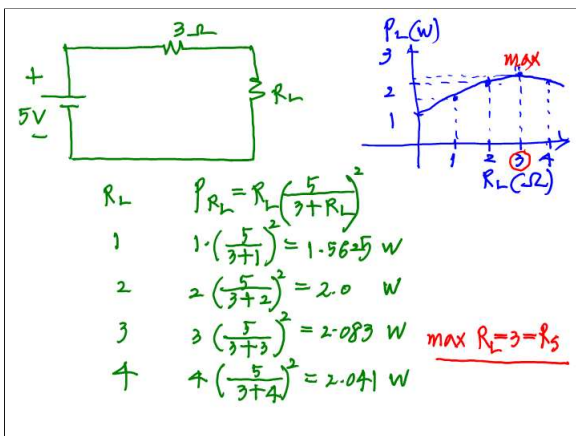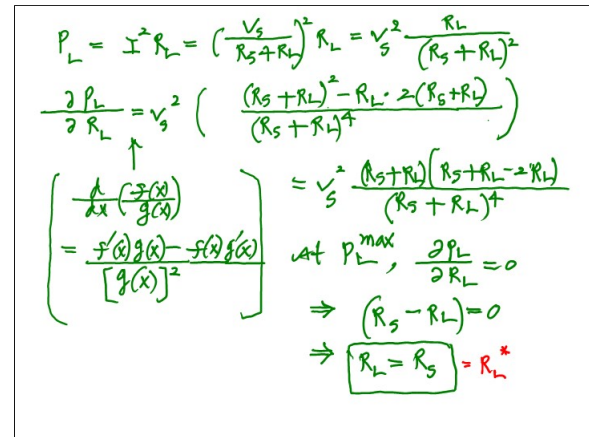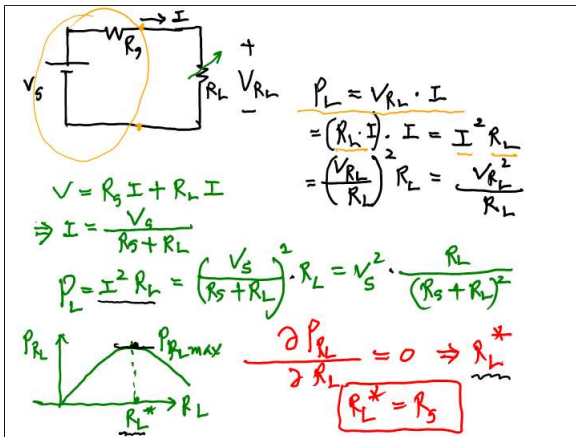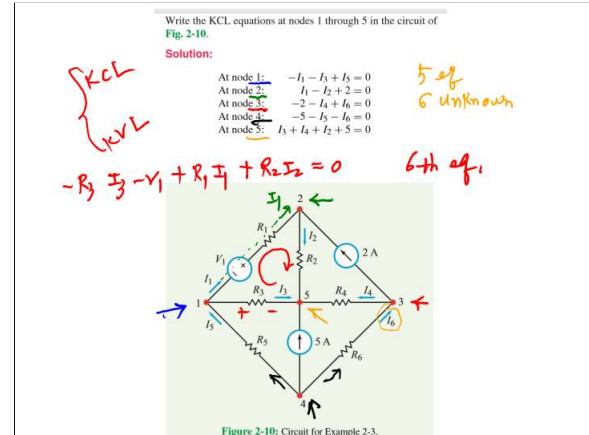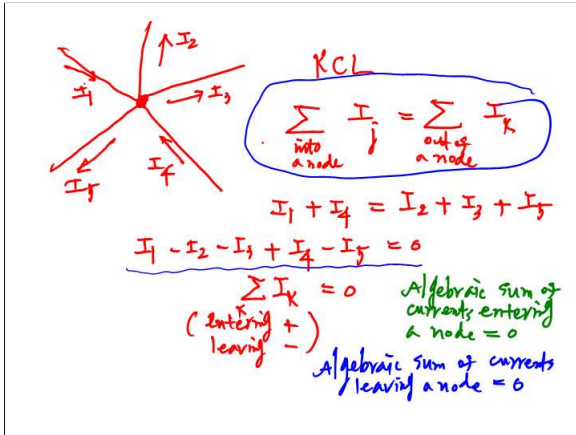

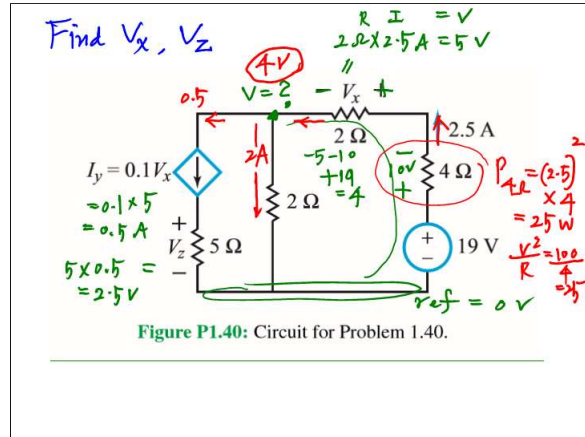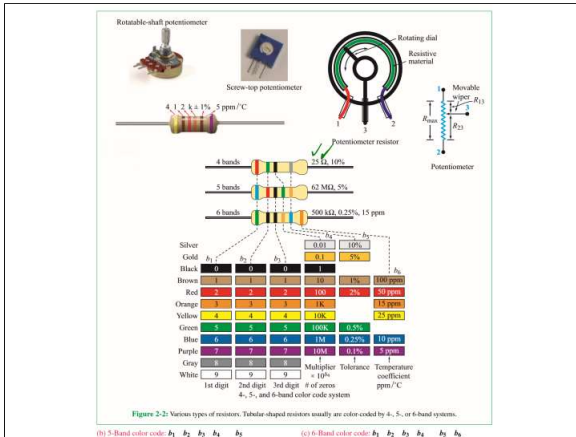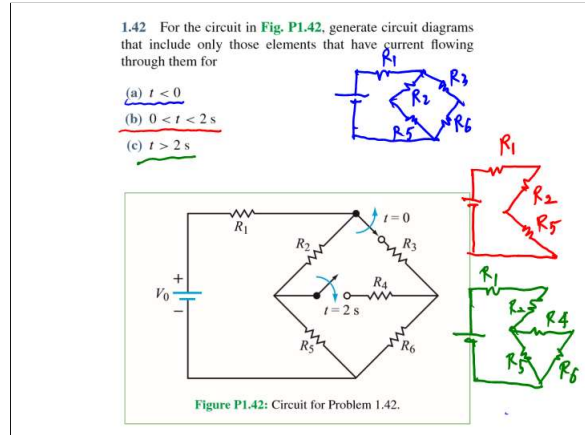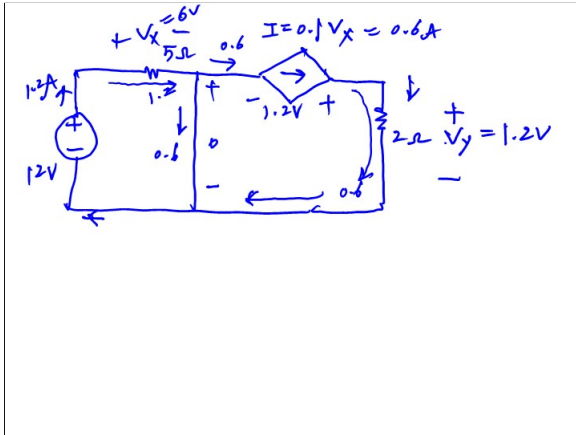

► The algebraic sum of the voltages around a closed loop must always be zero. ◀

This statement defines **Kirchhoff's voltage law** (KVL). In equation form, KVL is given by

$$\sum_{n=1}^N v_n = 0 \quad (\text{KVL}), \quad (2.11)$$

where  $N$  is the total number of branches in the loop and  $v_n$  is the  $n$ th voltage across the  $n$ th branch. Application of Eq. (2.11) requires the specification of a sign convention to use with it. Of those used in circuit analysis, the sign convention we chose to use in this book consists of two steps.

Hence, for the loop in Fig. 2-12, starting at the negative terminal of the 4 V voltage source, application of Eq. (2.11) yields

KVL:  $-4 + V_1 - V_2 - 6 + V_3 - V_4 = 0. \quad (2.12)$



Figure 2-12: One-loop circuit.

**Table 2-4:** Equally valid, multiple statements of Kirchhoff's Current Law (KCL) and Kirchhoff's Voltage Law (KVL).

- |            |   |
|------------|---|
| <b>KCL</b> | <ul style="list-style-type: none"> <li>Sum of all currents entering a node = 0<br/>[<math>i = "+"</math> if entering; <math>i = "-"</math> if leaving]</li> <li>Sum of all currents leaving a node = 0<br/>[<math>i = "+"</math> if leaving; <math>i = "-"</math> if entering]</li> <li>Total of currents entering = Total of currents leaving</li> </ul> |
| <b>KVL</b> | <ul style="list-style-type: none"> <li>Sum of voltages around closed loop = 0<br/>[<math>v = "+"</math> if + side encountered first in clockwise direction]</li> <li>Total voltage rise = Total voltage drop</li> </ul>   |
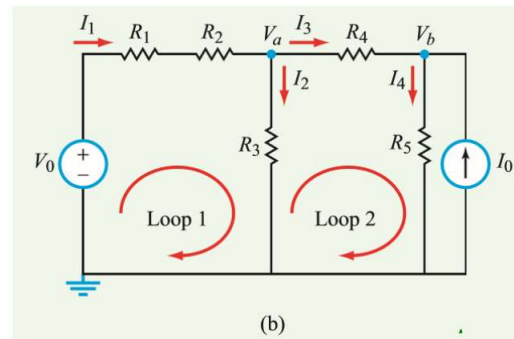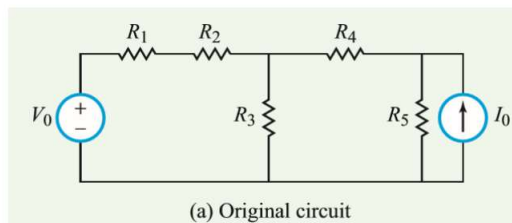
#### KCL/KVL Solution Recipe

- Use KCL, KVL, and Ohm's law to develop as many independent equations as the number of unknowns ( $N$ ).
  - (a) Write as many KVL loop equations as you can, picking up at least one additional circuit element for each loop. Let  $M$  be the number of such loop equations. Exclude loops that go through current sources.
  - (b) Write  $(N - M)$  KCL equations, making sure each node picks up an additional current.
- Write the equations in standard form (see Eq. (B.2) in Appendix B).
- Cast the standard-form equations in matrix form, as in Eqs. (B.19) and (B.20) of Appendix B.
- Apply matrix inversion to compute the values of the circuit unknowns (Appendix B).



#### (b) KVL equations

The circuit contains two independent loops that do not contain the current source  $I_0$ . The associated KVL equations are:

$$\begin{aligned} -V_0 + I_1 R_1 + I_1 R_2 + R_3 I_2 &= 0 & \text{(Loop 1),} \\ -I_2 R_3 + I_3 R_4 + I_4 R_5 &= 0 & \text{(Loop 2).} \end{aligned}$$

*4 unknowns  
2 equations*

Alternatively, we can replace either of the two loop equations with the KVL equation for the perimeter loop that includes both of them, namely the loop that starts at the ground node, then goes clockwise through  $V_0$ ,  $R_1$ ,  $R_2$ ,  $R_4$ , and  $R_5$ , and back to the ground node. Either approach leads to the same final result.

#### (c) KCL equations

We have two extraordinary nodes (in addition to the ground node). We designate their voltages as shown in Fig. 2-14(b). With current defined as positive when entering a node, their KCL equations are

$$\begin{aligned} I_1 - I_2 - I_3 &= 0 & \text{(Node a),} \\ I_3 - I_4 + I_0 &= 0 & \text{(Node b).} \end{aligned}$$

*additional  
2 equations*

#### (d) Arrange equations in matrix form

*4 equations  
⇒*

$$\underbrace{\begin{bmatrix} (R_1 + R_2) & R_3 & 0 & 0 \\ 0 & -R_3 & R_4 & R_5 \\ 1 & -1 & -1 & 0 \\ 0 & 0 & 1 & -1 \end{bmatrix}}_A \underbrace{\begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix}}_I = \underbrace{\begin{bmatrix} V_0 \\ 0 \\ 0 \\ -I_0 \end{bmatrix}}_B$$

*4 unknowns*

This is in the form

$$AI = B.$$

#### (e) Matrix inversion



$$I = A^{-1} B = \frac{\text{Adj } A}{|A|} B$$

After replacing the sources and resistors with their specified numerical values, matrix reduction, per MATLAB, MathScript, or the procedure outlined in Appendix B-2, leads to

$$\begin{aligned} I_1 &= 1.1 \text{ A}, & I_2 &= 0.9 \text{ A}, \\ I_3 &= 0.2 \text{ A}, & I_4 &= 1 \text{ A}. \end{aligned}$$



Find  $V_{ab}$

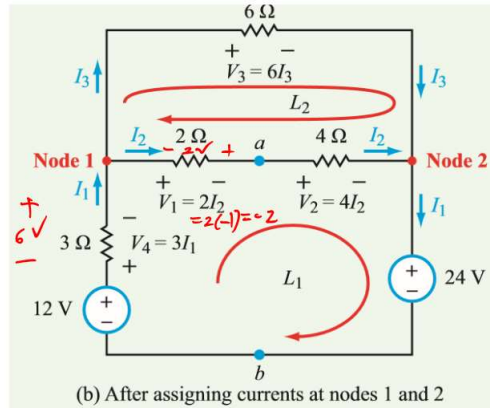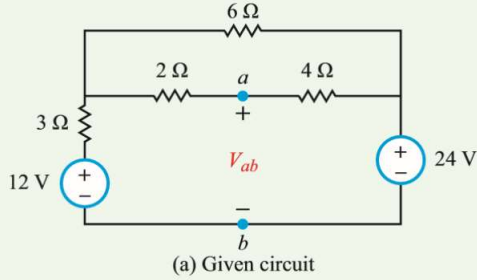

In terms of the labeled voltages, application of KVL around the two loops gives

$$-12 + V_4 + V_1 + V_2 + 24 = 0, \quad \text{(KVL for Loop 1)} \quad (2.14a)$$

$$V_3 - V_2 - V_1 = 0. \quad \text{(KVL for Loop 2)} \quad (2.14b)$$

Using Ohm's law for the four resistors, the two KVL equations become

$$-12 + 3I_1 + 2I_2 + 4I_2 + 24 = 0, \quad \text{(KVL for Loop 1)} \quad (2.15a)$$

$$6I_3 - 4I_2 - 2I_2 = 0. \quad \text{(KVL for Loop 2)} \quad (2.15b)$$

In terms of the labeled voltages, application of KVL around the two loops gives

$$-12 + V_4 + V_1 + V_2 + 24 = 0, \quad \text{(KVL for Loop 1)} \quad (2.14a)$$

$$V_3 - V_2 - V_1 = 0. \quad \text{(KVL for Loop 2)} \quad (2.14b)$$

Using Ohm's law for the four resistors, the two KVL equations become

$$-12 + 3I_1 + 2I_2 + 4I_2 + 24 = 0, \quad \text{(KVL for Loop 1)} \quad (2.15a)$$

$$6I_3 - 4I_2 - 2I_2 = 0. \quad \text{(KVL for Loop 2)} \quad (2.15b)$$

The two simultaneous equations contain three unknowns, namely  $I_1$  to  $I_3$ . A third equation is supplied by KCL at node 1 or node 2:

$$I_1 = I_2 + I_3. \quad \text{(KCL @ node 1 or 2)} \quad (2.16)$$

Equations (2.15a), (2.15b), and (2.16) constitute 3 equations in 3 unknowns. We can solve for  $I_1$  to  $I_3$  either by the substitution method or by matrix inversion (Appendix B). To apply the latter, we need to cast the three equations in standard form:

$$\begin{aligned} 3I_1 + 6I_2 &= -12, \\ -6I_2 + 6I_3 &= 0, \\ I_1 - I_2 - I_3 &= 0. \end{aligned}$$

3 unknowns  
2 equations  
1 additional eq.

3 unknowns  
3 equations

$$3I_1 + 6I_2 = -12,$$

$$-6I_2 + 6I_3 = 0,$$

$$I_1 - I_2 - I_3 = 0.$$

In matrix form:

$$\begin{bmatrix} 3 & 6 & 0 \\ 0 & -6 & 6 \\ 1 & -1 & -1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} -12 \\ 0 \\ 0 \end{bmatrix}.$$


Matrix inversion, as outlined in Appendix B, leads to

$$I_1 = -2 \text{ A}, \quad I_2 = -1 \text{ A}, \quad I_3 = -1 \text{ A}.$$


$$V_2 = 4I_2 = 4(-1) = -4 \text{ V} \quad V_{ab} = -4 + 24 = 20 \text{ V}$$

Find  $V_{ab}$



Loop Current Method

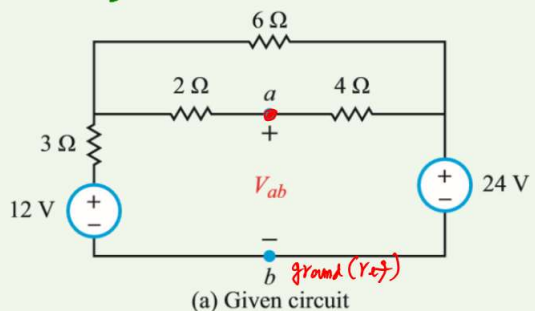

Find  $V_{ab}$

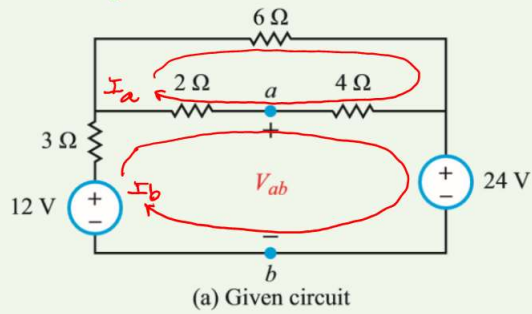


Find  $V_{ab}$

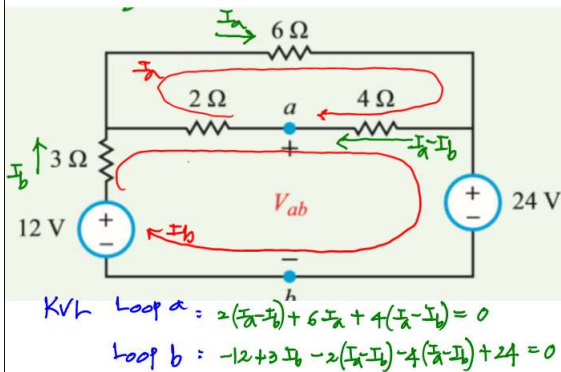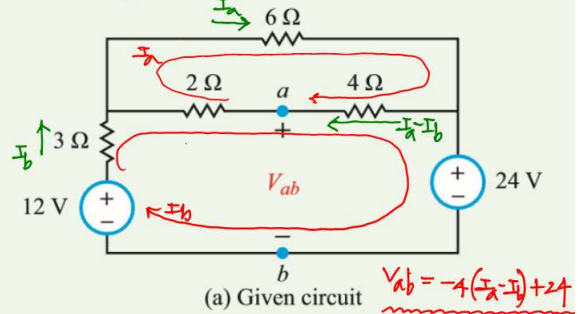

$$\begin{aligned} 12I_x - 6I_b &= 0 \\ -6I_x + 9I_b &= -12 \\ \Rightarrow 2I_x - I_b &= 0 \quad (\Rightarrow I_b = 2I_x) \\ -2I_x + 3I_b &= -4 \\ \text{add 2 eqns} \Rightarrow 0 + 2I_b &= -4 \Rightarrow I_b = -2 \text{ A} \\ 2I_x = I_b \Rightarrow I_x &= \frac{I_b}{2} = -1 \text{ A} \\ V_{ab} &= -4(I_x - I_b) + 24 \\ &= -4(-1 - (-2)) + 24 = 20 \checkmark \end{aligned}$$

Alternative Method: Nodal Analysis

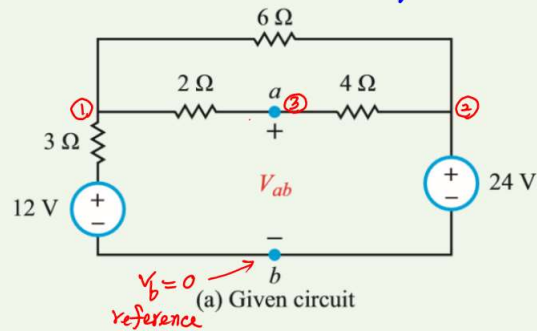

KCL

node 3:  $\frac{V_3 - V_1}{2} - \frac{V_3 - 24}{4} = 0$  (1)  
 node 1:  $\frac{12 - V_1}{3} - \frac{V_1 - 24}{6} - \frac{V_1}{2} = 0$  (2)

(1)  $\Rightarrow 2V_3 - 2V_1 - V_3 + 24 = 0$   
 $2V_3 - 2V_1 = -24$   
 $V_3 - V_1 = -12$

(2)  $\Rightarrow 2(12 - V_1) - (V_1 - 24) - 3(V_1 - V_3) = 0$   
 $24 - 2V_1 - V_1 + 24 - 3V_1 + 3V_3 = 0$   
 $-6V_1 + 3V_3 = -48$   
 $-2V_1 + V_3 = -16$

$\Rightarrow \begin{bmatrix} V_1 \\ V_3 \end{bmatrix} = \frac{1}{4} \begin{bmatrix} 1 & 3 \\ 2 & 2 \end{bmatrix} \begin{bmatrix} -24 \\ -16 \end{bmatrix} = \frac{1}{4} \begin{bmatrix} 18 \\ 20 \end{bmatrix}$

$V_{ab} = V_3 - V_1 = \frac{18}{4} - \frac{20}{4} = -\frac{2}{4} = -0.5$  (Wait, this contradicts the previous result. Let's recheck the nodal analysis.)

Rechecking Nodal Analysis:  
 Node 1:  $\frac{12 - V_1}{3} - \frac{V_1 - 24}{6} - \frac{V_1}{2} = 0$   
 $\frac{2(12 - V_1) - (V_1 - 24) - 3V_1}{6} = 0$   
 $24 - 2V_1 - V_1 + 24 - 3V_1 = 0$   
 $-6V_1 + 48 = 0$   
 $-6V_1 = -48$   
 $V_1 = 8$

Node 3:  $\frac{V_3 - V_1}{2} - \frac{V_3 - 24}{4} = 0$   
 $\frac{V_3 - 8}{2} - \frac{V_3 - 24}{4} = 0$   
 $2(V_3 - 8) - (V_3 - 24) = 0$   
 $2V_3 - 16 - V_3 + 24 = 0$   
 $V_3 + 8 = 0$   
 $V_3 = -8$

$V_{ab} = V_3 - V_1 = -8 - 8 = -16$  (This also contradicts the previous result. Let's recheck the circuit diagram.)

Rechecking Circuit Diagram: The 24V source is in parallel with the 4Ω resistor. The 12V source is in series with the 3Ω resistor. The 2Ω resistor is in parallel with the 6Ω resistor. The 4Ω resistor is in series with the 24V source. The voltage V\_ab is across the 4Ω resistor.

Rechecking KCL:  
 Node 3:  $\frac{V_3 - V_1}{2} - \frac{V_3 - 24}{4} = 0$   
 Node 1:  $\frac{12 - V_1}{3} - \frac{V_1 - 24}{6} - \frac{V_1}{2} = 0$

Rechecking Equations:  
 (1)  $\Rightarrow 2V_3 - 2V_1 - V_3 + 24 = 0$   
 $V_3 - 2V_1 = -24$   
 (2)  $\Rightarrow 2(12 - V_1) - (V_1 - 24) - 3(V_1 - V_3) = 0$   
 $24 - 2V_1 - V_1 + 24 - 3V_1 + 3V_3 = 0$   
 $-6V_1 + 3V_3 = -48$   
 $-2V_1 + V_3 = -16$

$\Rightarrow \begin{bmatrix} V_1 \\ V_3 \end{bmatrix} = \frac{1}{4} \begin{bmatrix} 1 & 3 \\ 2 & 2 \end{bmatrix} \begin{bmatrix} -24 \\ -16 \end{bmatrix} = \frac{1}{4} \begin{bmatrix} 18 \\ 20 \end{bmatrix}$

$V_{ab} = V_3 - V_1 = \frac{18}{4} - \frac{20}{4} = -\frac{2}{4} = -0.5$

Cramer's Rule

$$\begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} = \begin{bmatrix} b_1 \\ b_2 \end{bmatrix} \quad AX = b$$

$$x_1 = \frac{\begin{vmatrix} b_1 & a_{12} \\ b_2 & a_{22} \end{vmatrix}}{\begin{vmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{vmatrix}} \quad x_2 = \frac{\begin{vmatrix} a_{11} & b_1 \\ a_{21} & b_2 \end{vmatrix}}{\begin{vmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{vmatrix}}$$

$$\begin{bmatrix} 2 & -3 \\ -2 & 1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} -24 \\ -16 \end{bmatrix}$$

$$V_2 = \frac{\begin{vmatrix} 2 & -24 \\ -2 & -16 \end{vmatrix}}{\begin{vmatrix} 2 & -3 \\ -2 & 1 \end{vmatrix}} = \frac{2 \times (-16) - (-24) \times (-2)}{2 \times 1 - (-3) \times (-2)} = \frac{-32 - 48}{-4} = \frac{-80}{-4} = 20 = V_{ab} \text{ (Ans)}$$