
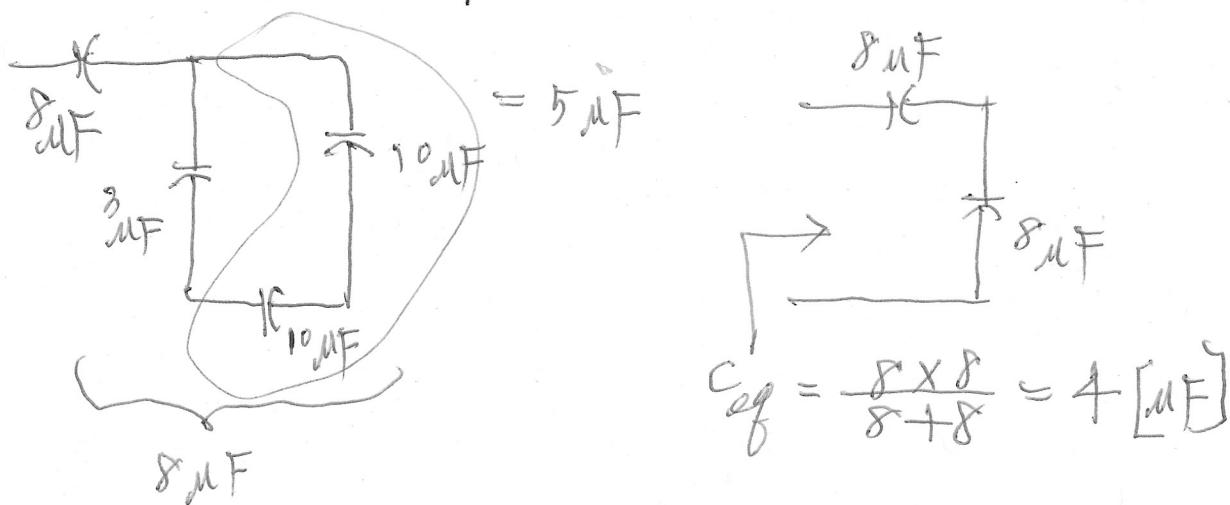


ECE101F19 Quiz 6, Nov. 7, 2019

Name _____ Student ID _____

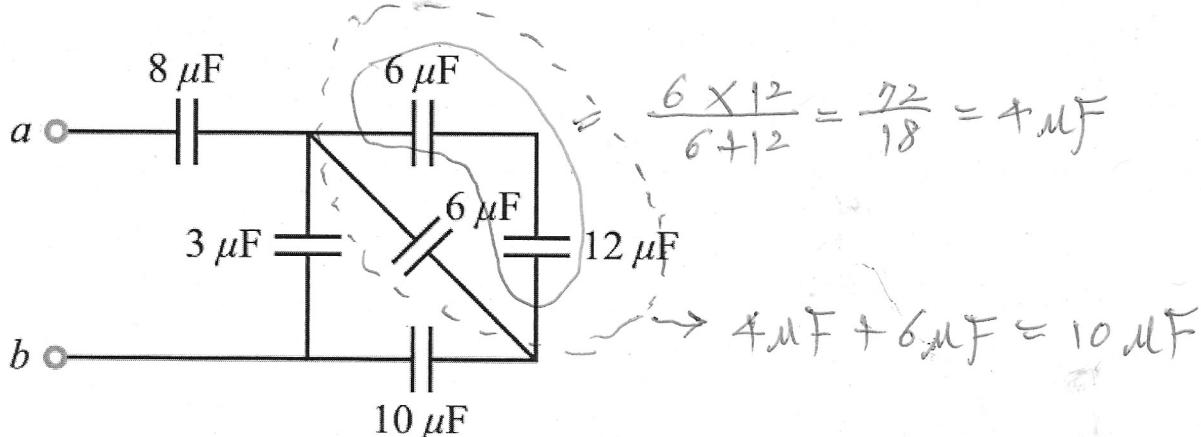(Part 1) (5points) Find the equivalent capacitance between terminals a and b.



Part 2 (5 points) What is the voltage across the $8 \mu F$ capacitor when $10 V$ is applied between a and b, i.e., $V_a - V_b = 2V$

